

## **CSE251: ELECTRONIC DEVICES AND CIRCUITS**

### **EXPERIMENT 4: STUDY OF HALF-WAVE & FULL-WAVE RECTIFIERS**

**NAME : ANIKA ISLAM**

**ID : 21101298**

**SECTION : 12**

**GROUP : 03**

**SEMESTER : SPRING 2023**

**DATE OF PERFORMANCE : 28/02/2023**

**DATE OF SUBMISSION : 13/03/2023**

## Data Sheet

### Experimental Observation: HW Rectifier

#### 1. HW Rectifier without Capacitor:

Peak output voltage,  $V_p$  (oscilloscope) = **4.24V**

Average or DC output voltage,  $V_{dc}$  (multimeter in DC mode) = **1.24V**

RMS or AC output voltage,  $V_{r-rms}$  (multimeter in AC mode) = **1.699V**

#### 2. HW Rectifier with $1\mu F$ Capacitor: $C = 0.99\mu F$

Peak output voltage,  $V_p$  (oscilloscope) = **4.24V**

Peak to peak ripple voltage,  $V_{r(p-p)}$  (oscilloscope) = **3.14V**

Average or DC value of the Ripple voltage,  $V_{dc}$  (multimeter in DC mode) = **2.23**

RMS or AC value of the ripple voltage,  $V_{r-rms}$  (multimeter in AC mode) = **1.062**

Ripple factor,  $r = V_{r-rms}/V_{dc}$  = **0.476**

#### 3. HW Rectifier with $4.7\mu F$ Capacitor: $C = 4.96\mu F$

Peak output voltage,  $V_p$  (oscilloscope) = **4.08V**

Peak to peak ripple voltage,  $V_{r(p-p)}$  (oscilloscope) = **1.28V**

Average or DC value of the ripple voltage,  $V_{dc}$  (multimeter in DC mode) = **3.087V**

RMS or AC value of the ripple voltage,  $V_{r-rms}$  (multimeter in AC mode) = **0.378**

Ripple factor,  $r = V_{r-rms}/V_{dc}$  = **0.116**

### Theoretical Calculation: HW Rectifier

#### 1. HW Rectifier Without Capacitor:

Peak output voltage,  $V_p$  (see the experimental observation) = **4.24**

Peak input voltage,  $V_m$  = **5V**

Diode voltage,  $V_{D0} = 0.7V$

DC output voltage of the rectifier,  $V_{dc} = \frac{V_m}{\pi} - \frac{V_{D0}}{2} = 1.24V$

RMS or AC output voltage,  $V_{r-rms} = \frac{V_f}{2} = 2.12$

#### 2. HW Rectifier With $1\mu F$ Capacitor:

Peak output voltage,  $V_p$  (see the experimental observation) = **4.24**

Peak to peak ripple voltage,  $V_{r(p-p)}$  (see the experimental observation) = **3.44**

DC value of the ripple voltage,  $V_{dc} = V_p - \frac{V_{r(p-p)}}{2} = 2.52$

RMS value of the ripple voltage,  $V_{r-rms} = \frac{V_{r(p-p)}}{2\sqrt{3}} = 0.993$

Ripple factor,  $r = V_{r-rms}/V_{dc}$  = **0.394**

#### 3. HW Rectifier with $4.7\mu F$ Capacitor:

Peak output voltage,  $V_p$  (see the experimental observation) = **4.08**

Peak to peak ripple voltage,  $V_{r(p-p)}$  (see the experimental observation) = **1.28**

DC value of the ripple voltage,  $V_{dc} = V_p - \frac{V_{r(p-p)}}{2} = 3.44$

RMS value of the ripple voltage,  $V_{r-rms} = \frac{V_{r(p-p)}}{2\sqrt{3}} = 0.3695$

Ripple factor,  $r = V_{r-rms}/V_{dc}$  = **0.1074**

### Experimental Observation: FW Rectifier

#### 1. FW Rectifier without Capacitor:

Peak output voltage,  $V_p$  (oscilloscope) = **3.68V**

Average or DC output voltage,  $V_{dc}$  (multimeter in DC mode) = **2.061**

RMS or AC output voltage,  $V_{r-rms}$  (multimeter in AC mode) = **1.281**

#### 2. FW Rectifier with $1\mu F$ Capacitor:

Peak output voltage,  $V_p$  (oscilloscope) = **3.52V**

Peak to peak ripple voltage,  $V_{r(p-p)}$  (oscilloscope) = **1.76**

Average or DC value of the ripple voltage,  $V_{dc}$  (multimeter in DC mode) = **2.621**

RMS or AC value of the ripple voltage,  $V_{r-rms}$  (multimeter in AC mode) = **0.540**

Ripple factor,  $r = V_{r-rms}/V_{dc}$  = **0.206028**

#### 3. FW Rectifier with $4.7\mu F$ Capacitor:

Peak output voltage,  $V_p$  (oscilloscope) = **3.44V**

Peak to peak ripple voltage,  $V_{r(pp-p)}$  (oscilloscope) = **0.64V**

Average or DC value of the ripple voltage,  $V_{dc}$  (multimeter in DC mode) = **3.069**

RMS or AC value of the ripple voltage,  $V_{r-rms}$  (multimeter in AC mode) = **0.148**

Ripple factor,  $r = V_{r-rms}/V_{dc}$  = **0.0482**

### Theoretical Calculation: FW Rectifier

#### 1. FW Rectifier without Capacitor:

Peak output voltage,  $V_p$  (see the experimental observation) = **8.68V**

Peak input voltage,  $V_m$  = **5V**

Diode voltage,  $V_{D0} = 0.7 V$

DC output voltage of the rectifier,  $V_{dc} = \frac{2V_m}{\pi} - 2V_{D0} =$

RMS or AC output voltage,  $V_{r-rms} = \frac{V_p}{\sqrt{2}} =$

#### 2. FW Rectifier with $1\mu F$ Capacitor:

Peak output voltage,  $V_p$  (see the experimental observation) = **3.52**

Peak to peak ripple voltage,  $V_{r(pp-p)}$  (see the experimental observation) = **1.76**

DC value of the ripple voltage,  $V_{dc} = V_p - \frac{V_{r(pp-p)}}{2} =$  **2.64**

RMS value of the ripple voltage,  $V_{r-rms} = \frac{V_{r(pp-p)}}{2\sqrt{3}} =$  **0.508**

Ripple factor,  $r = V_{r-rms}/V_{dc} =$  **0.192**

#### 3. FW Rectifier with $4.7\mu F$ Capacitor:

Peak output voltage,  $V_p$  (see the experimental observation) = **3.44**

Peak to peak ripple voltage,  $V_p$  (see the experimental observation) = **0.64**

DC value of the ripple voltage,  $V_{dc} = V_p - \frac{V_{r(pp-p)}}{2} =$  **3.12**

RMS value of the ripple voltage,  $V_{r-rms} = \frac{V_{r(pp-p)}}{2\sqrt{3}} =$  **0.184**

Ripple factor,  $r = V_{r-rms}/V_{dc} =$  **0.058**


### Table for Comparison

Use the experimental and theoretical data for comparison.


	C( $\mu F$ )	Experimental Observation			Theoretical Calculation		
		V <sub>r-rms</sub> (V)	V <sub>dc</sub> (V)	Ripple Factor	V <sub>r-rms</sub> (V)	V <sub>dc</sub> (V)	Ripple Factor
HW	1	1.067	2.23	0.476	0.998	2.52	0.394
	4.7	0.378	3.367	0.116	0.3695	3.49	0.1074
FW	1	0.540	2.621	0.2060%	0.508	2.64	0.192
	4.7	0.148	3.069	0.0482	0.184	3.12	0.058

✓  
28/02/23

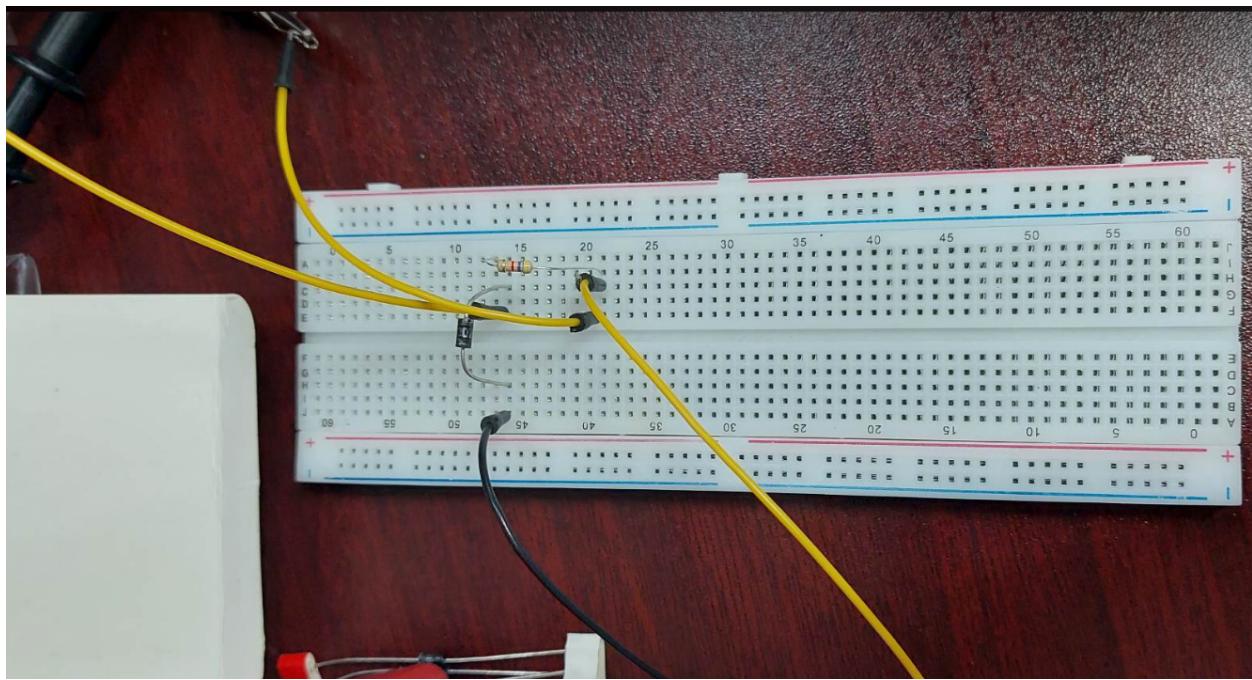
Circuit for Half-wave rectifier without capacitor :



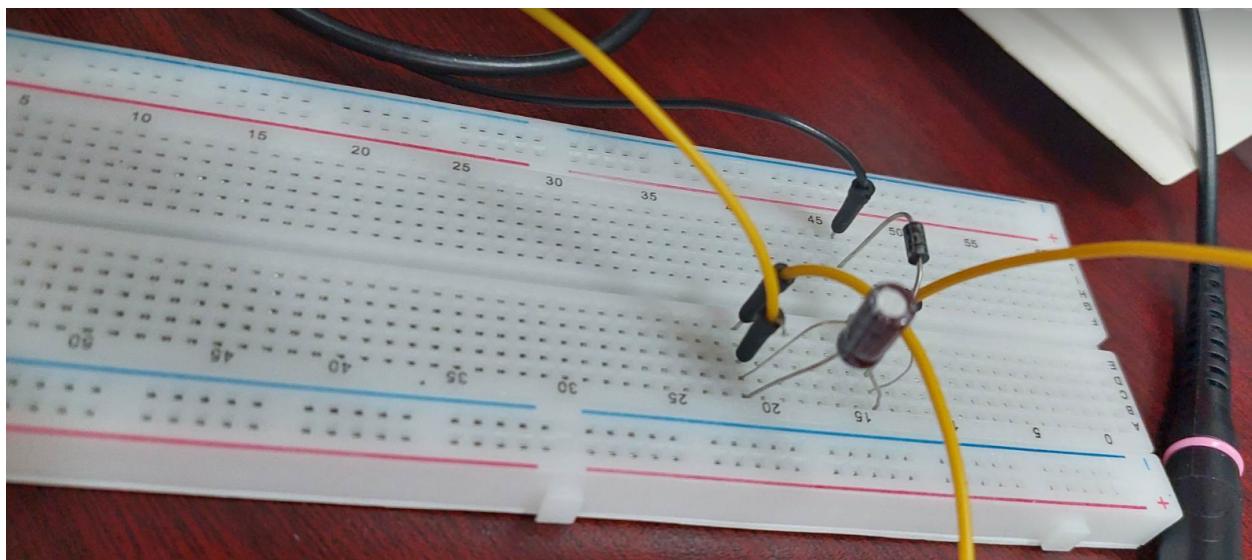
Circuit for Half-wave rectifier with 1uF capacitor :



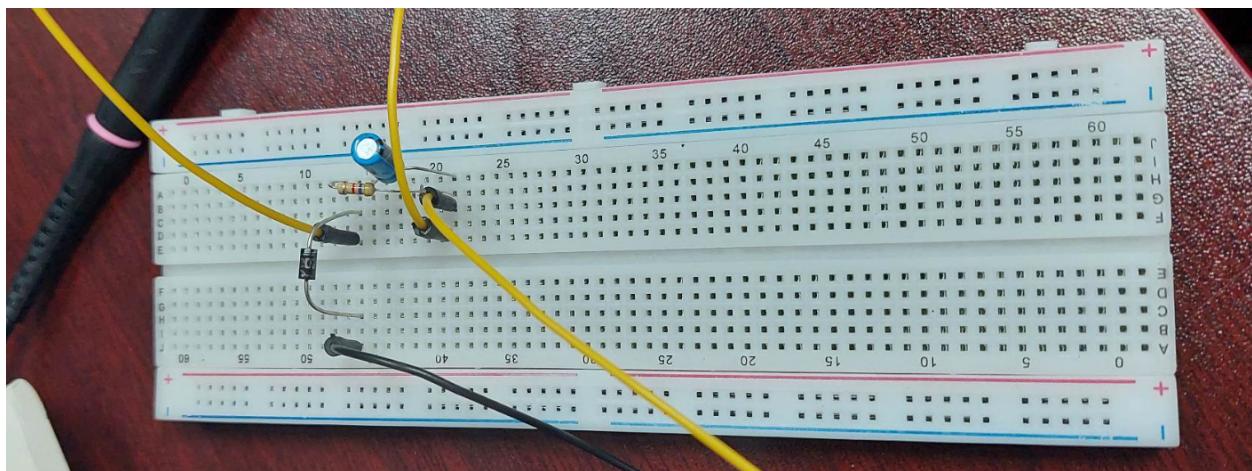
Circuit for Half-wave rectifier with 4.7uF capacitor :



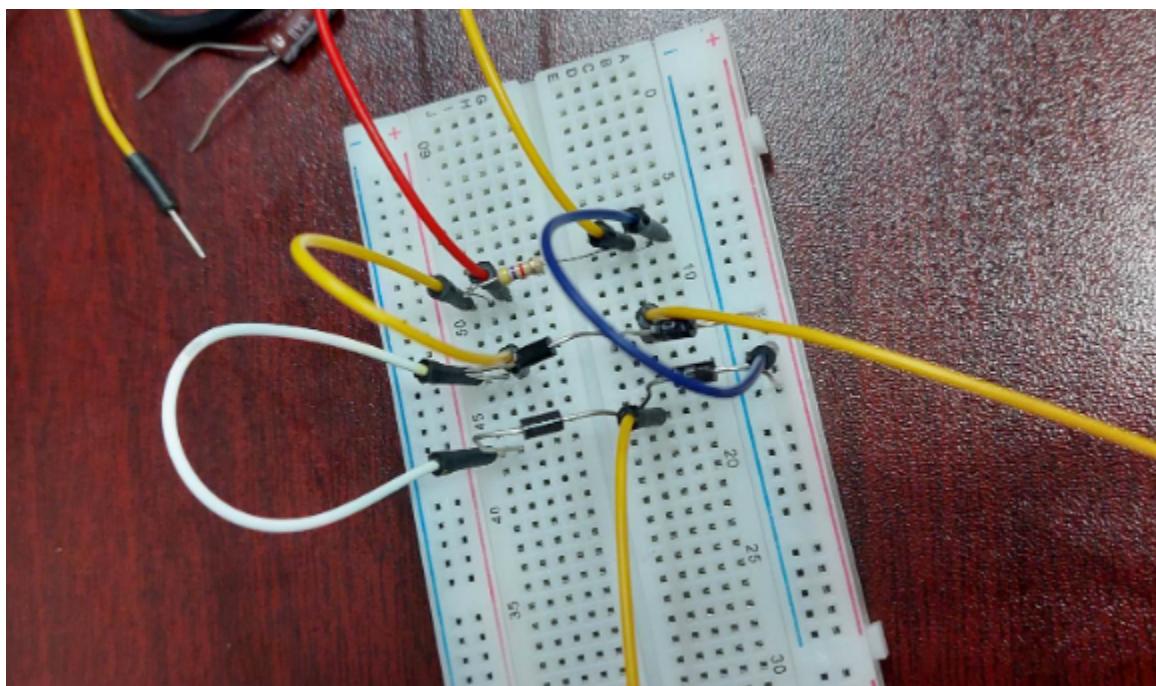
Circuit for Full-wave rectifier without capacitor :



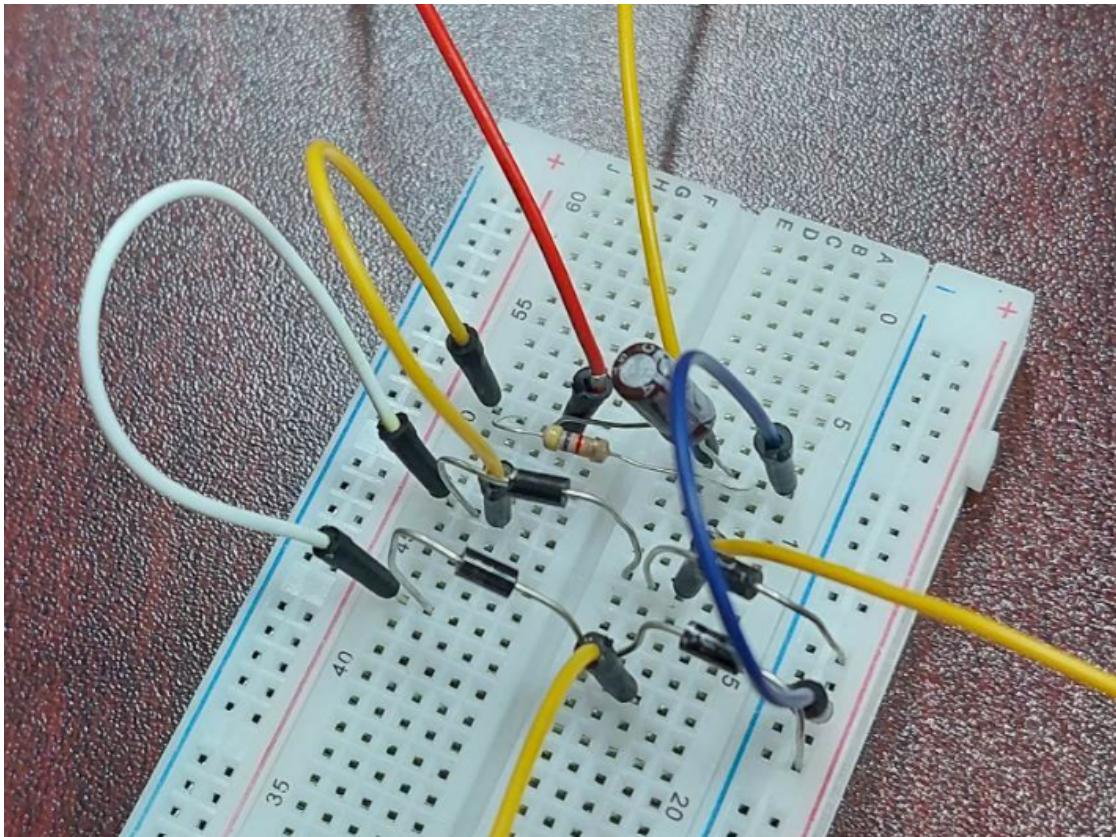
Circuit for Full-wave rectifier with 1uF capacitor :



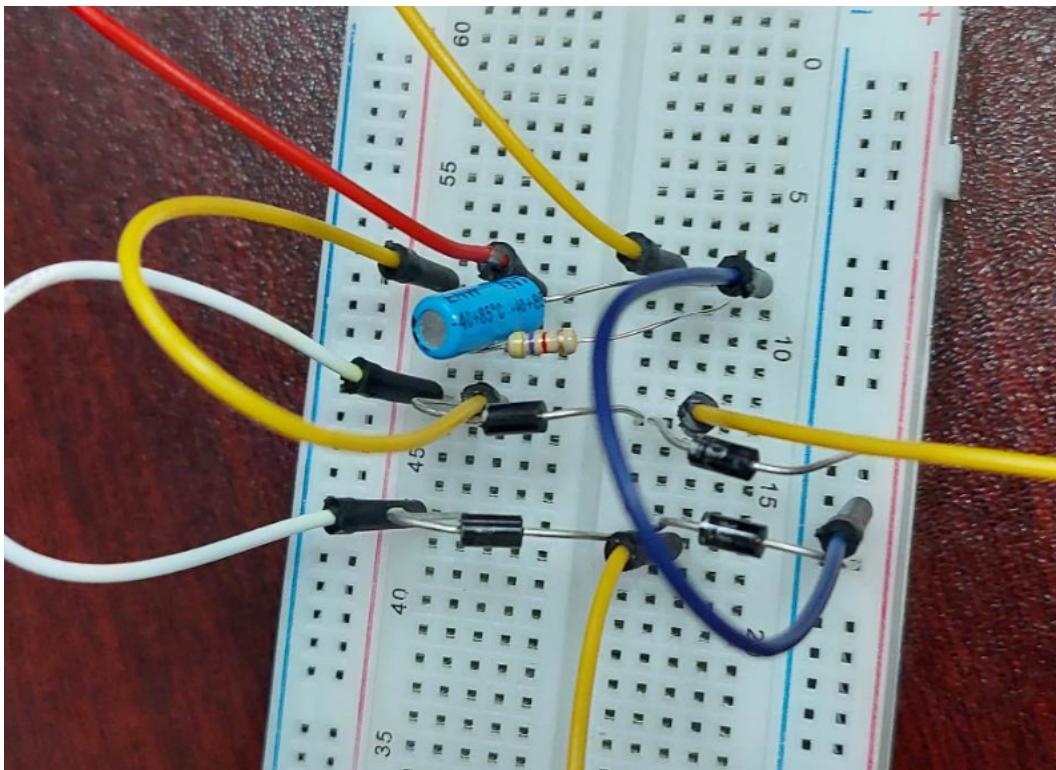
Circuit for Full-wave rectifier with 4.7uF capacitor :



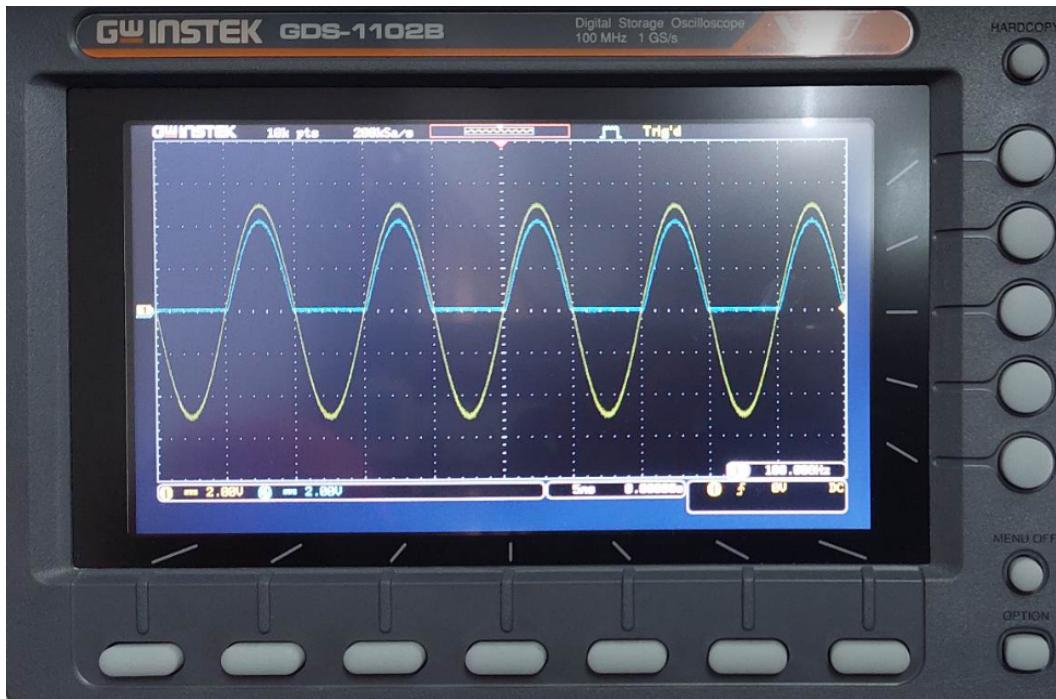
Input and output curves for Half-wave rectifier without capacitor :



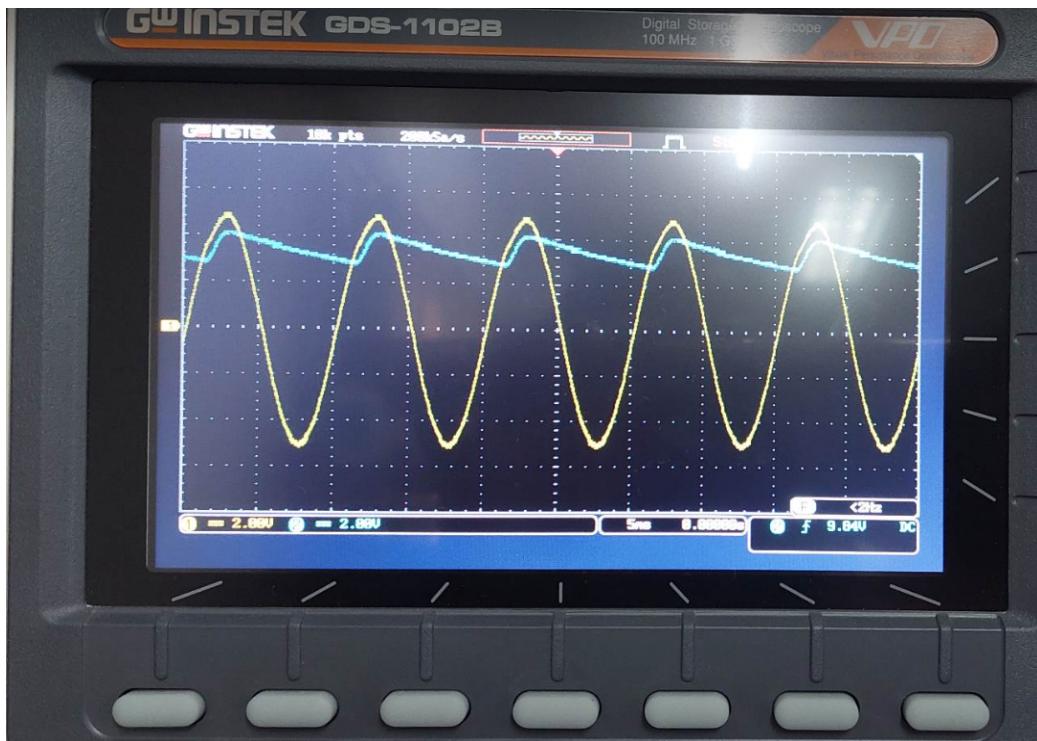
Input and output curves for Half-wave rectifier with 1uF capacitor :



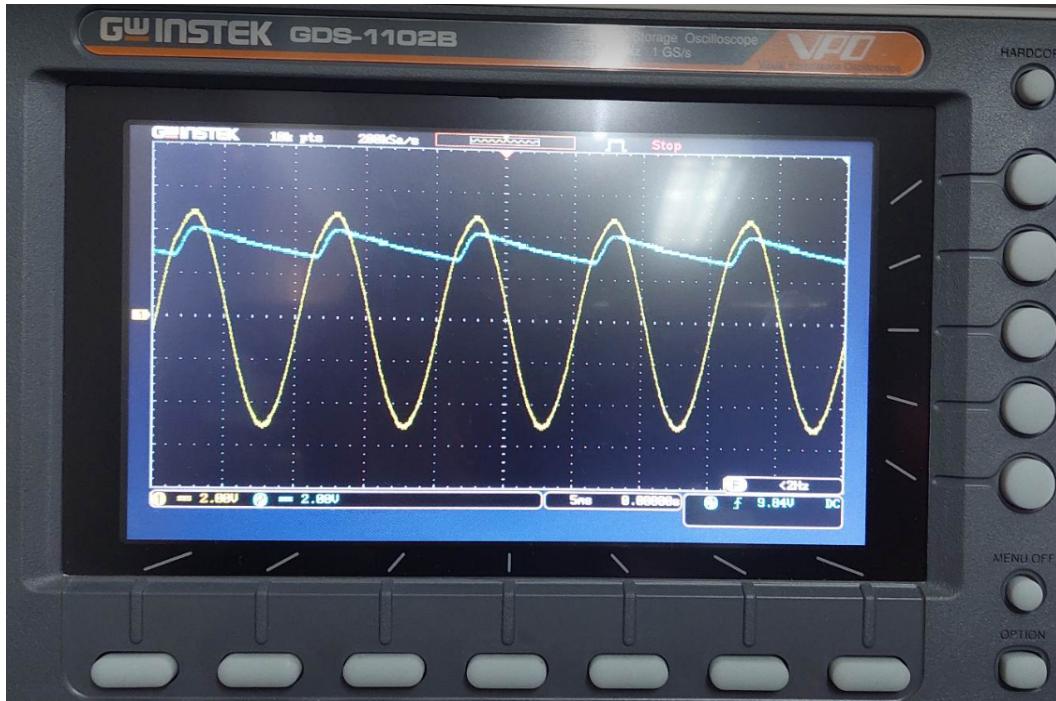
Input and output curves for Half-wave rectifier with 4.7uF capacitor :



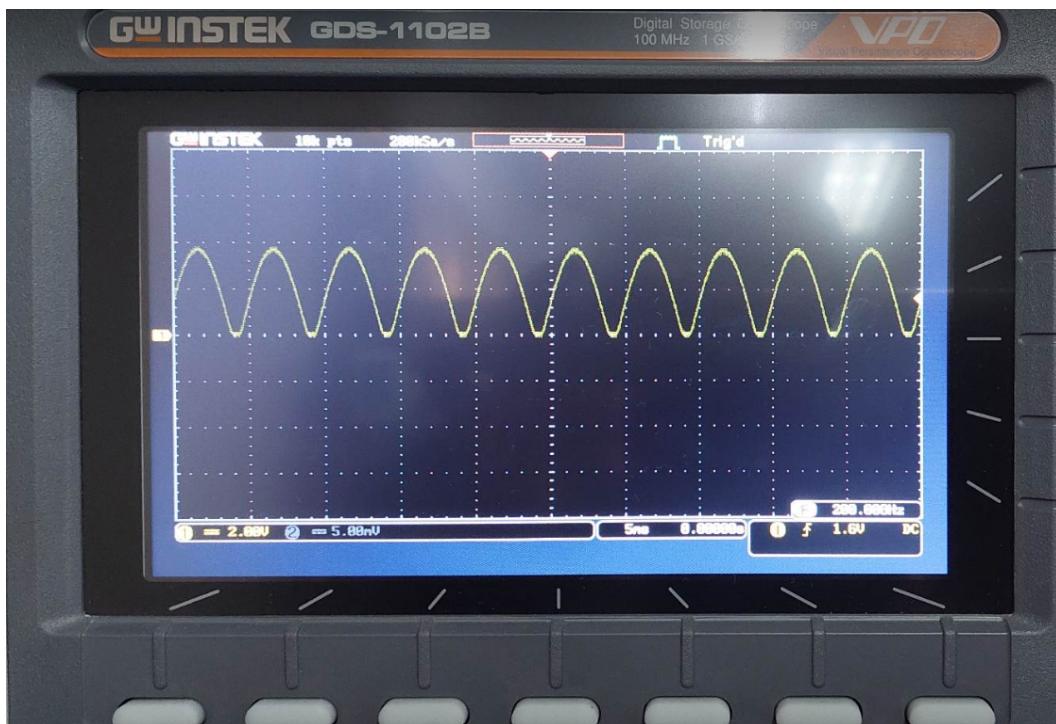
Output curve for Full-wave rectifier without capacitor :



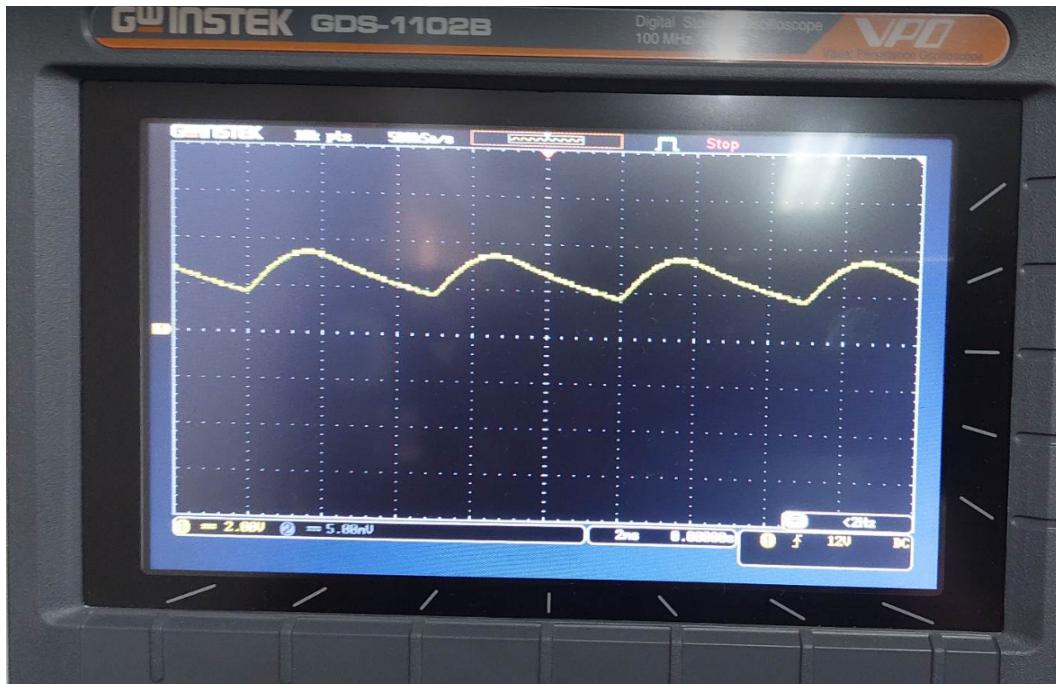Output curve for Full-wave rectifier with 1uF capacitor :



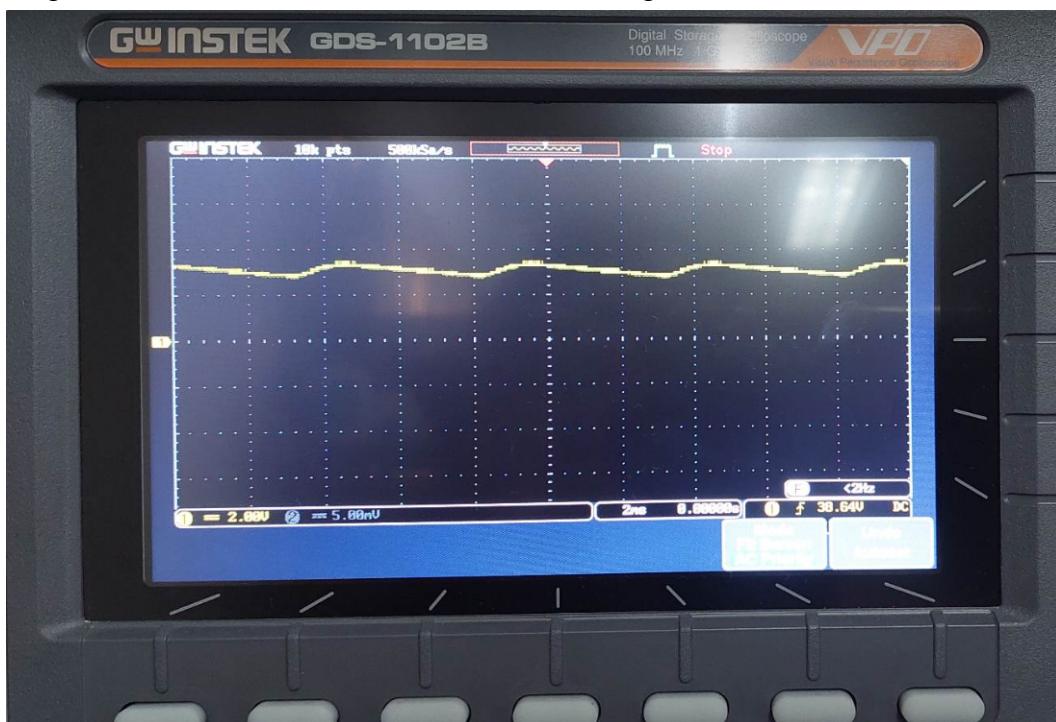Output curve for Full-wave rectifier with 4.7uF capacitor :



## DISCUSSION :

First of all, the half-wave rectifier is built using a  $100\text{k}\Omega$  resistor and diode connected in series with a function generator set at 5V and 100Hz connected to the channel 1 of the oscilloscope and channel 2 of the oscilloscope is connected to the resistor. Then, input and output curves are observed on the oscilloscope using the channel 1 and channel 2 respectively. Further,  $1\text{uF}$  and  $4.7\text{uF}$  are connected to the resistor parallelly one after another to observe the input and output curves to observe the smoothness of the curves caused by these capacitors.

Afterwards, a full-wave rectifier is built using two diodes connected in series and another two diodes connected in series. These are connected in parallel and the function generator is connected at the middle of both the series diodes. And, a  $100\text{k}\Omega$  resistor is connected in parallel to the diodes and channel 2 is connected to the resistor to observe the output curves. Again,  $1\text{uF}$  and  $4.7\text{uF}$  are connected to the resistors parallelly one after another to observe the output curve to observe the smoothness of the curves caused by these capacitors.

Through the observations, the curves are more smooth using a  $4.7\text{uF}$  capacitor for both half-wave and full-wave rectifiers.  $4.7\text{uF}$  capacitor discharges and charges at a faster rate than  $1\text{uF}$ , so the time taken to turn ON and OFF the diode becomes faster.

Among the half-wave and full-wave rectifiers, the full-wave rectifier is better because the diode does not turn OFF during the -ve half cycle, instead current flows through the circuit using the diodes which are in forward-bias during this process. As a result, there is an output voltage curve for both +ve and -ve half cycles producing a greater average output voltage and smaller ripple factor than the half-wave rectifier.

We cannot observe the input and output curves using only channel 2 because connecting both the inputs and outputs of the rectifiers to a single channel can be shorted the rectifier as the oscilloscope has ground referenced inputs.

The problem faced during the experiment was that the output curve of the full-wave rectifier contained noise. To eliminate the noise, a capacitor was connected to one of the wires connected to the resistor from where the channel 2 was connected.