



Theory
(76%)

- Attendance (10%)
- Assignment (10%) [n-1] (5%)
- Quiz (15%) [41] (5%)
- mid & final (20% + 20%)

Lab
(25%)

- Attendance (4%)
- Report (4%)
- Lab Test (7%)
- Project (10%)
[Water level indicator]


AND Gate

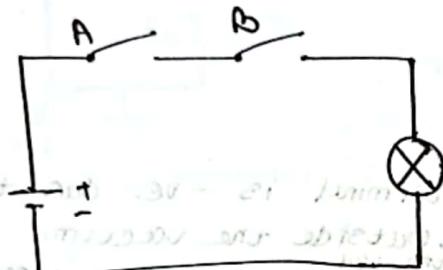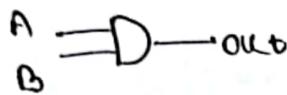

A	B	OUT
0	0	0
0	1	0
1	0	0
1	1	1

* If either A or B is open/off, there is no flow and thus there will be no outflow.

OR Gate

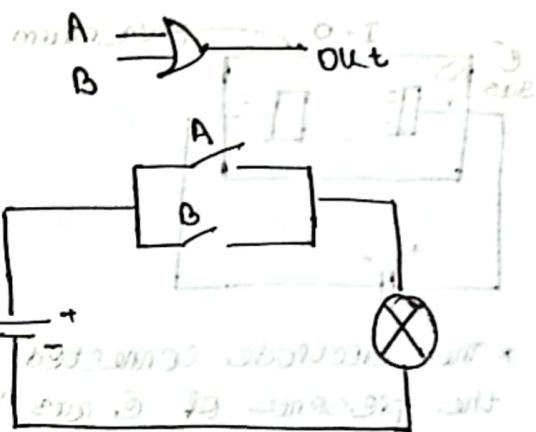


A	B	OUT
0	0	0
0	1	1
1	0	1
1	1	1

* If either A or B is open/off, there is still a flow along the path which is closed/on and thus there will be outflow.

CATHODE RAY

Ans 90

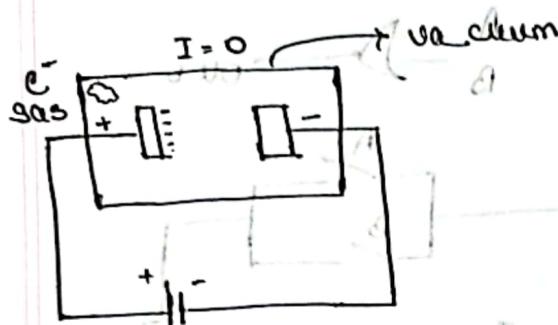


Ans 91



* The electrode connected to the +ve terminal is -ve due to the presence of \bar{e} gas in the vacuum. Outside the vacuum, the electrode is +ve. Thus, \bar{e} remains ^{attracted} in the electrode connected to +ve terminal. Thus, there is no flow of \bar{e} . $\therefore I = 0$

gas	0	0	0
0	0	0	0
0	1	0	0
0	0	0	1
1	1	1	1

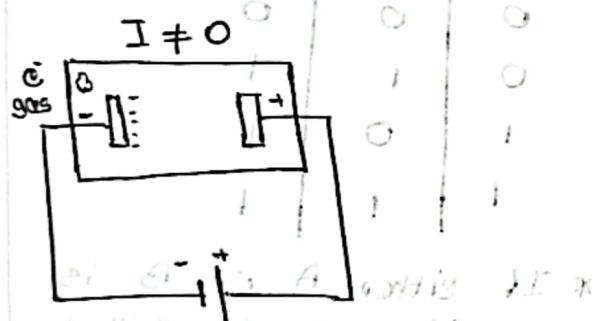

Q 92 A series of ESR
and ESR at 373K, 770K and
290K using the same
magnetic field and changing
the current no bias


Q 93 A series of ESR
and ESR at 373K, 770K and
290K using the same
magnetic field and changing
the current no bias

WEDNESDAY

DATE: 25/01/23

* ALTERNATE CIRCUIT REPRESENTATION


Ex-1

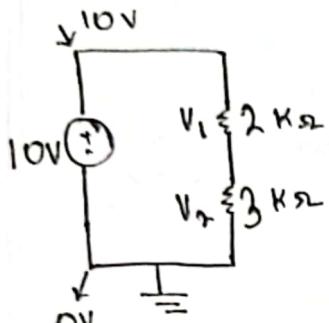

$$V_1 = \frac{r}{2+3} \times 10 = 4V$$

$$V_2 = 10 - 4 = 6V$$

Loop representation

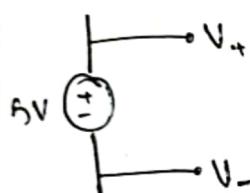


$$h = V_+ - V_-$$

$$\text{for ex-1, } 10 = V_+ - V_-$$

$$\Rightarrow 10 = V_+ - 0$$

$$\Rightarrow V_+ = 10V$$

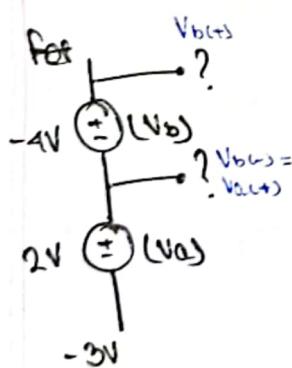

$$\text{Hence, } V_b = V_{b(+)} - V_{b(-)}$$


$$10 = V_{b(+)} - (-3)$$

$$\therefore V_{b(+)} = -1V = V_{b(-)}$$

$$\text{again, } V_b = V_{b(+)} - V_{b(-)}$$

$$-4 = V_{b(+)} - (-1)$$


$$\therefore V_{b(+)} = -3V$$

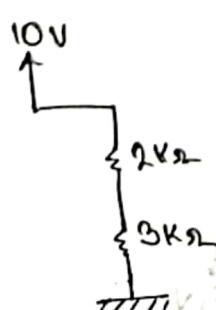


* 10V source is connected to ground. That's why we use an arrow to represent it.

* We represent ~~an~~ voltage source with arrows. If we use voltage source as the supply.

Ex-2

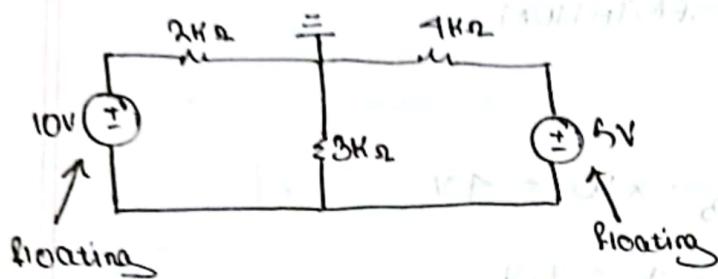


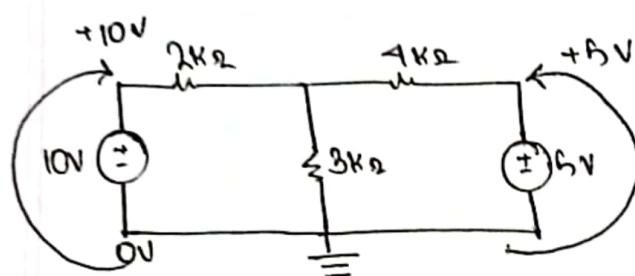- * Floating - the source does not have any reference point.
- * Both the supply must have same ground to avoid floating.




We have to design the circuit in such a way that the number of floating sources is minimized.

Alternate representation


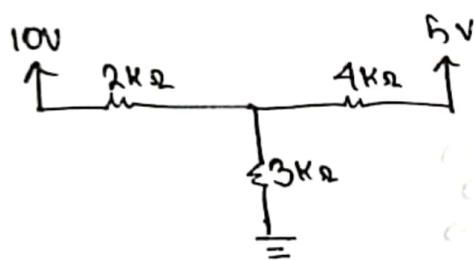


Ex-3


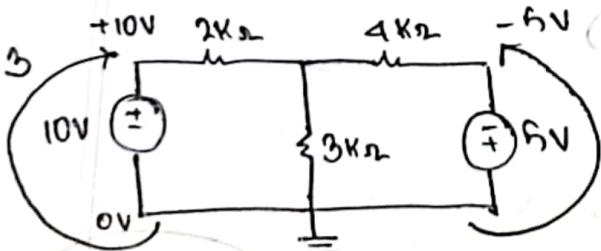


$$\begin{aligned} V_0 &= V_A - V_L \\ b &= 0 - V_L \\ \therefore V_L &= -bV \end{aligned}$$


Alternate representation

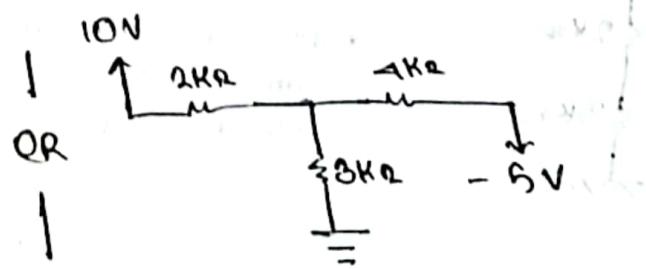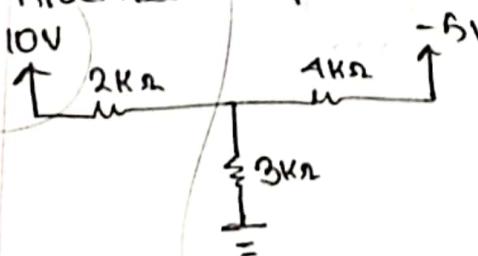

Ex-4

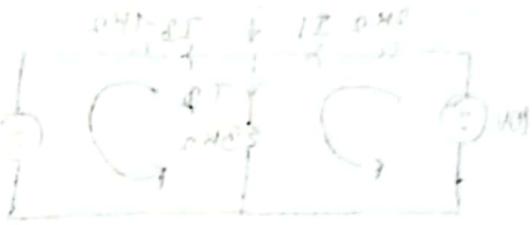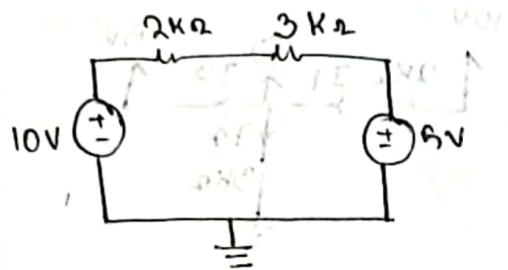

Alternate representation

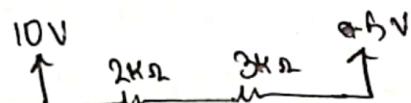


$0 = I \cdot 3k\Omega - 10 + 9V$

current I

current I


Ex-5

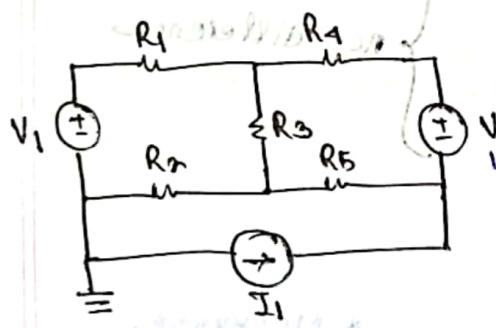

$0 = I \cdot 3k\Omega - 10 + 9V$


$0 = I \cdot 3k\Omega - 10 + 9V$

Alternate representation

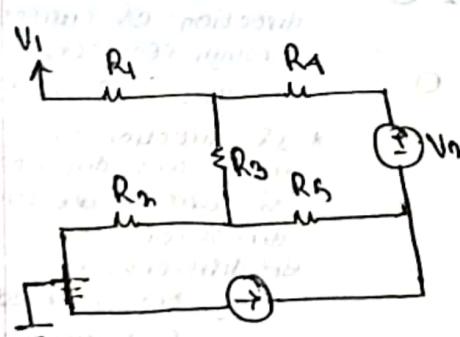

$0 = V_o - 9V$

$0 = V_o - 9V$


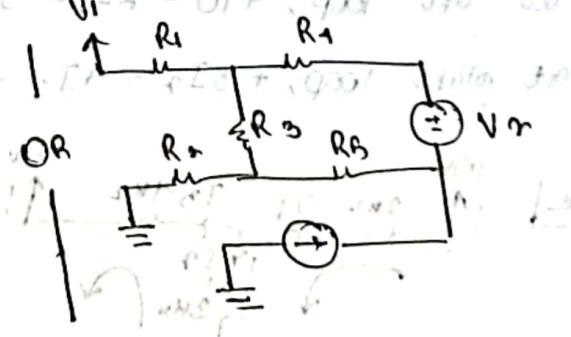


$0 = 0 = 10V - 9V = 1V$

$0 = 0 = 1V$

$0 = 0 = 1V - 9V = -8V$

$0 = 0 = 1V - 9V = -8V$

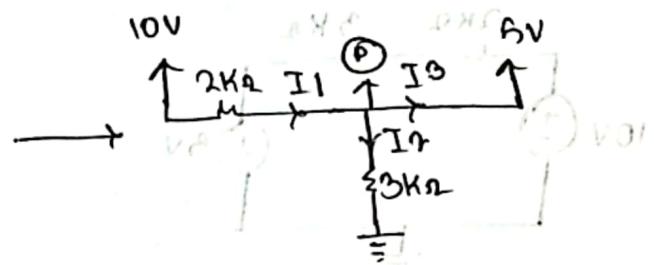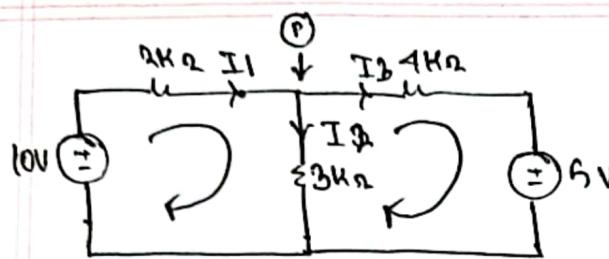

* KCL: At a node, $\sum I = 0$

Incoming
Incoming = Outgoing

Loop at p node, $I_1 = I_2 + I_3$

Alternative at p node, $I_1 = I_2 + I_3$


no difference

* KVL: At a closed loop, $\sum V = 0$

Loop at left loop, $+10 - 2I_1 - 3I_2 = 0$

at right loop, $+3I_2 - 4I_3 - 5 = 0$

Alternative

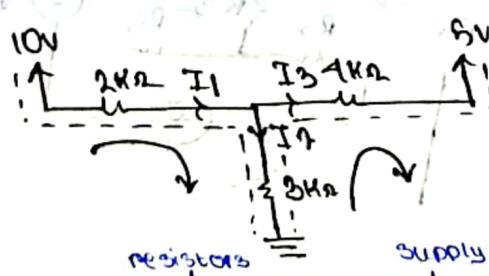

at left line, $-2I_1 - 3I_2 + V_{end} - V_{start} = 0 - 10$

OR

$2I_1 + 3I_2 = V_{start} - V_{end} = 10 - 0$

at right line, $3I_2 - 4I_3 + V_{end} - V_{start} = 5 - 0$

OR

$-3I_2 + 4I_3 = V_{start} - V_{end} = 0 - 5$

* Clockwise

* direction of route
is same as the direction of current through resistor.
a -ve sign is used.

* If direction of route and direction of current are through different resistors
are different, a +ve sign is used



* sign of destination is used for supply

~~3811000137407~~

known

* NODAL




61

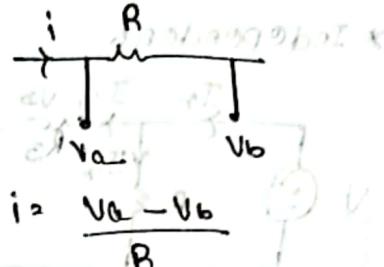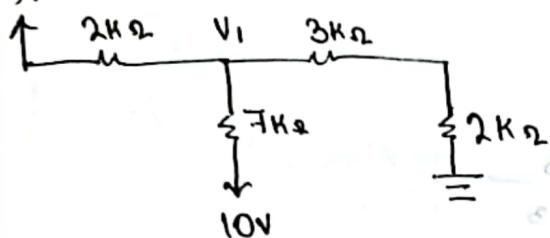

at v_1 node,

$$\frac{V_1 - 6}{2} + \frac{V_1 - 10}{4} + \frac{V_1 - 0}{3+2} = 0$$

— OR —

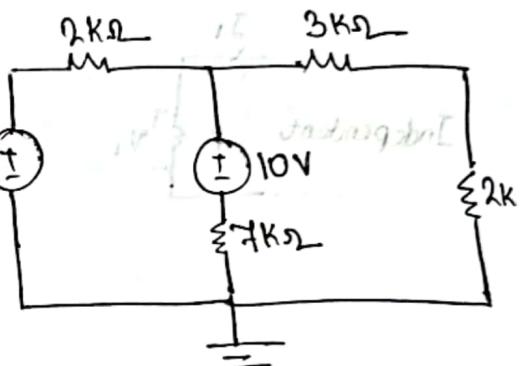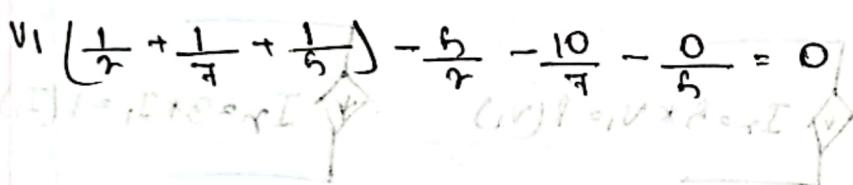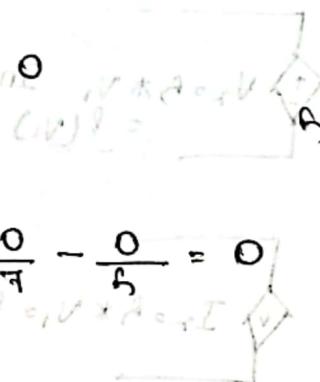

Loop representation

LECTURE


3

MONDAY


DATE: 30/01/23

* DEPENDENT & INDEPENDENT SOURCE

* Independent

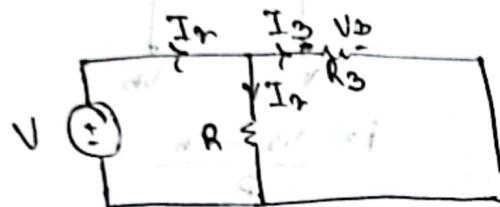

$$I_R = \frac{V_s}{R}$$

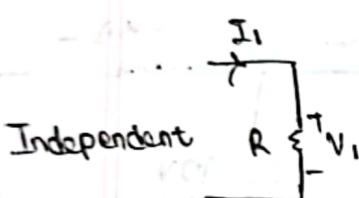


$$V_s = I_s \cdot R$$


$$I_s = \frac{V_s}{R}$$

$$I_s = B \cdot I_1 = f(I_1)$$

* Amplifiers

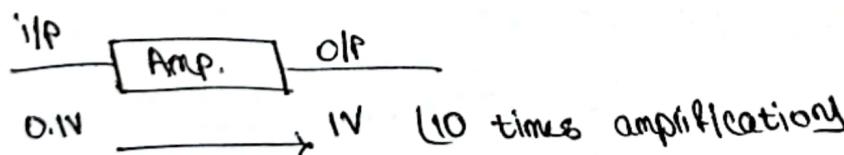

$$i/p \rightarrow o/p = k \cdot (i/p)$$

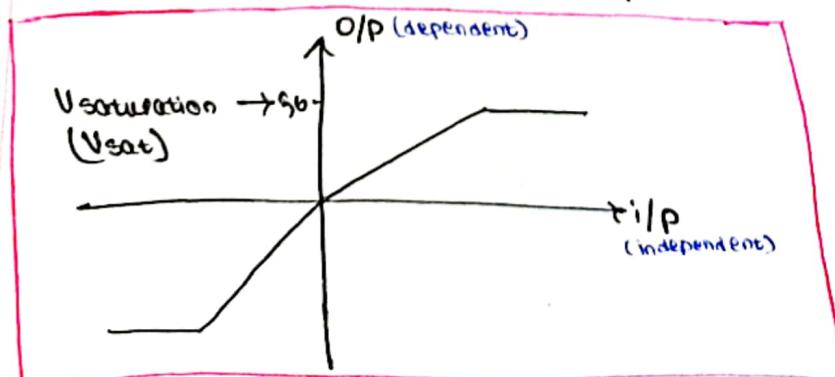


* Transfer characteristics

* Amplifiers does not have infinity power supply.


$$100V \rightarrow 10,000V$$

(may not be possible if the

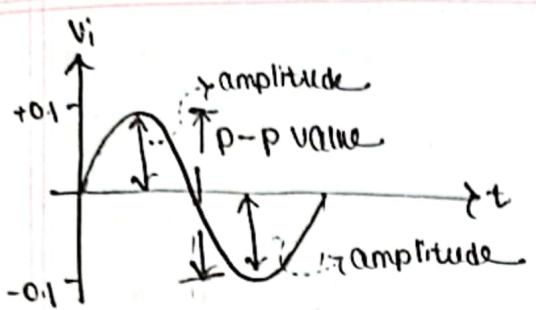amplifier does not permit due to the limitation)




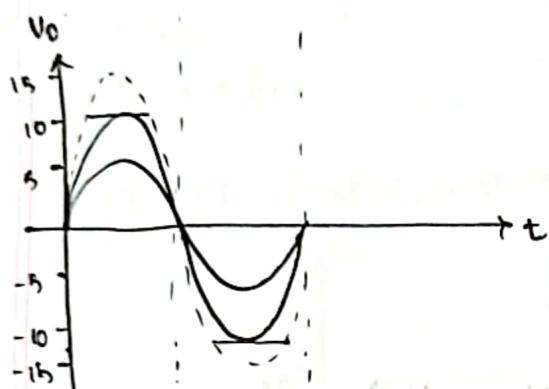amplitude $\Rightarrow 0.1V$ using this sin wave
 P-P value $\Rightarrow 0.2V$
 $V_i = 0.1 \sin \omega t$
 $\text{max}^2 = 1$
 $(V_i)_{\text{max}} = 0.1V$



$V_{\text{sat}} = 10V$
 ↓ amplitude

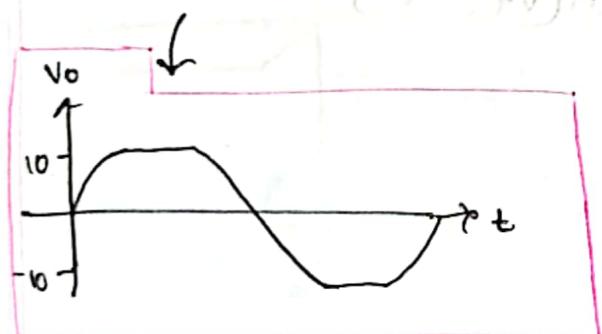* When OLP reaches V_{sat} , ^{for} any ILP
 which gives value $\Rightarrow V_{\text{sat}}$, the graph
 will be cut at the V_{sat} .




$$V_{\text{sat}} = \pm 10V$$

$$V_{\text{ILP}} = 0V$$

$$A_{\text{OLP}} = 1$$

$$S = 0.1$$

* OPERATIONAL AMPLIFIER (OP-AMP)

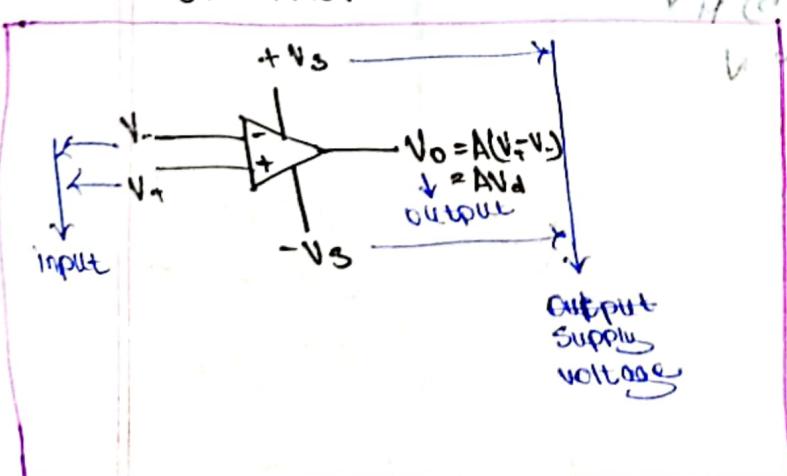

$V_{\text{sat}} = \pm 10V$
 $V_{\text{ILP}} = 0V$
 $A_{\text{OLP}} = 1$
 $S = 0.1$

* OLP cannot be greater than V_{sat} . V_{sat} is the $+V_s$ and $-V_s$ (supply voltage) ^{upper limit}
 ↓ lower limit

$$V_{\text{sat}} = \pm 10V$$

$$V_{\text{ILP}} = 0V$$

$$A_{\text{OLP}} = 1$$

$$S = 0.1$$


$$V_{\text{sat}} = \pm 10V$$

$$V_{\text{ILP}} = 0V$$

$$A_{\text{OLP}} = 1$$

$$S = 0.1$$

Equivalent circuit of op-amp:

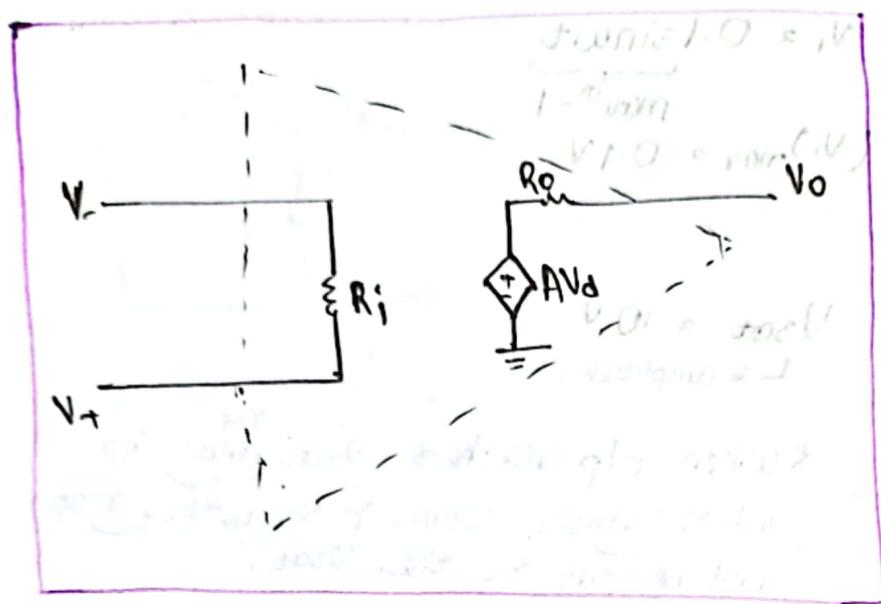

* Characteristics: $V_o = A V_d \Rightarrow V_o = A(V_+ - V_-)$

* Case 1: $V_+ = 1 \text{ mV}$

$$V_- = 0.5 \text{ mV}$$

$$A = 2 \times 10^5$$

$$V_o = ?$$

Case 1: $V_o = A(V_+ - V_-)$

$$= 2 \times 10^5 \times 0.5 \times (1 - 0.5) \text{ mV}$$

$$= 2 \times 10^5 \times 0.5 \times 10^{-6} \text{ V}$$

$$= 0.1 \text{ V}$$

* Case 2: $V_+ = 1 \text{ mV}$

$$V_- = 0.2 \text{ mV}$$

$$A = 2 \times 10^5$$

$$V_o = ?$$

$$V_o = A(V_+ - V_-)$$

$$= 2 \times 10^5 (1 - 0.2)$$

$$= 2 \times 10^5 \times 0.8 \times 10^{-6}$$

$$= 0.16 \text{ V}$$

in an op-amp,

$V_o, \text{max} = +V_3$



$V_o, \text{min} = -V_3$

if $+V_3 = 15V$,

$-V_3 = -15V$

$\therefore V_o = +15V$

* Transfer characteristics

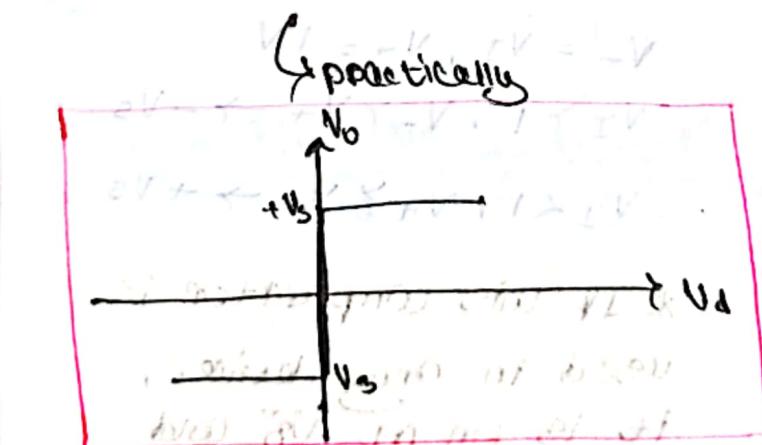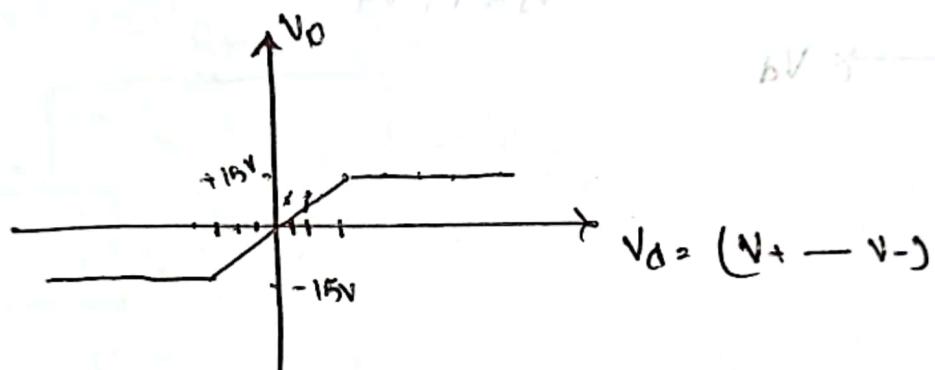

if $V_d > 0, V_o = +V_3$

$\nexists (V_+ - V_-) > 0$




$\therefore V_+ > V_-$

if $V_d < 0, V_o = -V_3$

$\nexists V_+ - V_- < 0$

$\therefore V_+ < V_-$

* Comparator

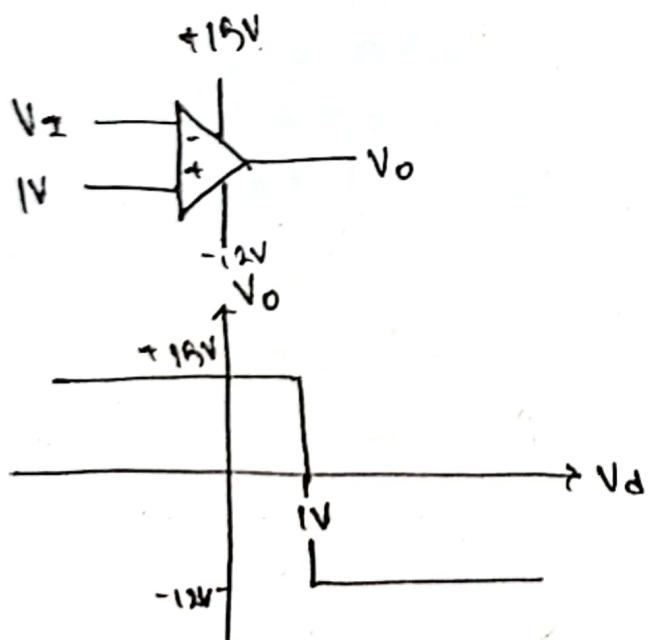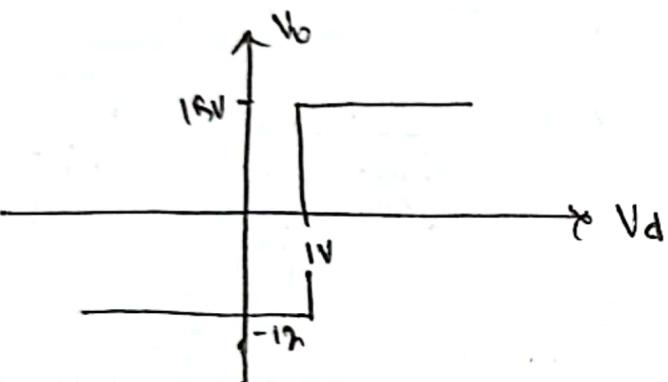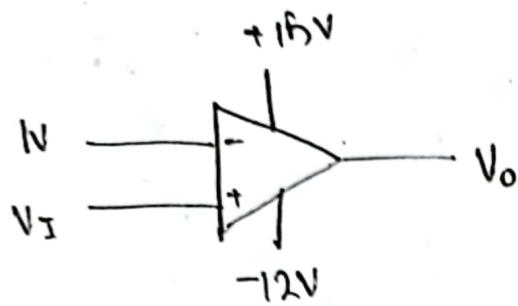

$$(-V - +Vs) = 0V$$

* If this comparator is used in any device, it is on at V_S^+ and off at V_S^- . [ON for higher voltage]

$$V_- = 0V, V_+ = V_I \text{ for } V_+ > V_S^+$$

$$V_I > 1, V_+ < V_- \rightarrow +V_S^*$$

$$V_I < 1, V_+ < V_- \rightarrow -V_S^-$$



$$V_- = V_I, V_+ = 1V$$

$$V_I > 1, V_- < V_+ \rightarrow -V_S^-$$

$$V_I < 1, V_+ > V_-, \rightarrow +V_S^*$$

* If this comparator is used in any device, it is on at V_S^- and off at V_S^+ . [ON for lower voltage]


$$V_- = 0V, V_+ > V_I \rightarrow +V_S^*$$

$$-V_S^+ < V_+$$

$$0V < V_+, V_+ > V_I \rightarrow +V_S^*$$

$$0V < V_+, V_+ < V_I \rightarrow -V_S^-$$
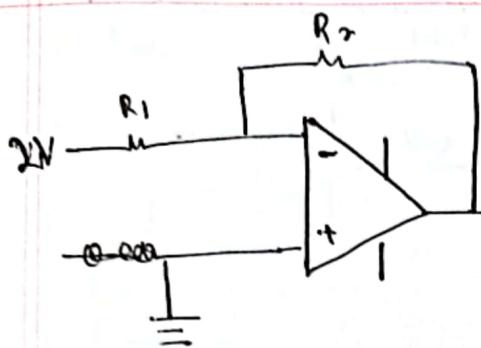
$$-V_S^+ < V_+, V_+ < V_I \rightarrow -V_S^-$$



$$R_i \approx 1 \text{ m} \approx$$

$R_0 = 0.1 \cdot K_{52}$

$$A = 2 \times 10^6 \text{ m}^2$$



$$0 = \frac{\partial U - W}{\partial t} + \frac{\partial U - W}{\partial q} + \frac{\partial U - W}{\partial R} \text{, where } W \text{ is 0}$$

$$\frac{V_1 - V_r}{R_1} + \frac{V_1 - V_m}{R_{mr}} + \frac{V_1 - 10}{R_2} = 0 + \frac{V_m - V_r}{R_2}$$



$$M_1 \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{1 \times 10^6} \right) = V_{R_2} \left(\frac{1}{R_2} \right) = \frac{I}{R_{\text{parallel}}} \quad \text{--- (1)}$$

$$\frac{V_n - V_1}{R_m} + \frac{V_n - V_{A1}}{R_o} = 0$$

$$-V_1 \left(\frac{1}{R_F} \right) + V_{IN} \left(\frac{1}{R_F} - \frac{AV_d}{R_{IN}} \right) = 0 \quad \text{ii.} \quad \boxed{V_{IN} = 0.925 \text{ V}} \quad \boxed{R_{IN} = 22.0 \text{ M\Omega}}$$

W. 89405 3A 08700-000, VL & PC, in zone, Part of
an area of 2000' on a north slope, 1000' above the 1000' E.

*

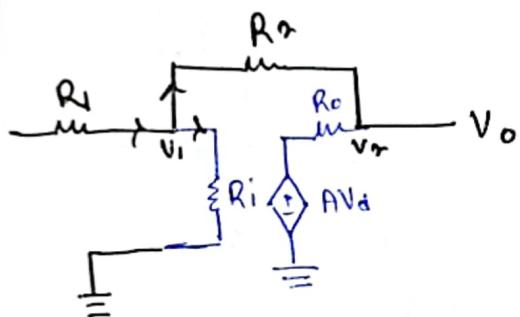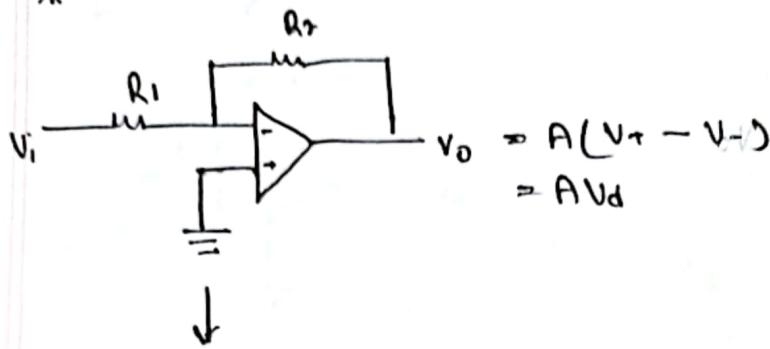


$$\text{At } V_1 \text{ node, } \frac{V_1 - V_{oi}}{R_1} + \frac{V_1 - 0}{R_D} + \frac{V_1 - V_R}{R_R} = 0$$

$$\text{At } V_2 \text{ node, } \frac{V_2 - V_{\text{ND}}}{R_0} + \frac{V_2 - V_1}{R_m} = 0$$

* Application

Automatic AC \uparrow air conditioning

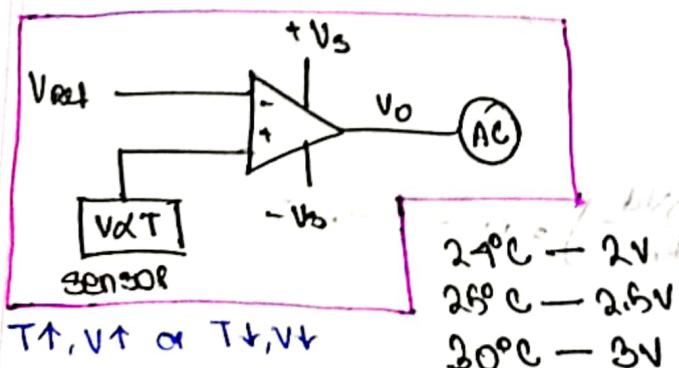


$$V_{ref} = 2.5 \text{ V}$$

If $V_d T$ gives $3V$, $3V \neq 2.5V$, $V_o = +ve$, so AC turns on.

If VdT gives 2N, 3N & 2N, NO₂ - ve, so AC turns off.

IP V_{d7} gives 2.6V, $2.6V = 2.6V$, No 2 O, 50 AC turns all

Smoke Detector

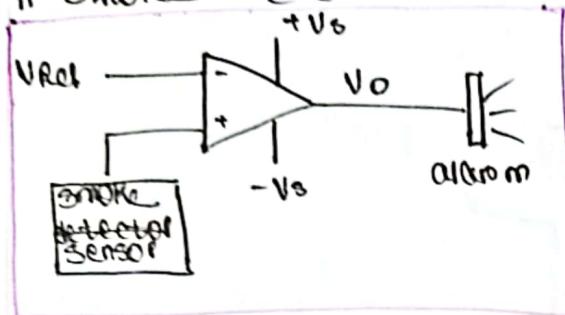


$$V_o = A(V_i - V_f) = 4 \cdot 1$$

$$AV = 6.7$$



$$V_f = 1$$

$$V_o = 4$$

smoke sensor:

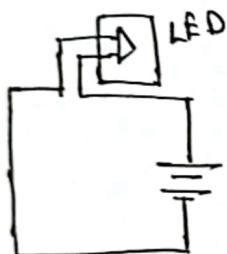

LDR (Light-dependent resistor)

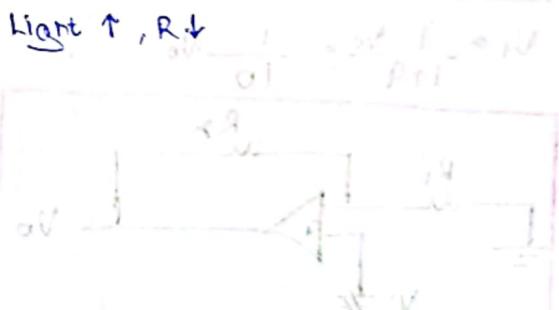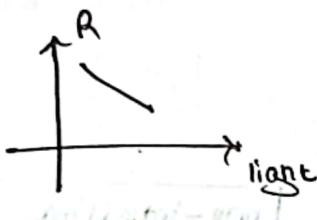


V_oR

no smoke: R_p small, V_oR small \rightarrow 1V

smoke: R_p large, V_oR large \rightarrow 3V

$$V_{ref} = 2.9V$$

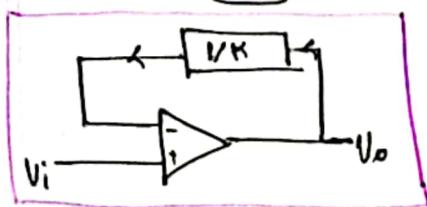* Introducing feedback: we get a controlled gain (A)



$$V_o = A(V_+ - V_-)$$

$$\text{Here, } V_+ = \frac{1}{K} V_o \quad (V_+ = V_i)$$

$$V_+ = V_i$$

$$V_o = A(V_i - \frac{1}{K} V_o)$$

$$\Rightarrow V_o = A V_i - \frac{A}{K} V_o$$

$$\Rightarrow V_o (1 + \frac{A}{K}) = A V_i \quad \text{if } A \rightarrow \text{extremely large}$$


$$\therefore V_o = -\frac{A}{A+K} V_i$$

if $K = 10$, $V_o = 1V$

$$V_o = KV_i$$

$$= 10 \times 1$$


$$= 10V$$

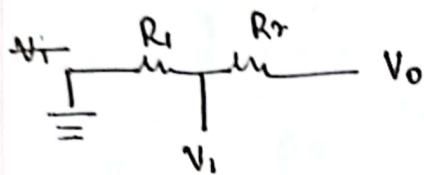

$$V_i = \frac{R_1}{R_1 + R_2} \times V_o$$

$$R_1 = 1 \text{ k}\Omega, R_2 = 9 \text{ k}\Omega$$
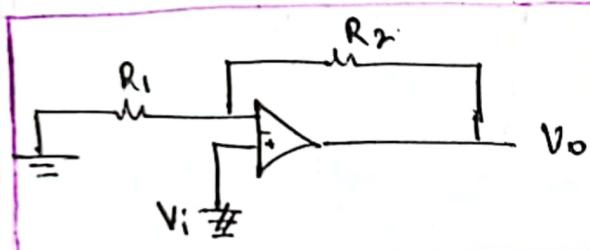
$$V_i = \frac{1}{1+9} V_o = \frac{1}{10} V_o$$



$$V_i = \frac{R_1}{R_1 + R_2} V_o$$

$$V_i = V_i$$

$$\rightarrow V_i = \frac{1}{10} V_o$$

$$V_i = V_i$$

$$\therefore V_o = KV_i = 10V_i$$

$$= (1+9)V_i$$

$$V_o = (1 + \frac{R_2}{R_1}) V_i$$




non-inverting amplifiers

* Characteristics of an ideal op-amp

i) $A \rightarrow \infty$

ii) $R_i \rightarrow \infty$

iii) $R_o \rightarrow 0$

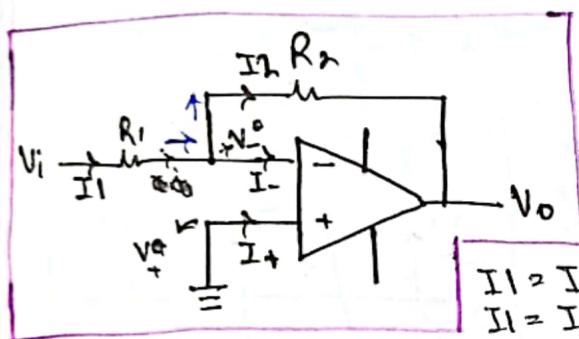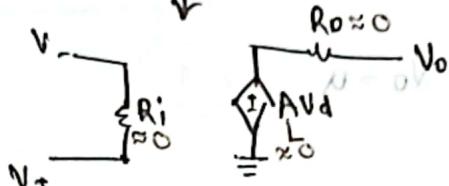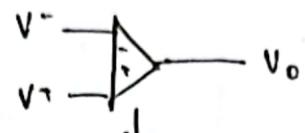

the inverting amplifier

$$I_1 = I_2 + I_- \\ I_1 = I_2 + 0$$

$$\text{Here, } I_- = \frac{V_-}{R} = \frac{0}{R} = 0$$

$$I_+ = \frac{V_+}{R} = \frac{0}{R} = 0$$

$$\# A(V_+ - V_-) = V_o$$

$$\Rightarrow V_+ - V_- = \frac{V_o}{A} = \frac{V_o}{\infty} = 0$$

$$\Rightarrow V_+ = V_-$$

Because there is a feedback.
[Virtual short circuit]

$$\text{Hence, } V_+ = V_-$$

$$V_+ = 0V = V_-$$

[Virtual ground]


$$I_1 = I_2$$

→ no current flows through -

$$\frac{V_i - V_-}{R_1} = \frac{V_- - V_o}{R_2}$$


$$V_o = \frac{-R_2}{R_1} V_i$$

inverting amplifier

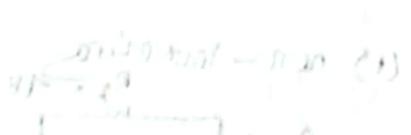

$$V_o = V_+ \cdot \infty$$
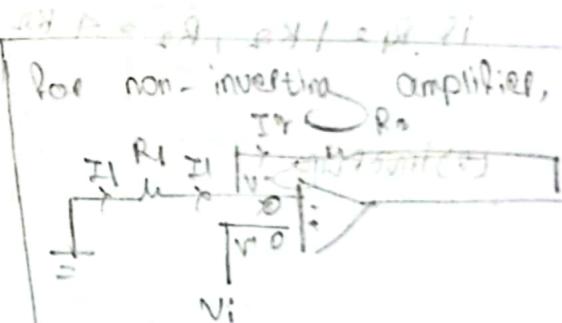
$$I_+ = \frac{V_+}{R_f} = \frac{V_o}{R_f}$$



$$\text{Here, } V_+ = V_-$$

$$V_+ = V_i = V_-$$

$$I_1 = I_2$$

$$0 = V_- \Rightarrow \frac{V_- - V_o}{R_2} = 0$$

$$\frac{V_o - V_i}{R_1} \Rightarrow \frac{V_i - V_o}{R_1}$$

$$\frac{V_o}{R_2} \Rightarrow \frac{V_i}{R_1} + \frac{V_i}{R_2}$$


$$V_o = R_2 \left[\frac{1}{R_1} + \frac{1}{R_2} \right] V_i$$

$$V_o = \left(1 + \frac{R_2}{R_1} \right) V_i$$

* CR: $u_2 = R_2 u$

$q_10 - q_2$ least w/ 2nd order

(1) non-inverting Amp:

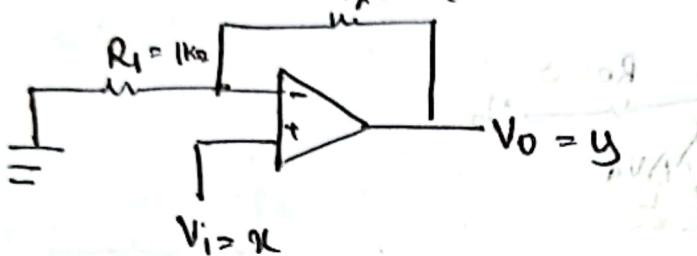

$-V_o = u$

$u = \frac{V_o}{4k\Omega}$

Here, $u = R_2 u$
 $\Rightarrow (1 + 4)u$

$$\frac{R_2}{R_1} = 4$$

If $R_1 = 1k\Omega$, $R_2 = 4k\Omega$

$$-1 + 4 = 3$$

$$3 \times 1 = 3$$

inverting

$$0 = \frac{u}{4k\Omega} + \frac{-V_o}{4k\Omega}$$

$$0 = \frac{u}{4} - \frac{V_o}{4}$$

$$0V = 6V -$$

$$\frac{u}{4} = \frac{0V}{4}$$

$$0 =$$

$$-V_o = 4V$$

for more info
visit


$-V_o = 4V$

more info $V_o = 4V$




MONDAY

DATE: 06/02/20

Example.

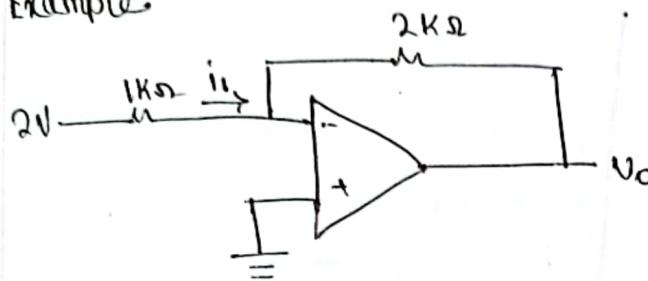
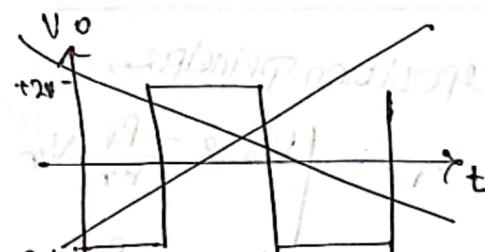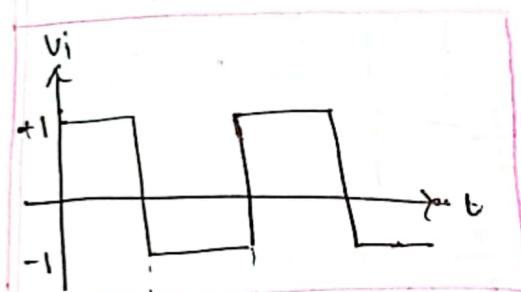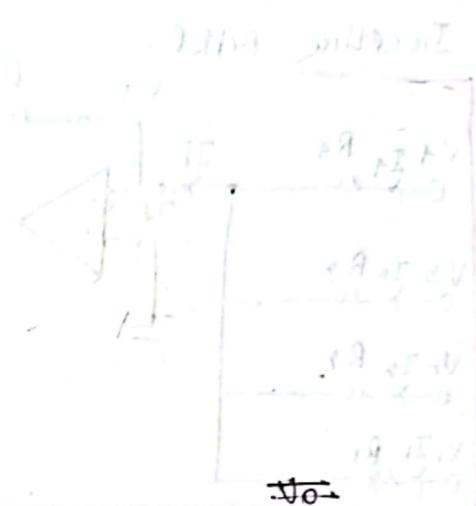
$$V_o = \frac{R_2}{R_1} V_i = \frac{2}{1} \times 2 = 4V$$




$$V_o = -\left(\frac{R_2}{R_1}\right)V_i$$

$$= -2V_i$$

if $V_i = +1V$, $V_o = -2V$

if $V_i = -1V$, $V_o = +2V$


Example

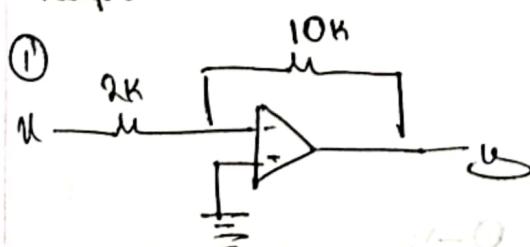

$$V_o = -\frac{10}{2} V_i$$

$$V_o = -5V_i$$

$$② V_o = 0.5V_i$$

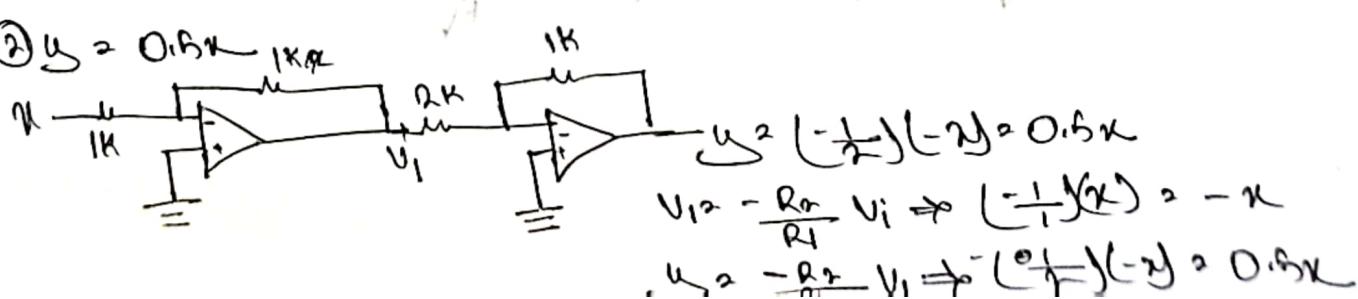


$$V_o = \left(-\frac{1}{2}\right)(-2) = 0.5V_i$$

$$V_{12} = \frac{R_2}{R_1} V_i \Rightarrow \left(-\frac{1}{2}V_i\right) = -V_i$$

$$V_o = -\frac{R_2}{R_1} V_i \Rightarrow \left(-\frac{1}{2}V_i\right)(-2) = 0.5V_i$$

Inverting Adder

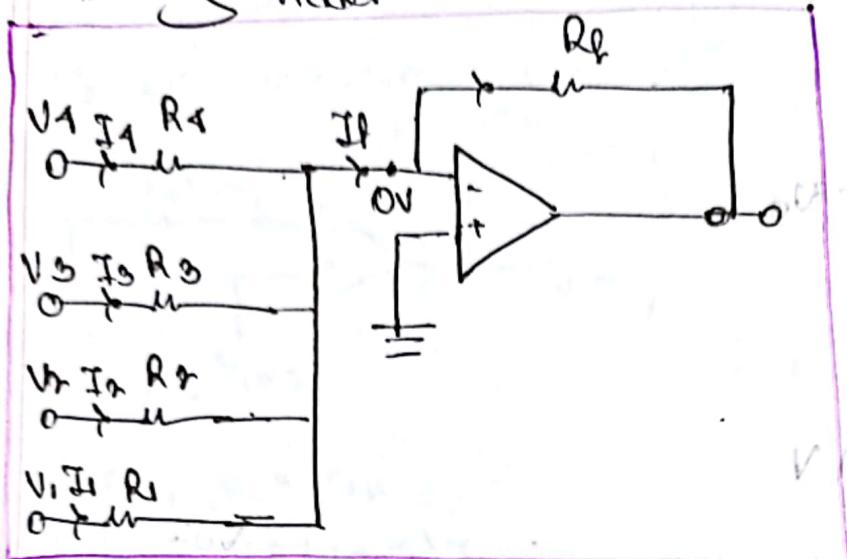

Using superposition principle,

$$V_{O4} = -\frac{R_f}{R_4} V_4$$

$$V_{O3} = -\frac{R_f}{R_3} V_3$$

$$V_{O2} = -\frac{R_f}{R_2} V_2$$

$$V_{O1} = -\frac{R_f}{R_1} V_1$$

$$V_0 = V_{O1} + V_{O2} + V_{O3} + V_{O4}$$

$$= -\frac{R_f}{R_1} V_1 - \frac{R_f}{R_2} V_2 - \frac{R_f}{R_3} V_3 - \frac{R_f}{R_4} V_4$$

$$V_0 = -\left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 + \frac{R_f}{R_4} V_4 \right)$$

OR,


$$I_1 + I_2 + I_3 + I_4 = I_f$$

$$\frac{V_1 - 0}{R_1} + \frac{V_2 - 0}{R_2} + \frac{V_3 - 0}{R_3} + \frac{V_4 - 0}{R_4} = \frac{0 - V_0}{R_f}$$

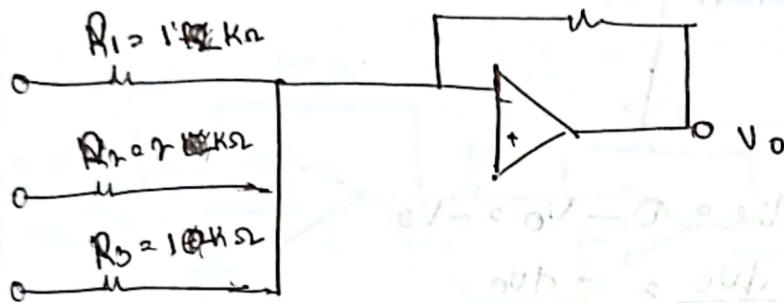Example

Implement the following function using op-amps:

$$V_O = -(V_1 + 0.5V_2 + V_3) \quad R_f = 1\text{ k}\Omega$$



$$V_O = -\frac{R_f}{R_3} V_3 \approx -\frac{1}{1} V_3$$

$$\frac{V_O}{V_3} = -\frac{1}{1}$$


$$V_O = -\frac{R_f}{R_2} V_2 \approx -\frac{1}{2} V_2$$

$$\frac{V_O}{V_2} = -\frac{1}{2}$$

$$V_O = -\frac{R_f}{R_1} V_1 \approx -\frac{1}{1} V_1$$

$$\frac{V_O}{V_1} = -\frac{1}{1}$$

Op-Amp as differentiator

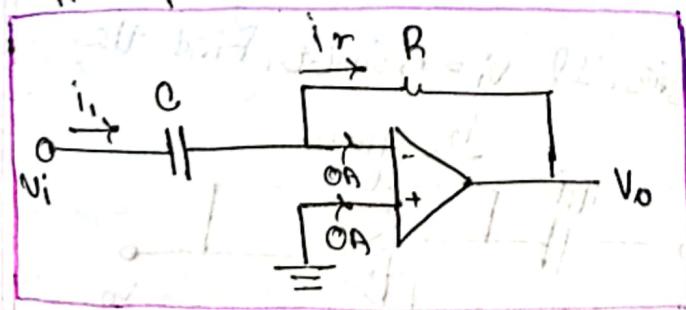


$$i_1 = i_{in}$$

$$\Rightarrow C \frac{dV_C}{dt} = -\frac{V_O - V_1}{R}, \quad V_C = V_1 - V_O$$


$$\Rightarrow C \frac{dV_1}{dt} = -\frac{V_O}{R}$$
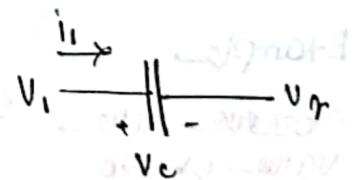
$$\Rightarrow V_O = -RC \frac{dV_1}{dt}$$



$$V_C = V_1 - V_O$$
$$i_1 = C \frac{dV_C}{dt} = C \frac{d}{dt} (V_1 - V_O)$$
$$i_1 = C \frac{dV_1}{dt} - C \frac{dV_O}{dt}$$

Op Amp as Integrator

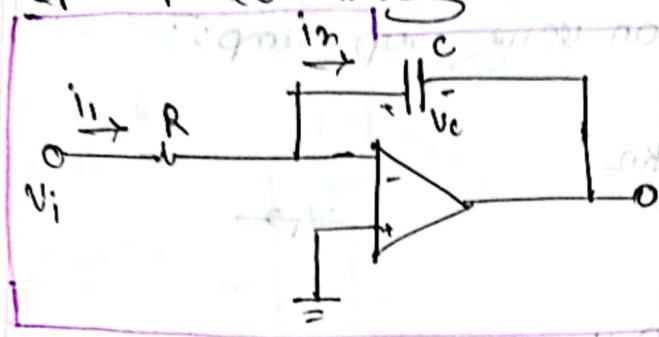

$$\Rightarrow \frac{Vi - 0}{R} = C \frac{dVc}{dt}, \quad Vc = 0 - V_o = -V_o \Rightarrow \frac{dVc}{dt} = -\frac{dV_o}{dt}$$

$$\Rightarrow \frac{Vi}{R} = -C \frac{dV_o}{dt}$$

$$\Rightarrow \frac{dV_o}{dt} = -\frac{Vi}{RC}$$

$$\Rightarrow V_o = -\frac{1}{RC} \int Vi dt$$

Example

Observe the following

figure. If $Vi = 5 \sin \omega t$, find the


Differentiator :-

$$V_o = (10^6 \times 10^3) \frac{d}{dt} (5 \sin \omega t)$$


$$V_o = (1) \frac{d}{dt} (5 \sin \omega t)$$

$$\therefore V_o = -5 \omega \cos \omega t$$

$$\therefore V_o = -30 \cos \omega t$$

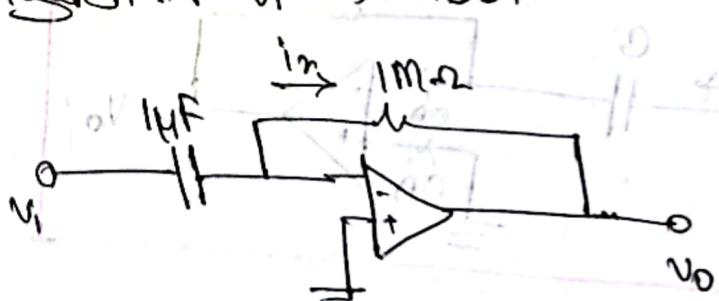

$$V_o = -RC \frac{dVc}{dt}$$

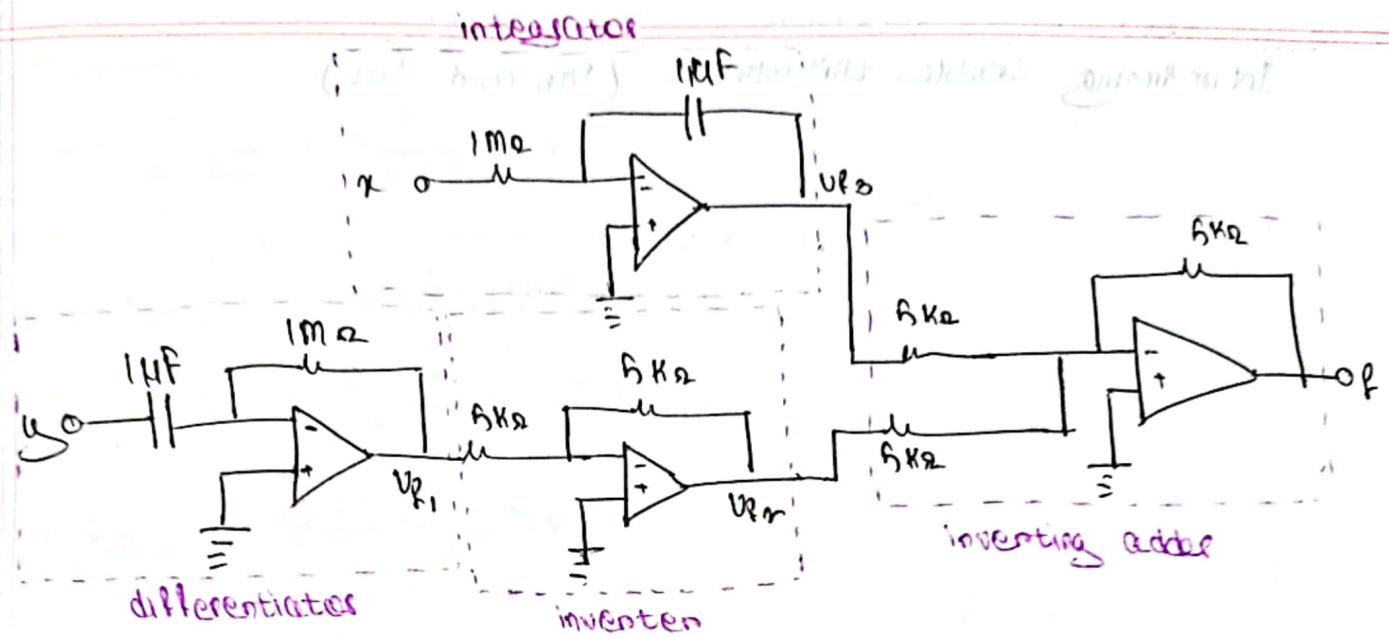

Differentiator top:

$$Vf_1^2 = (10^3 \times 10^6) \frac{d}{dt} (u)$$

$$Vf_1^2 = \frac{d}{dt} (u)$$

Integrator

$$Vf_3^2 = \frac{1}{10^6 \times 10^3} \int u \frac{dt}{dt} dt$$

$$Vf_3^2 = \int u \frac{dt}{dt} dt$$

~~$$Vf_3 = (5 \times 10^3 \times 5 \times 10^3)$$~~


Inverting Amplifiers

$$Vf_2^2 = \left(\frac{5 \times 10^3}{5 \times 10^3} \right) Vf_1$$


$$Vf_2^2 = Vf_1^2 = \frac{du}{dt}$$

$$Vf^2 = \left(\frac{5 \times 10^3}{5 \times 10^3} Vf_3 + \frac{5 \times 10^3}{5 \times 10^3} Vf_2 \right)$$
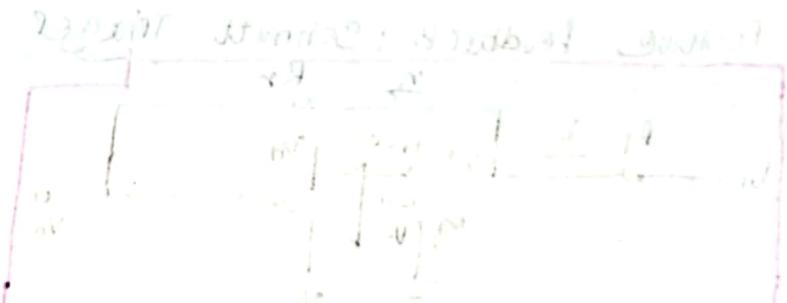
$$Vf^2 = \left(- \int u \frac{dt}{dt} dt + Vf_2 \right) - \frac{du}{dt}$$



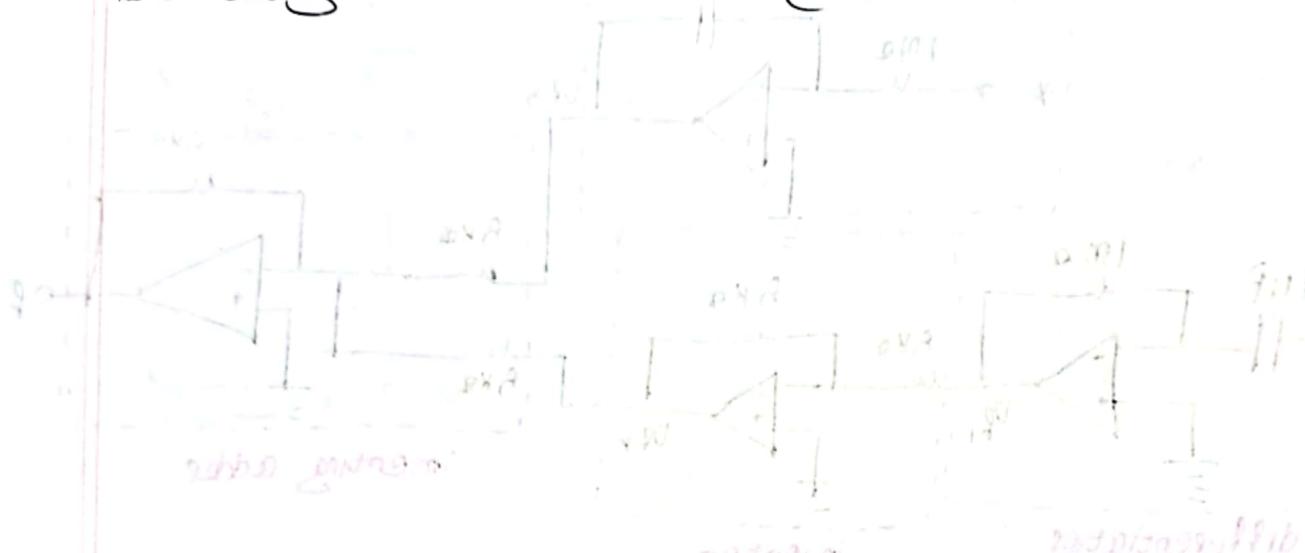Introducing double thresholds (V_{th} and V_{th})




$$(\omega)_{fb}^b (\omega)_{fb}^a = e^{i\omega t} - \text{nonlinear}$$

$$(\omega)_{fb}^b = e^{i\omega t}$$

$$s_b + s_a \left(\frac{1 - e^{i\omega t}}{\omega} \right) = e^{i\omega t} \text{ non-linear}$$

Positive feedback: Schmitt Trigger

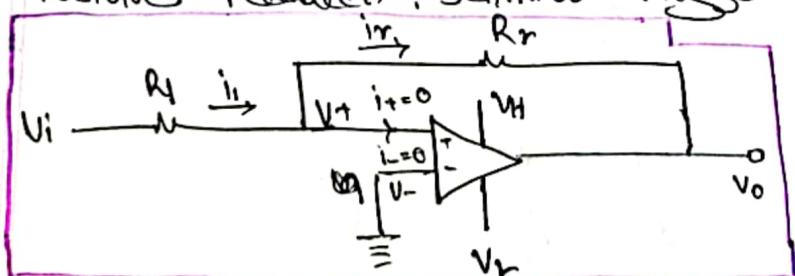

$$i_1 = i_2$$

$$\Rightarrow \frac{V_i - V_+}{R_1} = \frac{V_+ - V_0}{R_r}$$

$$\Rightarrow \frac{V_i}{R_1} - \frac{V_+}{R_1} = \frac{V_1}{R_r} - \frac{V_0}{R_r}$$

$$\Rightarrow \frac{V_i + V_0}{R_1} = V_1 \left(\frac{1}{R_1} + \frac{1}{R_r} \right)$$

* The feedback from V_0 goes to the input side \rightarrow (+) feedback

$$= V_+ \left(\frac{R_1 + R_r}{R_1 R_r} \right)$$

$$V_+ = \frac{R_1 R_r}{R_1 + R_r} \left[\frac{V_i}{R_1} + \frac{V_0}{R_r} \right]$$

$$= \frac{R_r}{R_1 + R_r} V_i + \frac{R_1}{R_1 + R_r} V_0$$

Assume initially $V_0 = V_r$

$$V_+ = \frac{R_r}{R_1+R_r} V_i + \frac{R_1}{R_1+R_r} V_r$$

if we want to have $V_0 = V_H$,

then $V_+ \neq V_- \Rightarrow V_+ \neq V_0$

$$\Rightarrow \frac{R_r}{R_1+R_r} V_i + \frac{R_1}{R_1+R_r} V_r \neq 0$$

$$\Rightarrow \frac{R_r}{R_1+R_r} V_i \neq -\frac{R_1}{R_1+R_r} V_r$$

$$\Rightarrow V_i \neq -\frac{R_1}{R_r} V_r \rightarrow \text{upper threshold } (V_{TH})$$

if we want to have $V_0 = V_L$,

then $V_+ \neq V_- \Rightarrow V_+ \neq V_0$

Assuming $V_0 = V_H$


$$V_+ = \frac{R_r}{R_1+R_r} V_i + \frac{R_1}{R_1+R_r} V_H$$

$$\Rightarrow \frac{R_r}{R_1+R_r} V_i + \frac{R_1}{R_1+R_r} V_H \neq 0$$

$$\Rightarrow \frac{R_r}{R_1+R_r} V_i \neq -\frac{R_1}{R_1+R_r} V_H$$


$$\Rightarrow V_i \neq -\frac{R_1}{R_r} V_H \rightarrow \text{lower threshold } (V_{TL})$$

Schmitt Trigger

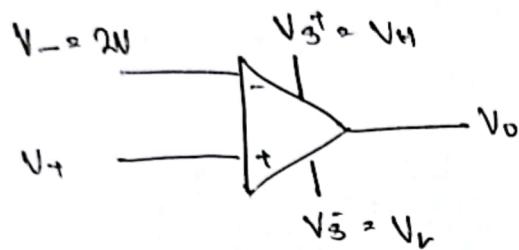

$$V_+ > V_-, V_0 = V_H$$

$$V_+ < V_-, V_0 = V_L$$

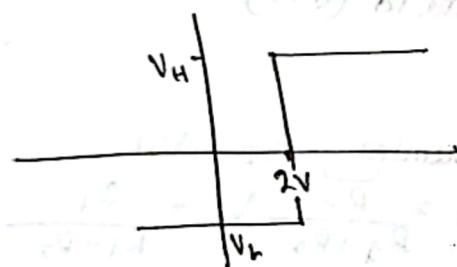


In Schmitt trigger, due to introduction of feedback with V_f , we are getting two thresholds.

* If V_{in} is greater than V_{TH} and V_f is not less than V_{TH} , then V_0 will be V_H . When V_{in} crosses V_{TH} , then V_0 will be V_L . [For high to low]

* If V_{in} is less than V_{TH} and

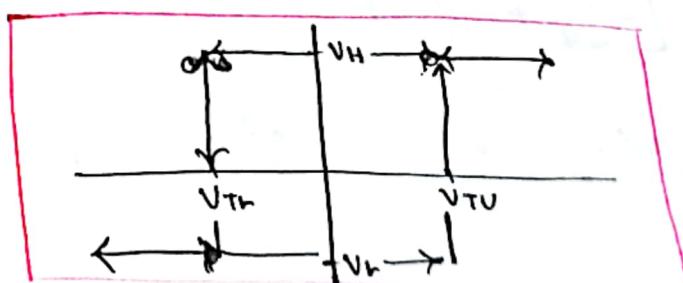
* If V_{in} is less than V_{TH} and is not greater than V_{TH} , then V_0 will be V_L . When V_{in} crosses V_{TH} , then V_0 will be V_H . [For low to high]





* By changing V_+ from 0 to a value, we can tune the threshold voltage.

$$V_i > -\frac{R_1}{R_2} V_L + V_{ref} \frac{R_1 + R_2}{R_2} \quad \leftarrow \text{upper threshold } (V_{TH})$$
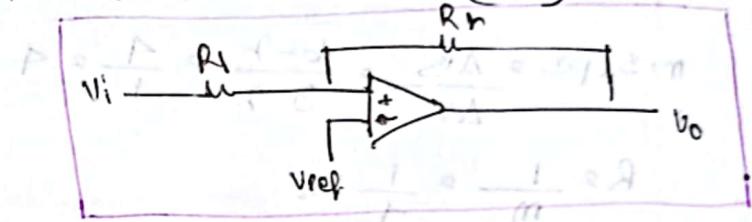
$$V_i < -\frac{R_1}{R_2} V_H + V_{ref} \frac{R_1 + R_2}{R_2} \quad \leftarrow \text{lower threshold } (V_{TH})$$



* I-V Characteristics:

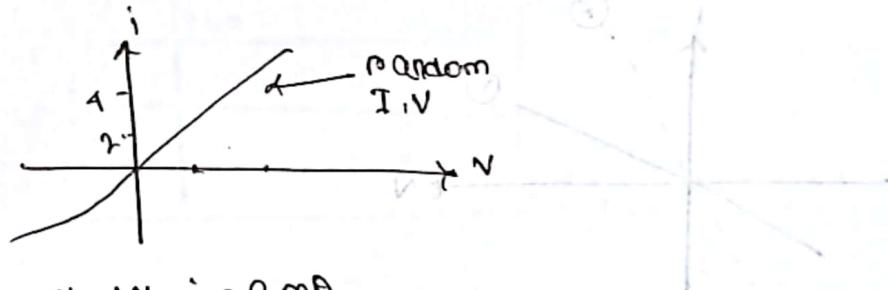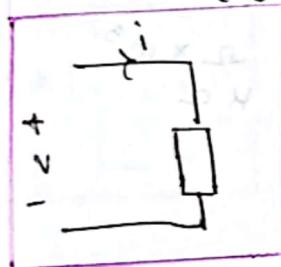


$$V = 1V, i = 2mA$$

$$V = 2V, i = 4mA$$


$$V = \dots, i = \dots$$

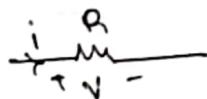* Some linear devices
Simple linear device
Resistor




Ohm's law
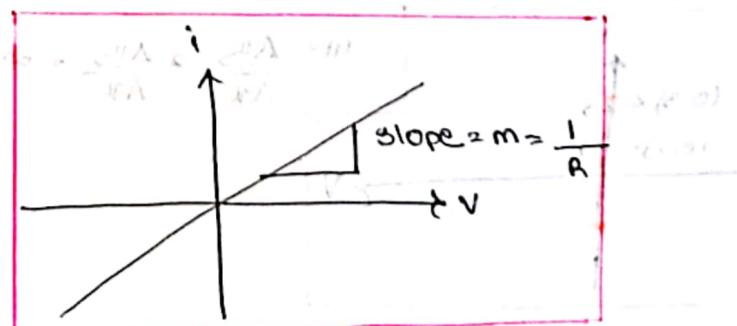
$$\begin{cases} i = \frac{V}{R} \\ V = iR \end{cases}$$



1. When $V = 0$, $i = 0$

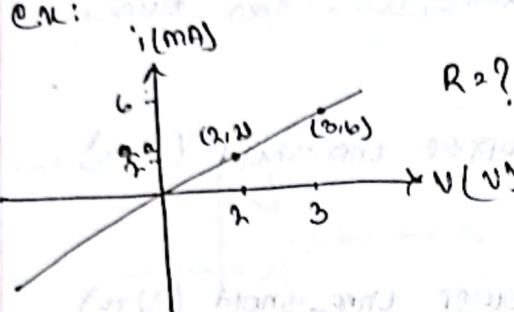

$$m = \text{slope} = \frac{\Delta V}{\Delta I} = \frac{b - 0}{3 - 2} = \frac{1}{1} = 1$$


$$R = \frac{1}{m} = \frac{1}{1} \Omega$$

$$R = \frac{V}{I} = \frac{V}{mA} = \frac{V}{A \times 10^3}$$

$$= \frac{V}{A} \times 10^3$$

$$= 1 \times 10^3$$

$$= 1 \Omega$$

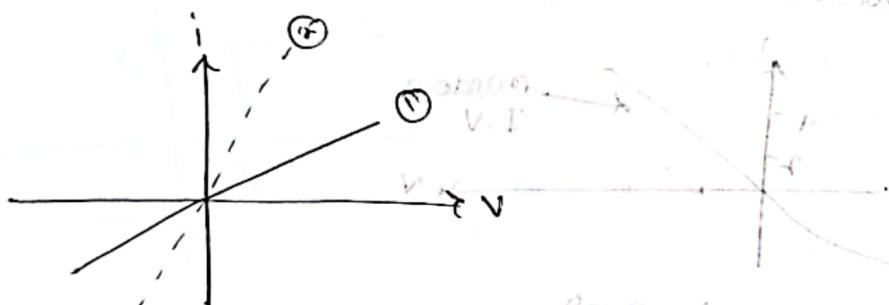


Slope of 2 \neq slope of 1

$$m_2 \neq m_1$$

$$\neq \frac{1}{R_2} \neq \frac{1}{R_1}$$

$$\neq R_1 \neq R_2$$


Short circuit (SC)

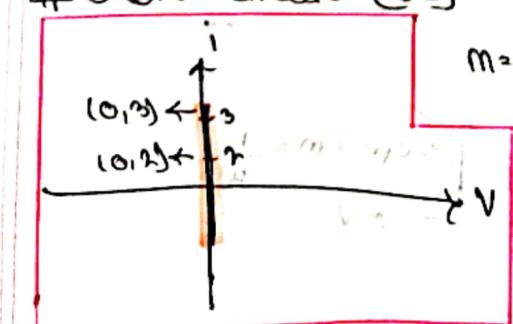

$$m = \frac{\Delta V}{\Delta I} = \frac{0 - 0}{2 - 0} = \infty, R = \frac{1}{m} = \frac{1}{\infty} = 0$$


A --- B
A - B shorted

Open circuit


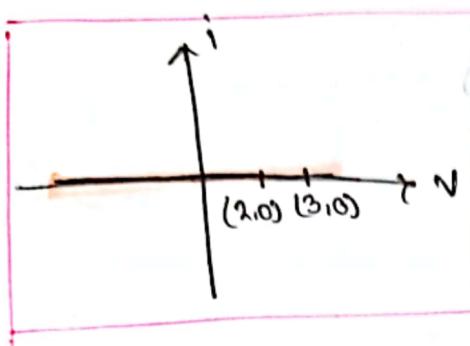


$$m = \frac{\Delta V}{\Delta x} \rightarrow \frac{0-0}{3-2} = 0$$


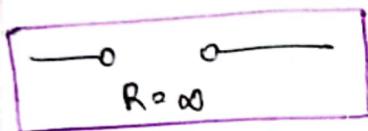
$$R = \frac{1}{m} \rightarrow \frac{1}{0} = \infty$$



Current source:

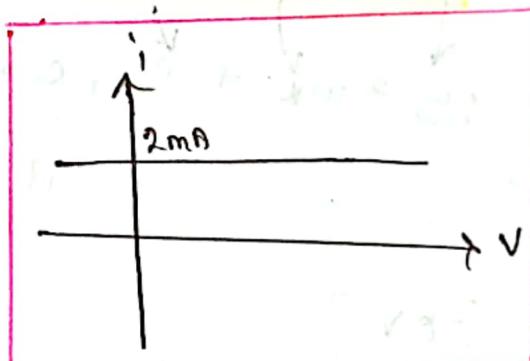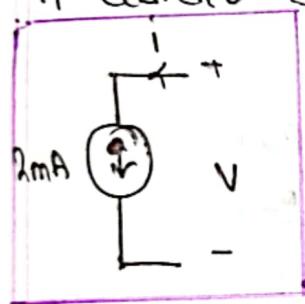


Voltage source

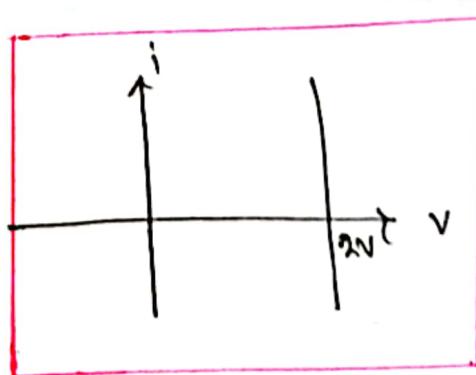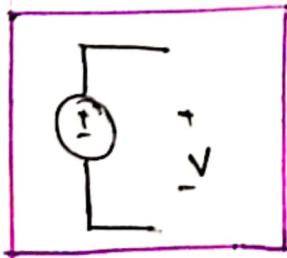

Compound linear device:

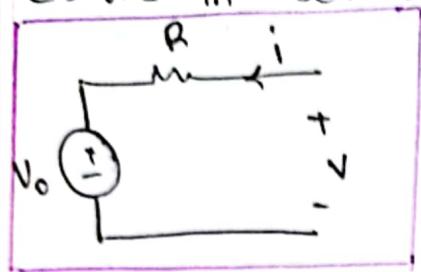(1) V & S in series with $\alpha \rightarrow R$ ($V, S, +R_S$)



$$V = iR + V_0$$


$$i = \frac{V - V_0}{R}$$

$$= \frac{V}{R} - \frac{V_0}{R}$$

$$i = \frac{V}{R} + \left(-\frac{V_0}{R} \right)$$

$$i = mV + c, c = -\frac{V_0}{R}$$

if $V_0 = +ve$,
 $c \rightarrow -ve$

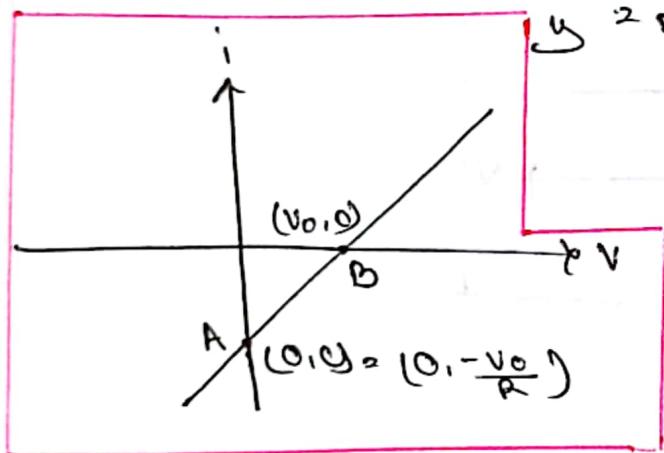


at $V, i = 0$

$$0 = \frac{V}{R} - \frac{V_0}{R}$$


$$\Rightarrow V = V_0$$

if we change R ?

m & c will change.

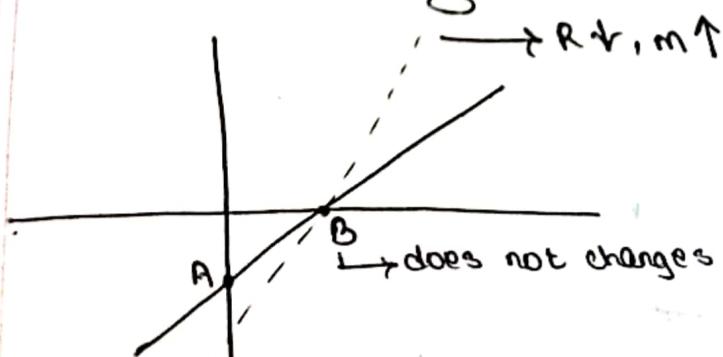

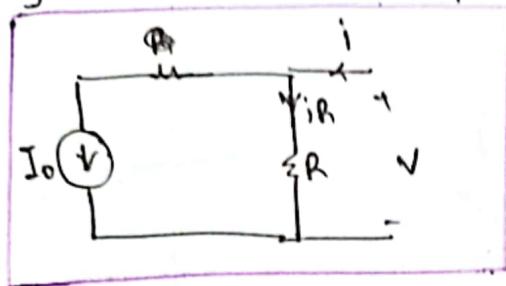ii) Current source in parallel to R ($i_s + R_p$)




Applying KCL,

$$i = i_R + I_0$$

$$\Rightarrow i = \frac{V}{R} + I_0$$

$$y = mx + c, c = I_0$$


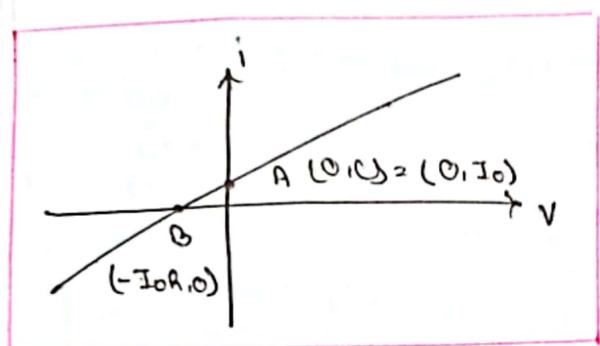
if $I_0 \rightarrow +ve$
 $c \rightarrow +ve$



$$i = 0, \frac{V}{R} + I_0$$

$$\Rightarrow V = -I_0 R$$

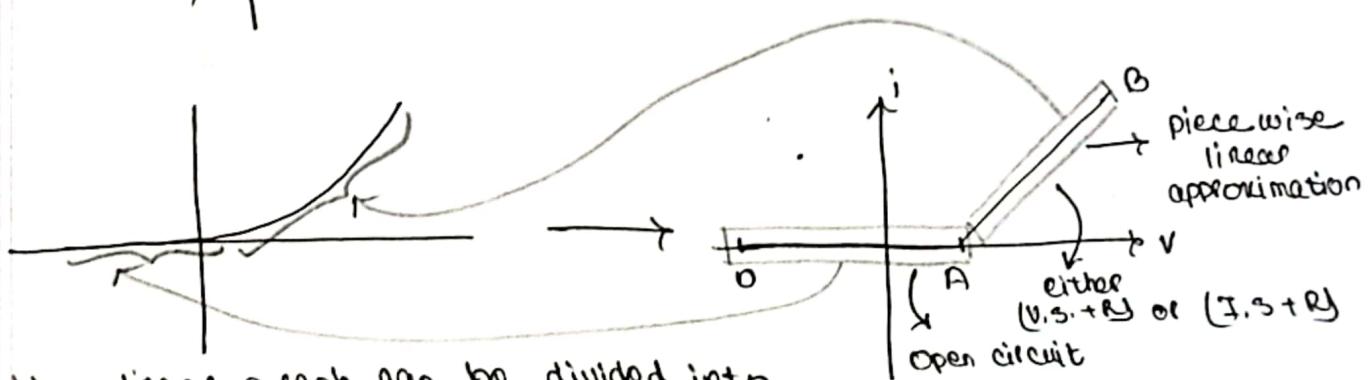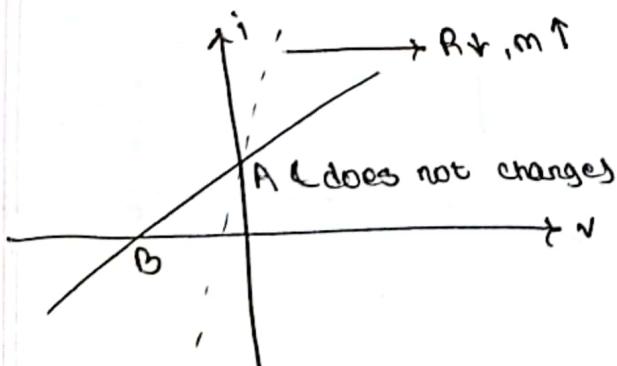if R changes, A does not change
as there is no $R \cdot B$ changes.



Non-linear graph can be divided into linear parts and solved.

(a) \rightarrow $i = \frac{V}{R}$ in the following network

$$A \rightarrow B \rightarrow m = \frac{1}{R_1} = \frac{1}{0.2} = 5 \text{ K}\Omega$$

$$B \rightarrow C \rightarrow R_2 = \infty \text{ K}\Omega$$

$$C \rightarrow D \rightarrow R_3 = \frac{2-2}{3-0} = \frac{0}{3} = 0 \text{ K}\Omega \text{ (voltage source with } 2 \text{ V)}$$

$$D \rightarrow E \rightarrow m = 0.2, R_4 = \frac{1}{0.2} = 5 \text{ K}\Omega$$

$$\text{at } DE, R = \frac{1}{\text{slope}} = \frac{1}{0.2} = 5 \text{ K}\Omega$$

$$C.S + R_P = i = \frac{V}{R} + I_0$$

$$i = \frac{V}{5} + I_0$$


at D (2, 3)

$$3 = \frac{2}{5} + I_0$$

$$I_0 = 3 - \frac{2}{5}$$

$$I_0 = 2.6 \text{ mA}$$


$$i = \frac{V}{5} + 2.6$$

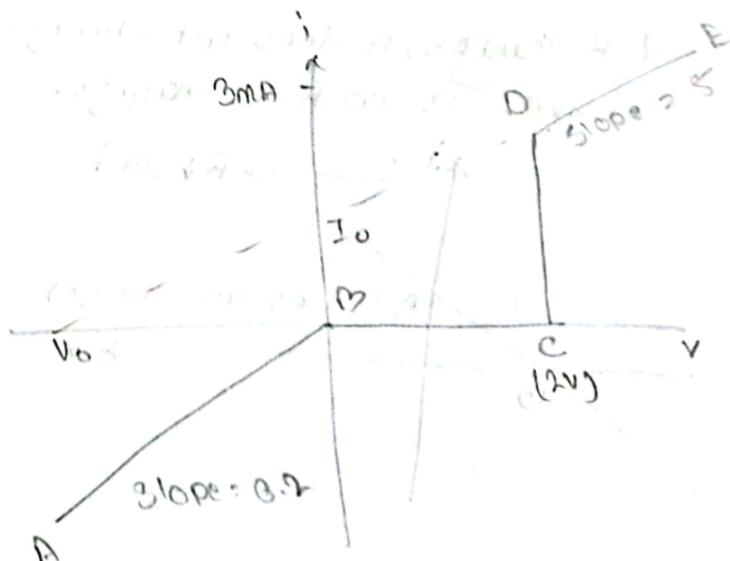





MONDAY

DATE: 13/02/23

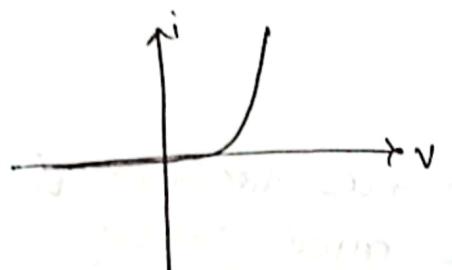
* Non-linear devices: Semiconductors, diodes, transistors, etc.



* AC to DC conversion:

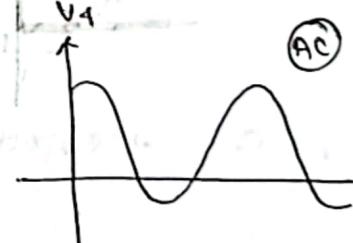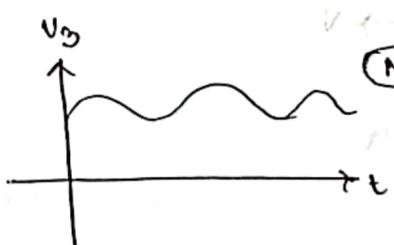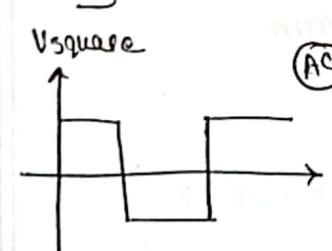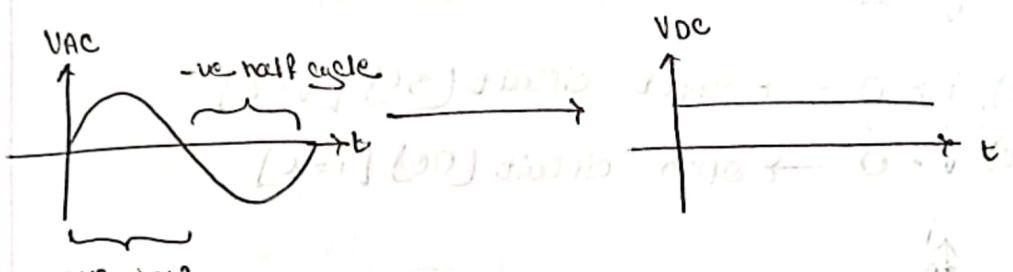


* AC to DC

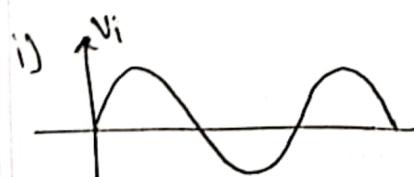

Rectification
only one side appears (+ve/-ve)



ii) Filtering

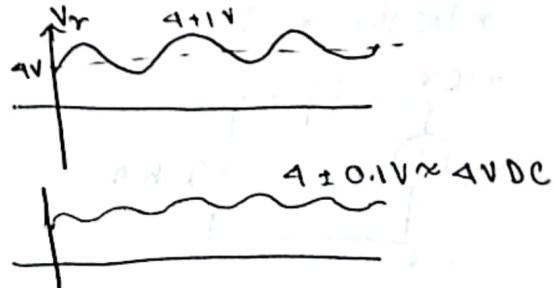

iii) Regulation

* Rectification & magnification require non-linear device.

* Filtering requires capacitor.


* Rectification allows current flow in +ve direction to get the +ve curve. It does not allow current flow in -ve direction and no curve is produced, i.e.

* Non-linear device: we want to have a value.



we want: i) $i > 0 \rightarrow$ short circuit [SC] [$V=0$]

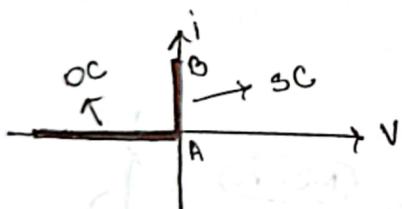ii) $V < 0 \rightarrow$ open circuit [OC] [$i=0$]



expected result



* Diode



i) $i_d > 0 \rightarrow$ ON ($V_d = 0$) [short circuit]


ii) $V_d < 0 \rightarrow$ OFF ($i_d = 0$) [open circuit].

* Node in DC:

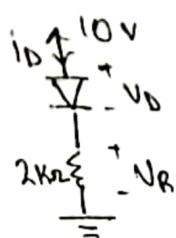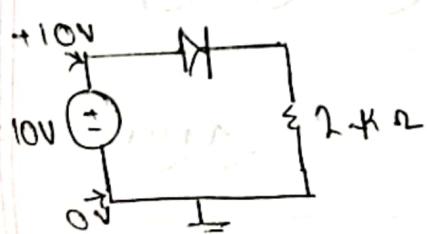

* We have solve twice.
(i) considering diode to be ON, find the variables.
(ii) considering diode to be OFF, find the variables.
(i) or (ii) must have, the assumptions

Let the diode be is ON. \rightarrow SC

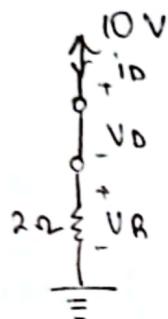

$$\therefore V_D = 10V$$


$$id = \frac{10-0}{2} = 5 \text{ mA} \neq 0$$

(assumption verified)

$$V_R = id * R$$
$$= 25 * 2$$

$$V_R = 10V$$

Say, diode is Off \rightarrow OC

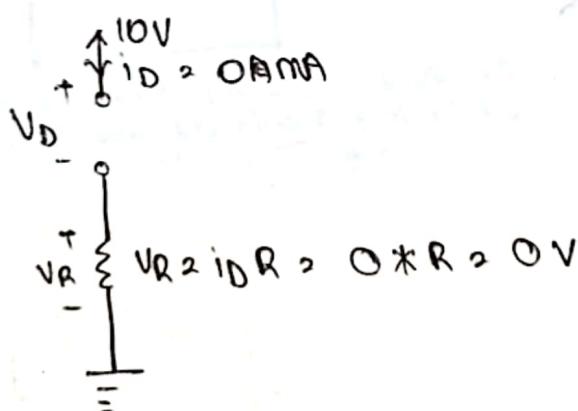


$$\text{Hence, } V_D = V_A - V_C$$

$$= 10 - 0$$


$$V_D = 10V \neq 0$$

(assumption wrong)

⑥

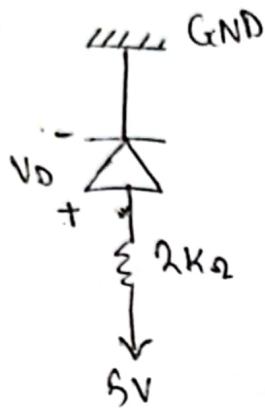

Let the diode be ON \rightarrow SC

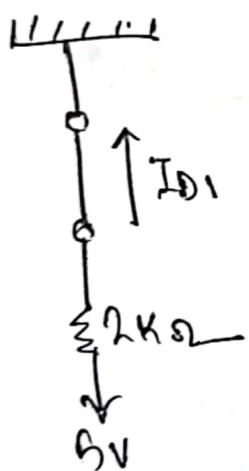


$$I_{D1} = \frac{5 - 0}{2} \text{ or } I_{D1} = 2.5 \text{ mA} \approx 0 \text{ mA}$$

∴ Assumption is correct.


WEDNESDAY

DATE: 15/02/23



* Ideal diode

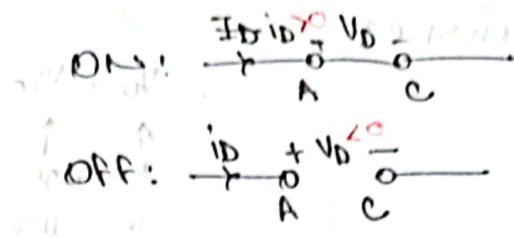

* Application as Half-wave rectifier:

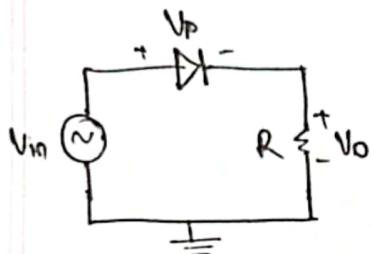


(+) half cycle:

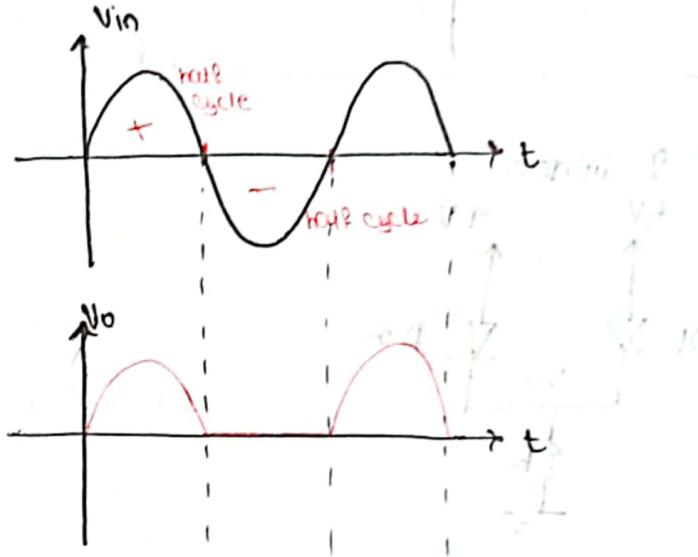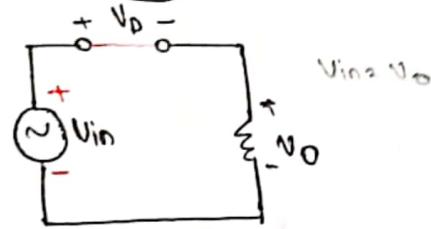


* when +ve part of diode is connected to higher potential, diode is generally ON.

(-) half cycle:

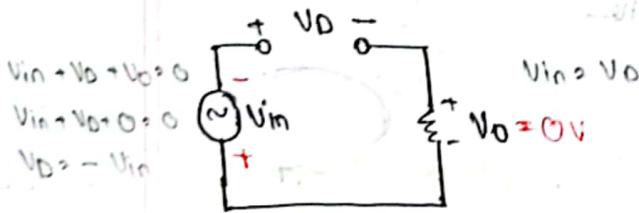


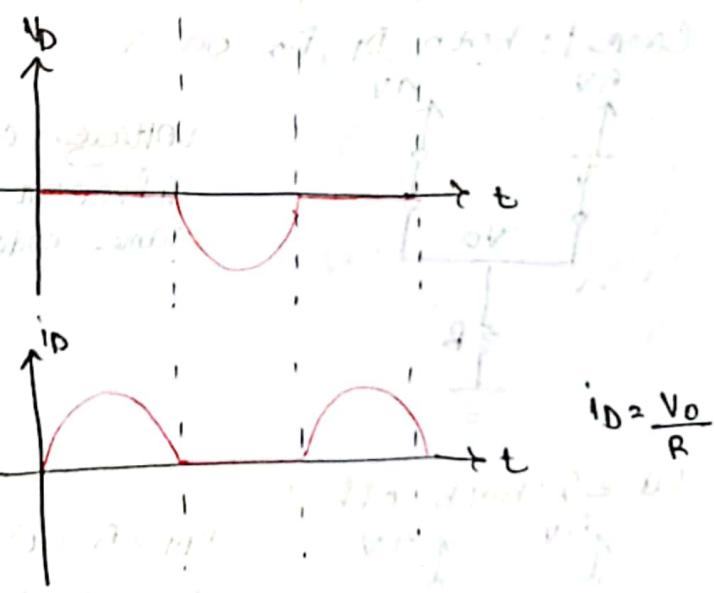* when +ve part of diode is not connected to higher potential, diode is generally OFF.



$$i_D = \frac{V_o}{R}$$

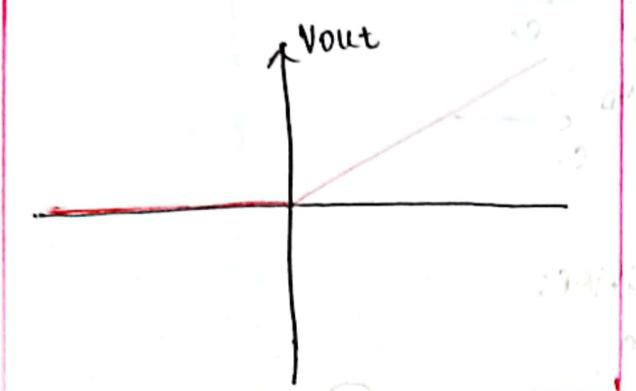* Transfer characteristics: (for ideal diodes)




$$V_o = V_{in}$$


$$V_o = 0$$

$$V_o = mV_{in} \quad [m = 1]$$


* 2 diodes

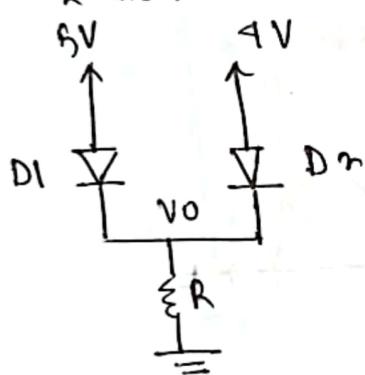

Graph of Vout vs Vin for two diodes. The x-axis is Vin and the y-axis is Vout. A red line starts at (0,0) and goes to (1,1). A blue line starts at (0,0) and goes to (1,0). The output Vout is the difference between these two lines."/>

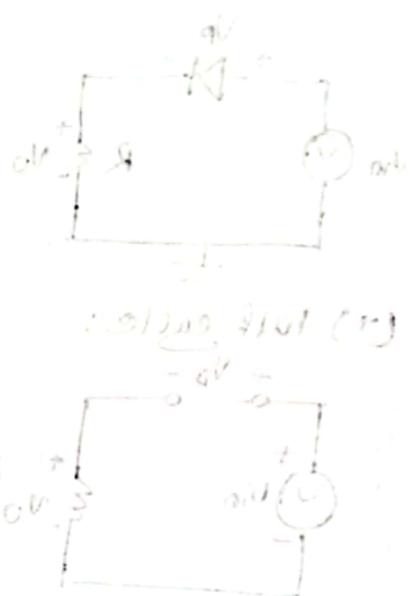


Case 1: both D_1, D_2 on \times

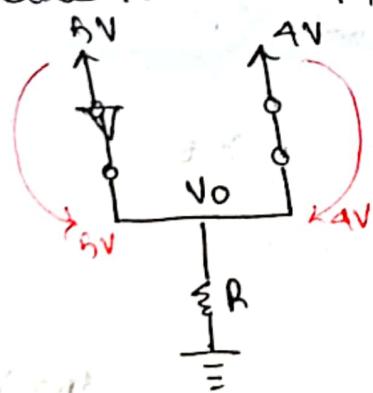

Voltage cannot be different at the same node




Case 2: both off \times


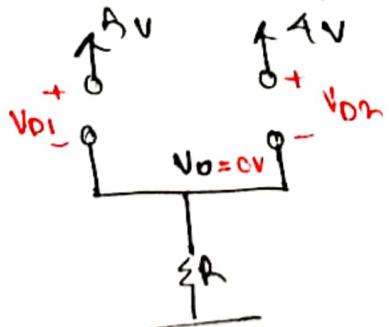


$$V_{D1} = 5 - 0 = 5V \neq 0$$

$$V_{D2} = 4 - 0 = 4V \neq 0$$

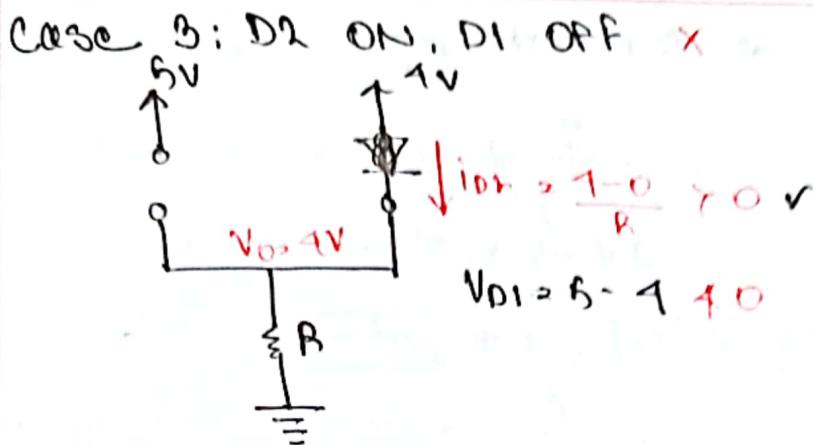


Case 4: D1 ON, D2 OFF

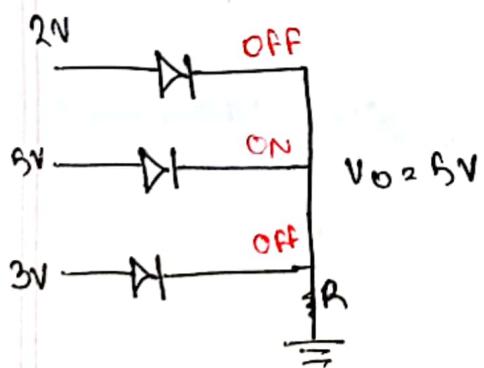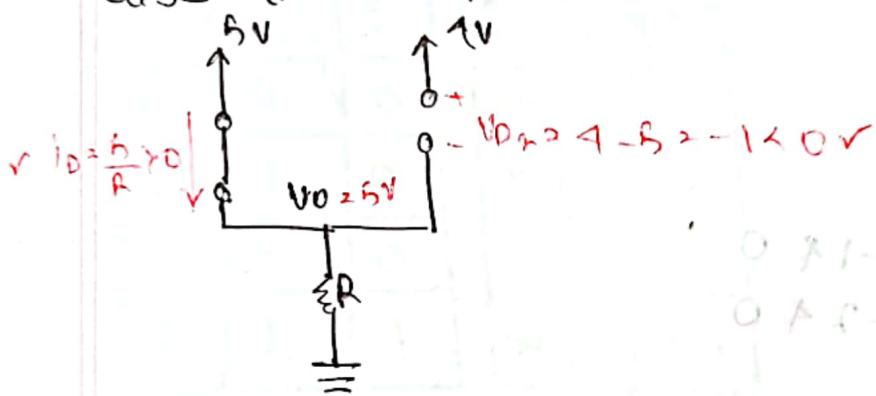


* The diode connected with the highest potential is ON and the rest is OFF. (For parallel V0 = MAX(V1, V2, V3, ..., VN))

$$V_0 = \text{MAX}(V_1, V_2, V_3, \dots, V_N)$$

* exception

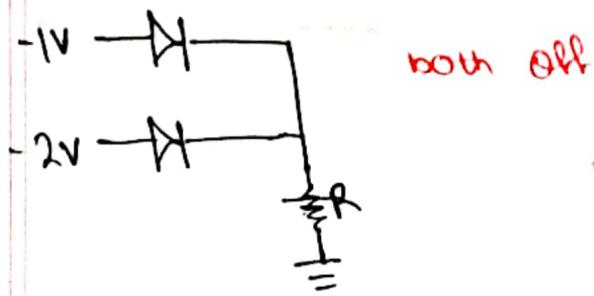


* with out forward bias

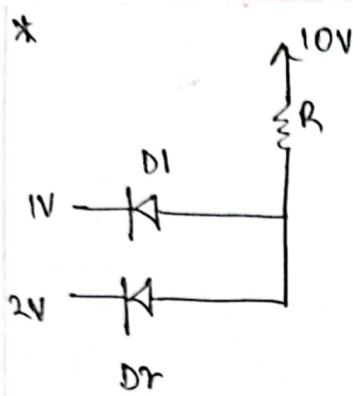

Case 1: Both ON
(Same reasons $\rightarrow \times$)


Case 2: Both OFF \times

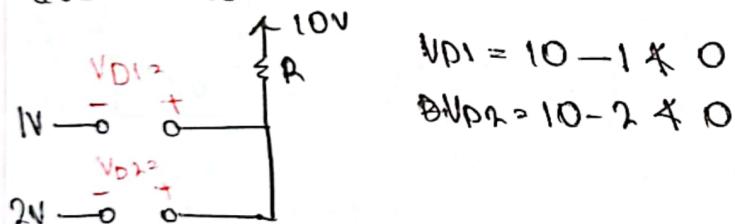

$$V_{D1} = 10 - 1 \neq 0$$

$$V_{D2} = 10 - 2 \neq 0$$

Case 3: D1 ON, D2 Off

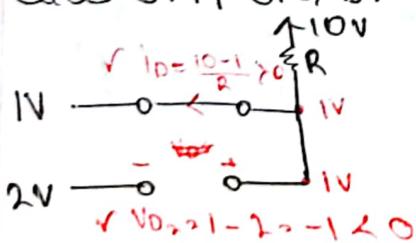


$$V_{D1} = 10 - 1 = 9V$$

$$V_{D2} = 1 - 2 = -1V$$

* The diode connected to the lowest potential is ON and the rest is OFF. (In series)

$$V_0 = \min(V_1, V_2, V_3, \dots, V_N)$$

* exception (V_{ref})

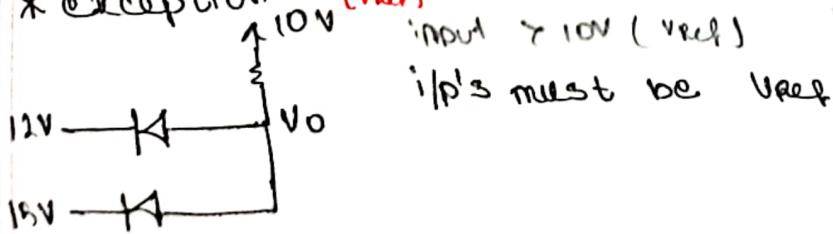

input $> 10V (V_{ref})$

i/p's must be V_{ref}

* Logic gate using ideal diode

Representing Boolean in circuit

(voltage) $5V \rightarrow 1$, $0V \rightarrow 0$

$3.3 - 5V \rightarrow 1$, $0 - 2.7V \rightarrow 0$

AND:

x	y	f
0	0	0
0	1	0
1	0	0
1	1	1

x	y	f
0V	0V	0V
0V	5V	0V
5V	0V	0V
5V	5V	5V

(min)

OR:


x	y	f
0	0	0
0	1	1
1	0	1
1	1	1


x	y	f
0V	0V	0V
0V	5V	5V
5V	0V	5V
5V	5V	5V

(max)


* Implement using ideal diode:

$$f = x + y$$


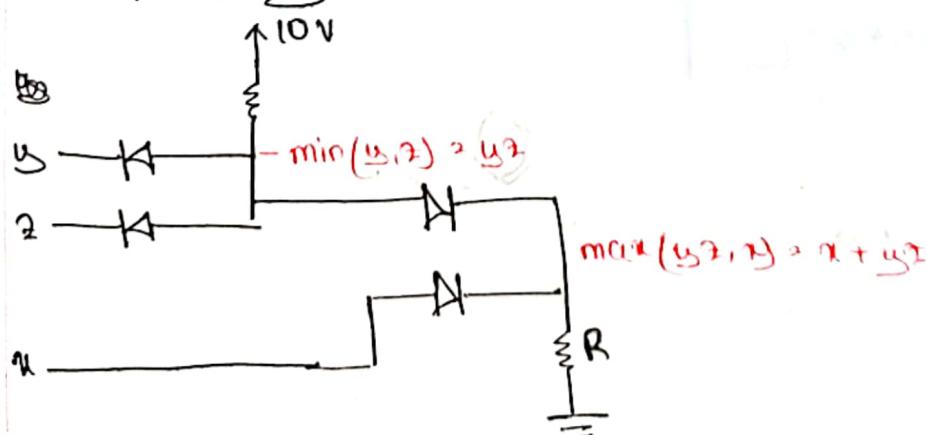


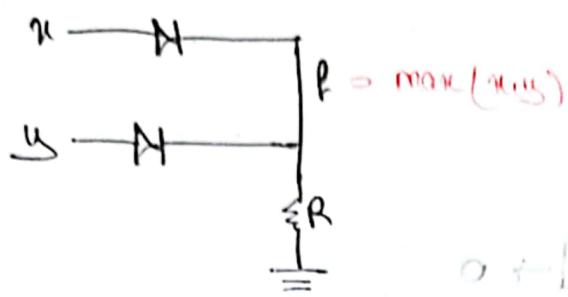

when both ends of f is shorted

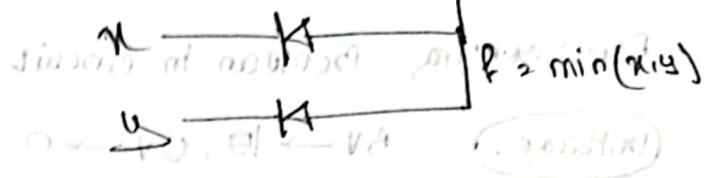

$0 < [f - U] < [U - f]$

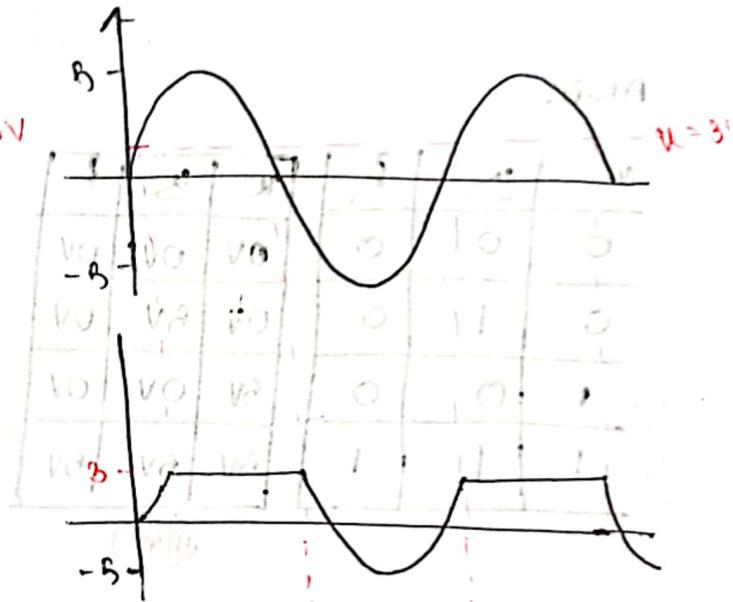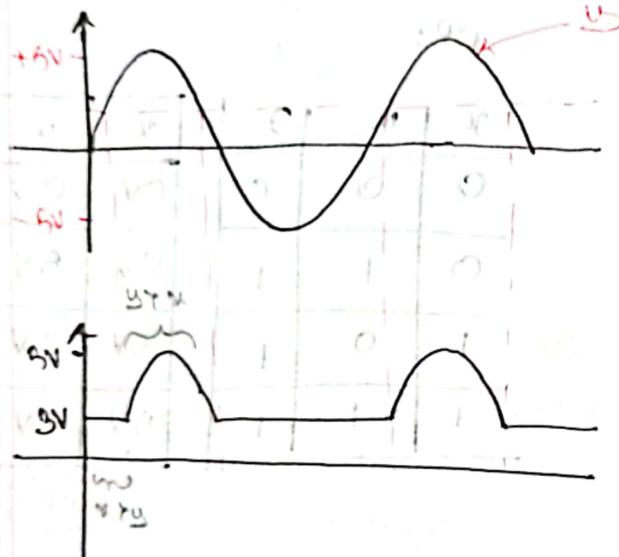

when both ends of f is shorted

$$f = U = 3V$$


V_{01}





MONDAY

DATE: 20/02/23

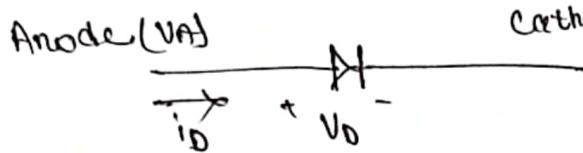Ideal Diode Model (6.9) with applied material physics - 2 - p 919



OFF state: Open circuit

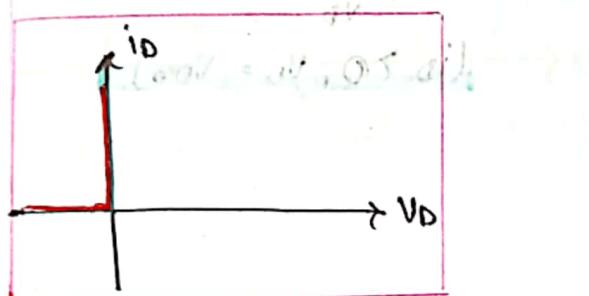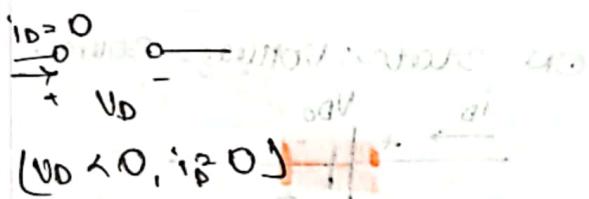


ideal diode


Cathode (VC)

αT


ON state: Short circuit

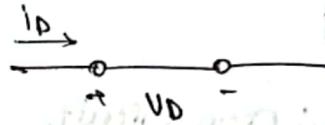

$$(i_D \neq 0, V_D = 0)$$

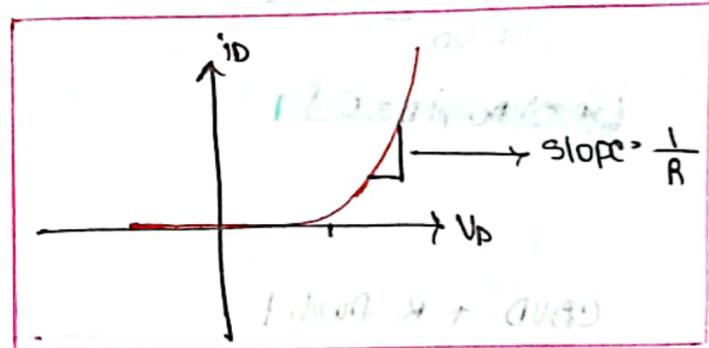

Real diode

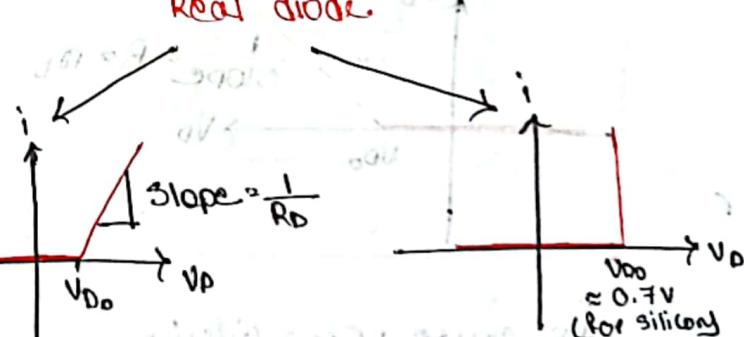

if slope \uparrow , $R_D \downarrow$
(CVD + R Model)

if slope $\rightarrow \infty$, $R_D \rightarrow 0$
(Constant voltage drop (CVD) model)

Dependence of i on V_D - $i = i_0 e^{V_D / V_T}$

for diode with $V_D > 0$


and \rightarrow from $i = i_0 e^{V_D / V_T}$, $i = i_0 e^{V_D / V_T}$

and $i = i_0$

CE101 (2021-22)

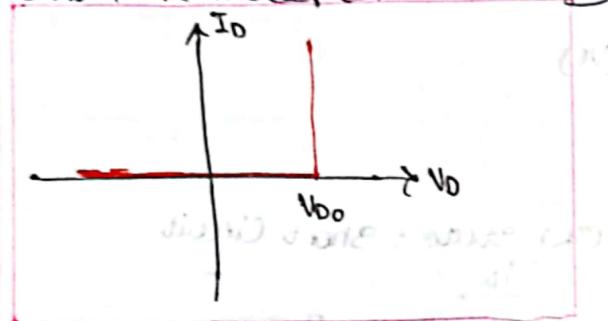10.2.2.2

CVI + R model (constant voltage drop (CVD) model)




OFF state: Open Circuit

$$i_D = 0 \quad (V_D < V_{D0}, V_D \neq 0)$$

$$(V_D < V_{D0}, i_D = 0)$$

CBVD + R model

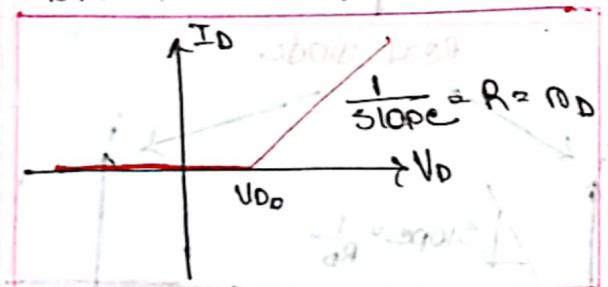


OFF state: Open Circuit

$$i_D = 0, V_D = 0$$

$$(V_D < V_{D0}, V_D \neq 0)$$


$$(V_D < V_{D0}, i_D = 0)$$

ON state: Voltage source

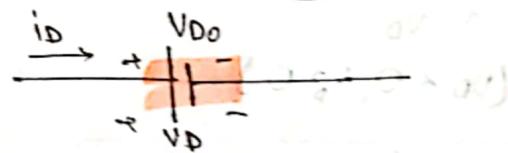

$$(i_D > 0, V_D = V_{D0})$$

ON state:

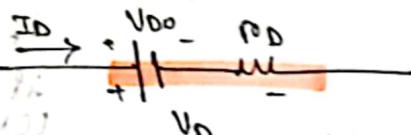


$$(V_D = V_{D0} + i_D r_D, i_D > 0)$$



if r_D small, $V_D = i_D r_D$ small + V_{D0} negligible

$$V_D = V_{D0}$$



Half-wave rectifiers (Ideal diode model)

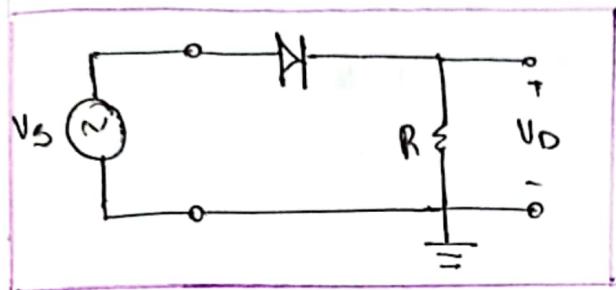


(+) half cycle of V_s

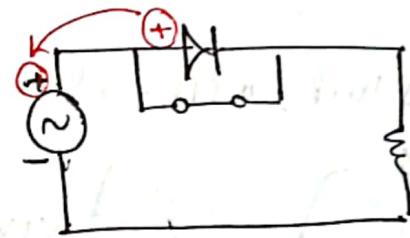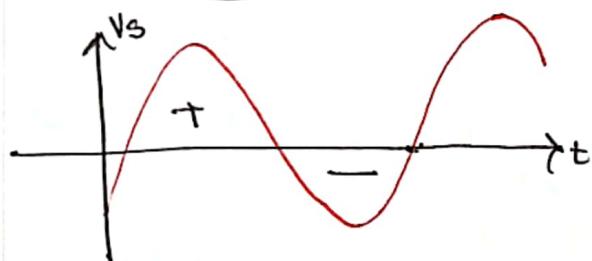


(-) half cycle of V_s

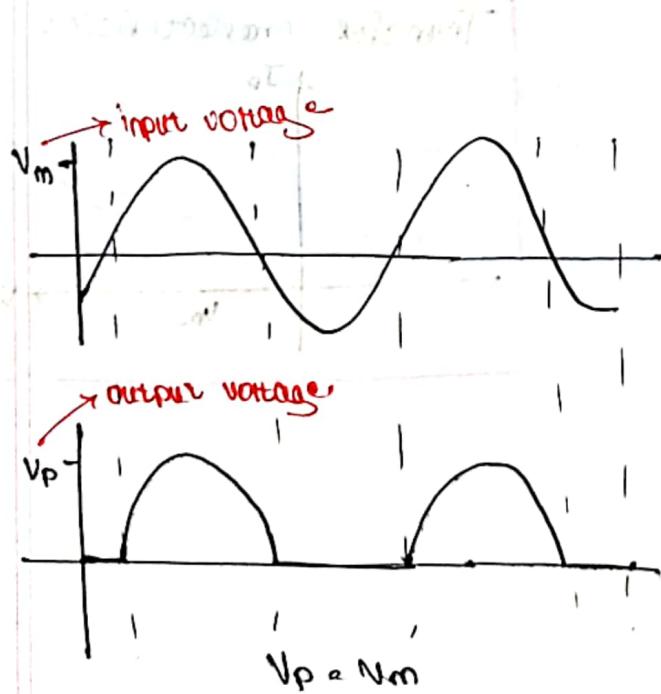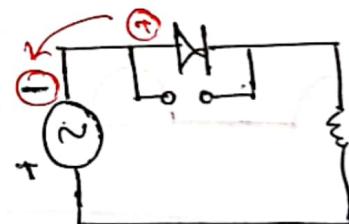

Half-wave rectification (CVD model)

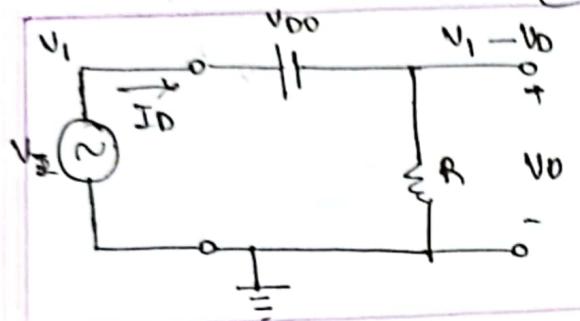


(+) half cycle, $V_0 = V_i - V_{D0}$

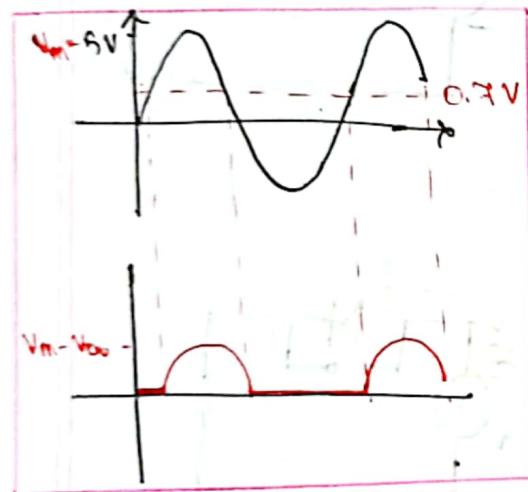


$$V_i = V_m \sin \omega t$$


max = 1, min = -1

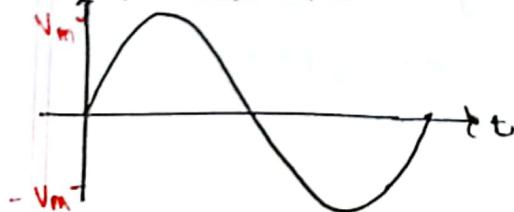

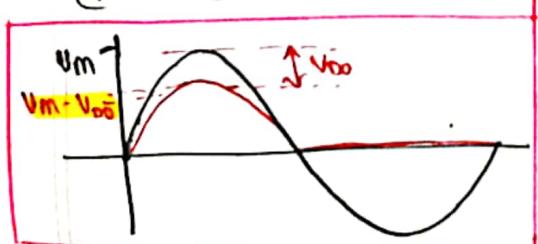
max^m value of output = $V_m - V_{D0}$
(peak of output)



Transfer characteristics

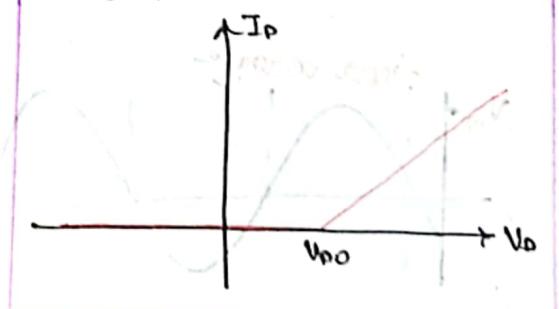


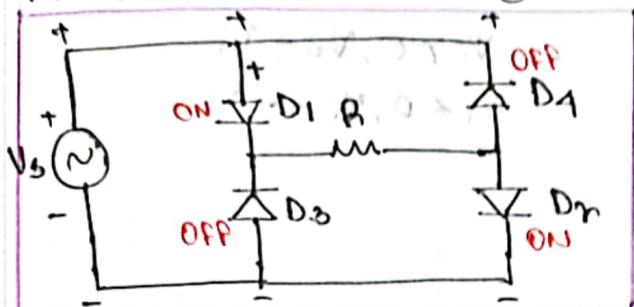Full wave rectifier (ideal diode & CWD model)





For $+ve$

(+) half cycle

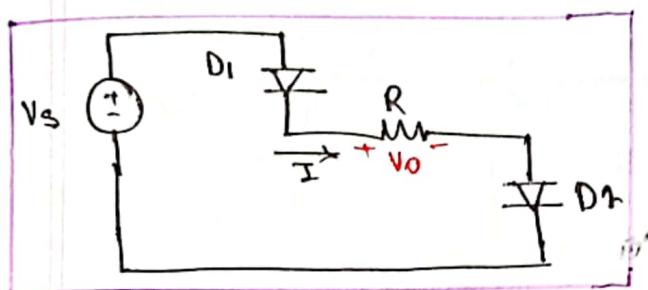


(-) half cycle

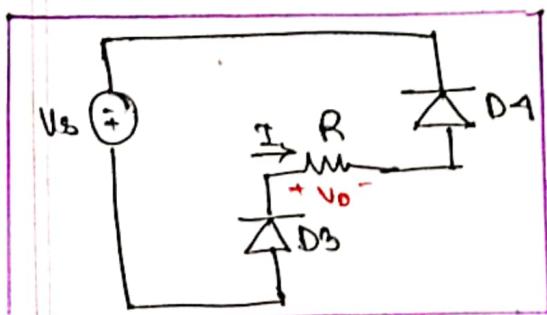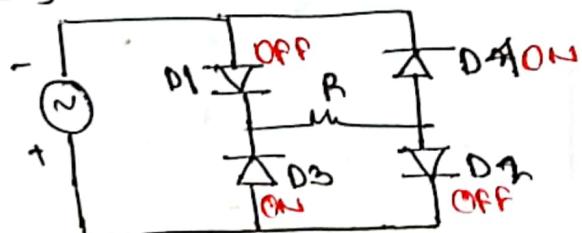

If the (+ve) end of diode and (+ve) terminal of source are on the same node, then that diode is ON.

Also, if the (-ve) end of the diode and (-ve) terminal of source are on the same node, then that diode is ON. Other than these conditions, all the diodes are OFF.

1) Ideal:

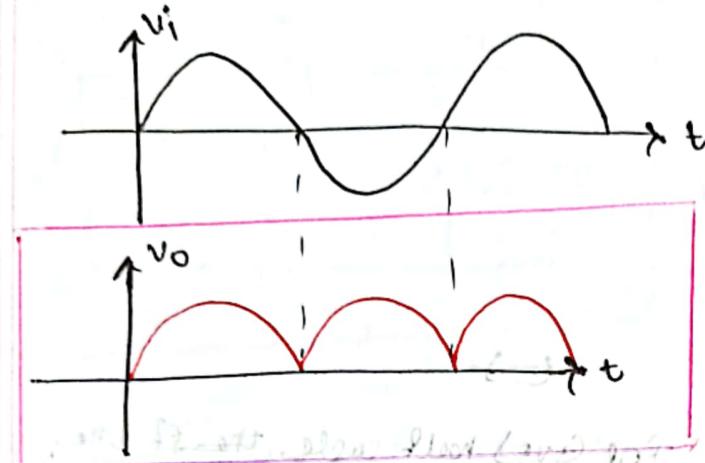

$$V_i > 0, V_o = V_i$$


$$V_i < 0, V_o = -V_i$$






signs first (+)

2) CVD Model:

$$V_{o2} - V_i = 2 \cdot V_{DD}$$

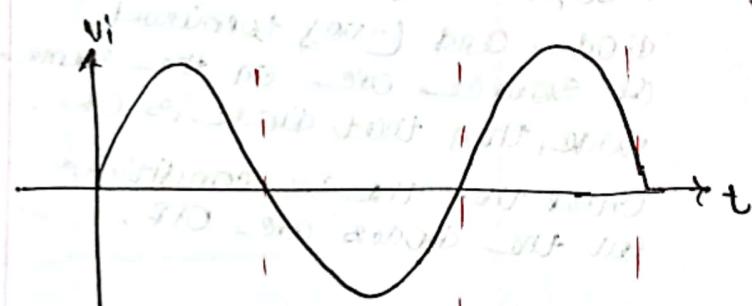

signs first (+)

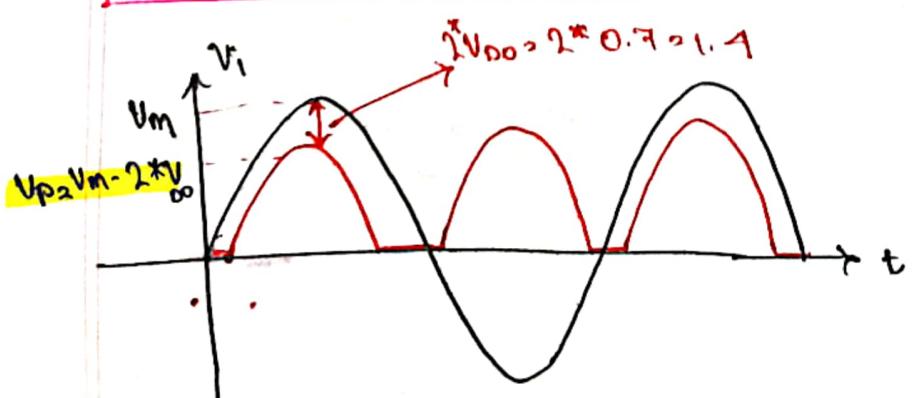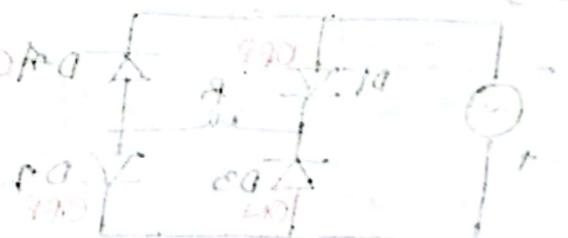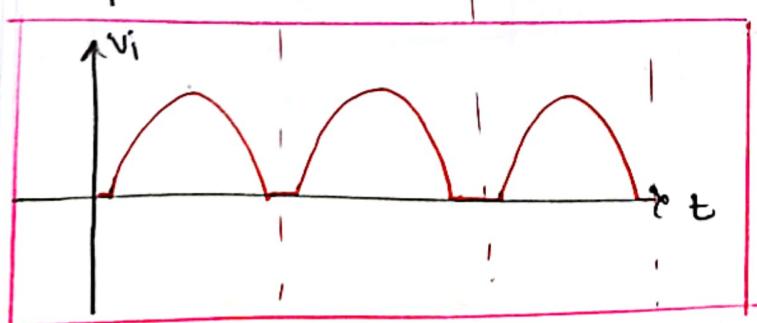


8/20/2021


11:00 AM

* Transfer Characteristics

ideal diode model

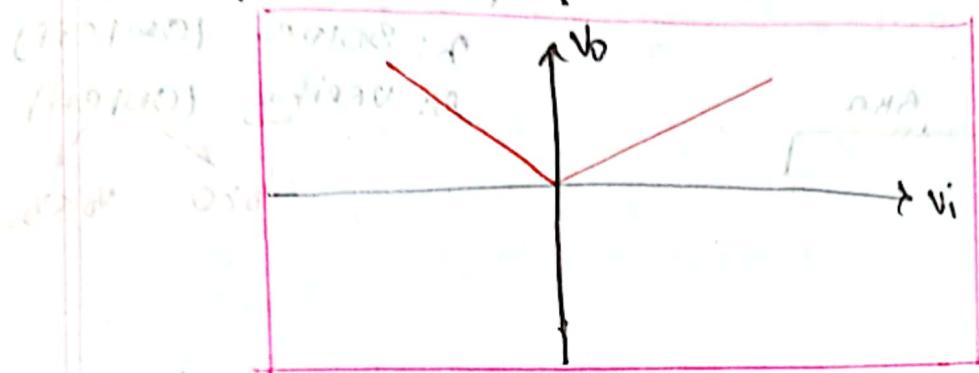


idealized model

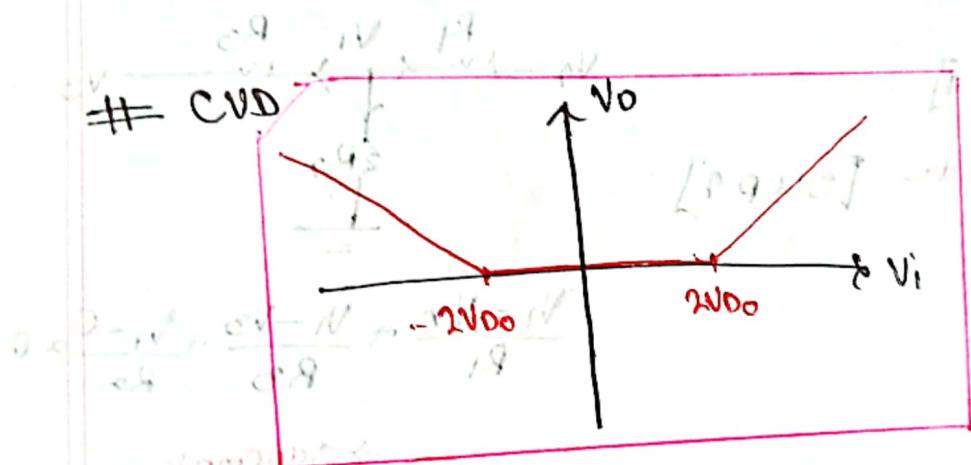

idealized model



idealized model

 

idealized model




idealized model

WEDNESDAY


DATE: 22/02/23

* Method of Assumed State

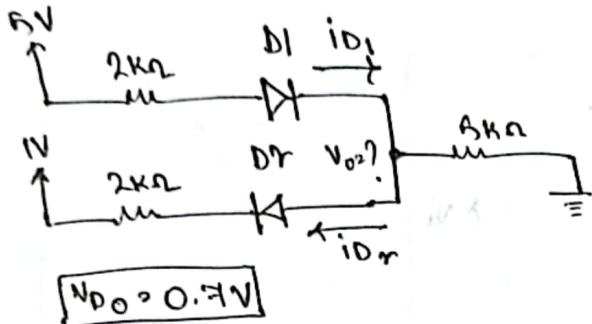

* 30th:

both D1, D2 ON [Step 1]

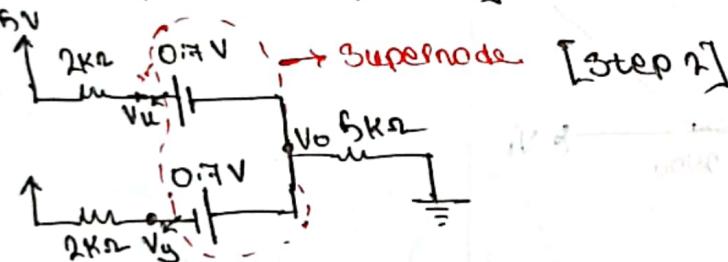

At the supernode,

$$\frac{V_0 - 0}{2} + \frac{V_U - 0}{2} + \frac{V_Y - 0}{2} = 0$$

Here,

$$V_U - V_0 = 0.7 \Rightarrow V_{UR} = V_0 + 0.7$$

$$V_0 - V_D = 0.7 \Rightarrow V_D = V_0 - 0.7$$

$$\cancel{V_U - V_D}$$



$$\Rightarrow \frac{V_0}{2} + \frac{V_0 + 0.7 - 0}{2} + \frac{V_0 - 0.7 - 0}{2} = 0$$

$$\Rightarrow V_0 \left(\frac{1}{2} + \frac{1}{2} + \frac{1}{2} \right) + \frac{-1.4}{2} + \frac{-1.4}{2} = 0$$

$$\Rightarrow V_0 = \frac{\frac{1.3}{2} + \frac{1.4}{2}}{\frac{1}{2} + \frac{1}{2} + \frac{1}{2}} \Rightarrow V_0 = 2.6V$$

Step 1: Assume (ON/OFF)
 2: Solve (ON/OFF)
 3: Verify (ON/OFF)
 $iD > 0$ $V_D < V_{D0}$

Review Supernode:

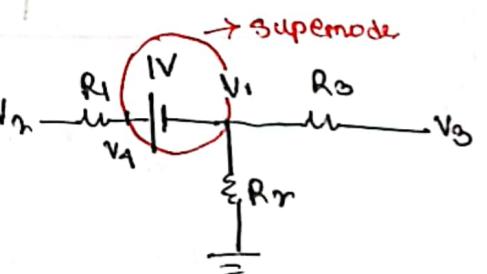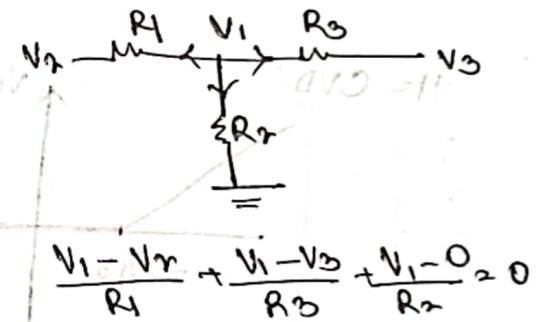

At the Supernode,

$$\frac{V_1 - V_3}{R_3} + \frac{V_1 - 0}{R_2} + \frac{V_1 - V_r}{R_1} = 0$$

$$\text{Here, } V_1 - V_3 = 0 \quad \text{1}$$


$$\Rightarrow V_1 = V_1 + 1$$

[Step 3]

$$i_{D1} = \frac{B - V_u}{r} = \frac{B - (V_0 + 0.7)}{r} = 0.9 \text{ mA} \neq 0$$

$$i_{Dr} = \frac{B - V_u - 1}{r} = \frac{(B - 0.7) - 1}{r} = 0.1 \text{ mA} \neq 0$$

∴ the assumption is correct.

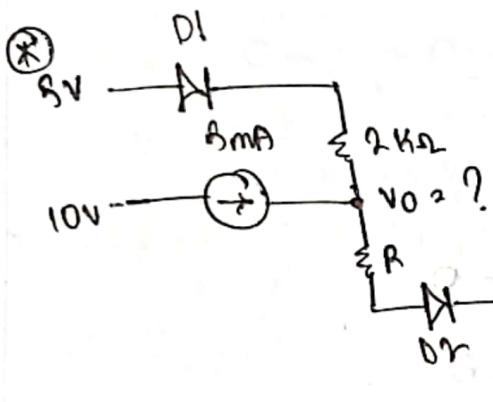


$$(i) R = 1\text{ k}\Omega$$

$$(ii) R = 5\text{ k}\Omega \rightarrow \text{HW}$$

$$V_{D0} = 0.8 \text{ V}$$

[cut-in voltage / threshold]

(i) Soln: Let D_2 ON, D_1 Off [Step 1]

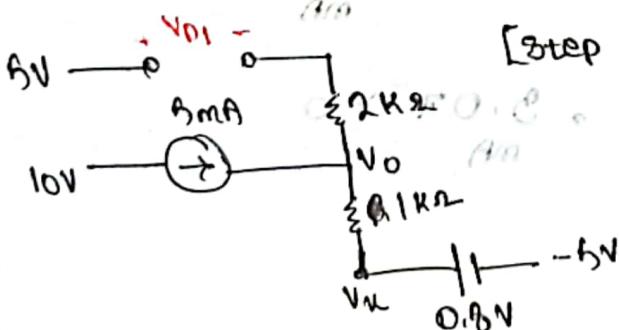

Hence,

$$V_{u1} - (-5) = 0.8 \Rightarrow V_{u1} = -4.2 \text{ V}$$

at V_0 node,

$$\frac{V_0 - V_u}{1} - B = 0$$

$$\frac{V_0 - (-4.2) - B}{1} = 0 \Rightarrow V_0 = 0.8 \text{ V}$$

[Step 2]

[Step 3]


$$i_{D2} = \frac{V_0 - V_u}{1} = \frac{B}{1} = 5 \text{ mA} \neq 0 \checkmark$$

$$V_{D1} = V_A - V_c = B - 0.8 = 4.2 + 0.8 \times$$

[By considering D_2 - ON, condition is fulfilled. So, for the next assumption, keep D_2 - ON and change D_1 only \rightarrow Rule of Thump]

* Let D_1 ON, D_2 ON

[Eq 9.28]

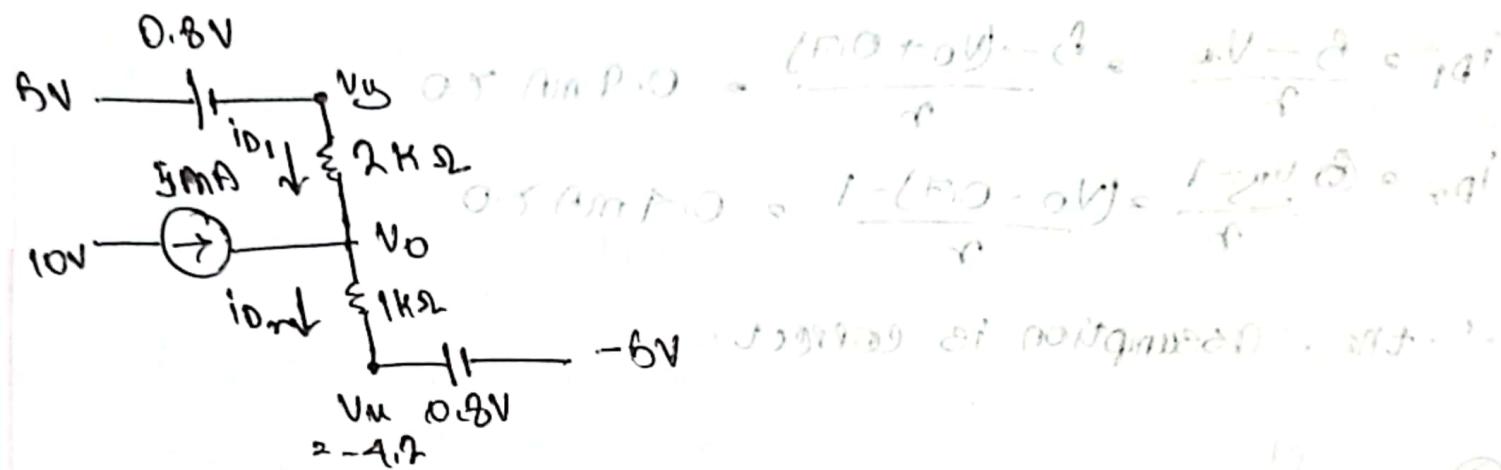

Here, $V_{D1, D2} = -4.2$ V

and, $6 - V_{D1, D2} = 0.8 \Rightarrow V_{D1, D2} = 4.2$ V

At V_o node, $\frac{V_o - V_{D1, D2}}{1} + \frac{V_o - V_{D1, D2}}{2} - 6 = 0$

$$\Rightarrow \frac{V_o - 4.2}{1} + \frac{V_o - 4.2}{2} - 6 = 0$$
$$\Rightarrow V_o = 1.93$$
 V

$i_{D1} = \frac{V_{D1, D2} - V_o}{2} = \frac{4.2 - 1.93}{2} = 1.14$ mA

$i_{D2} = \frac{V_{D1, D2} - V_o}{2} = \frac{4.2 - 1.93}{2} = 1.14$ mA

The assumption is correct.

Find $i_{D1, D2} = \frac{V_{D1, D2} - V_o}{1} = 4.2$ mA

$i_{D1, D2} = 4.2$ mA

and $i_{D1, D2} = 4.2$ mA

and $i_{D1, D2} = 4.2$ mA

and $i_{D1, D2} = 4.2$ mA


$V_{D1, D2} = 4.2$ V

when $i_D = 0$

$i_D = 0$

$V_{D1, D2} = 4.2$ V

Case 1: D1 = ON, D2 = OFF

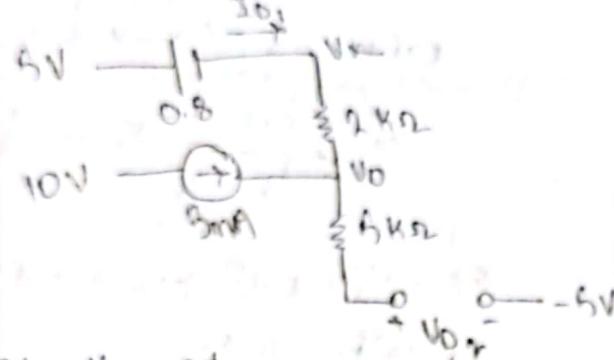

At V0 node,

$$\frac{V_0 - 1.2}{2k\Omega} + \frac{V_0}{5k\Omega} - \frac{5}{5mA} = 0$$


$$V_0 = 4.2V$$

$$5 - V_0 = 0.8 \Rightarrow V_0 = 4.2V$$

$$I_{D1} = \frac{1.2 - 4.2}{2k\Omega} = -5mA \text{ (0 mA)}$$

$$V_{D2} = 10V - 5 = 10.5V + 0.8V$$

Case 2: D1 = OFF, D2 = ON

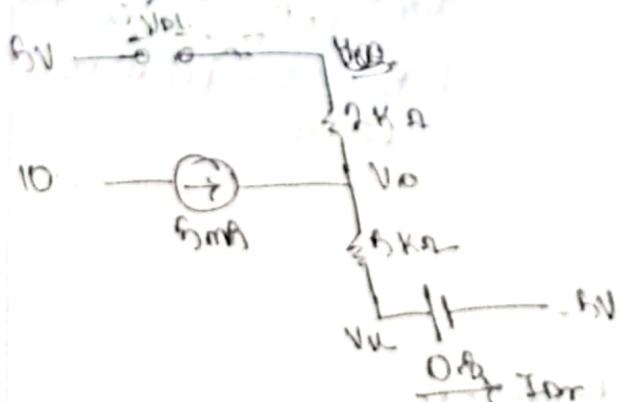


$$V_0 - (-5) = 0.8 \Rightarrow V_0 = 4.2V$$

$$\frac{V_0 - 10V}{5k\Omega} = 10mA \Rightarrow V_0 = 10V$$

$$I_{D2} = \frac{V_0 - V_{D2}}{2k\Omega} \Rightarrow I_{D2} = 2mA \text{ (0 mA)}$$
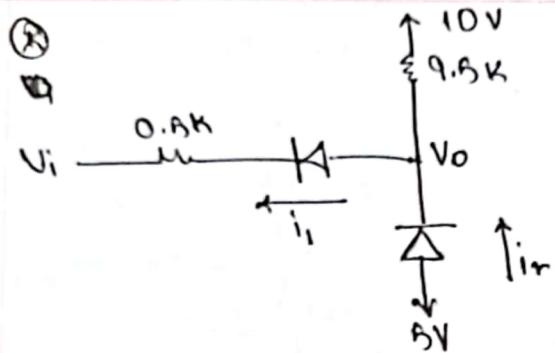
$$V_{D1} = 5 + 0.8 - V_0 \Rightarrow 5 - 5.2 = -0.8 < 0.8 \quad (\text{The assumption is incorrect.})$$




$$i_1 = ? \quad i_2 = ? \quad V_o = ?$$

use CVD model with $V_{D0} = 0.6V$

$$(i) V_i = 2V \quad (ii) V_i = 4V$$

(i) Soln: both ON

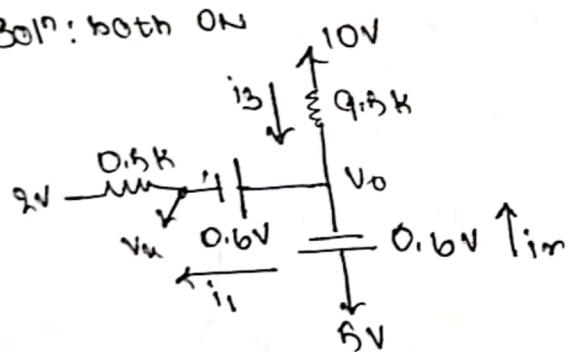

$$\text{Here, } 5 - V_o = 0.6$$

$$V_o = 4.4V$$

$$\text{and, } V_o - V_{D2} = 0.6$$

$$\Rightarrow V_{D2} = V_o - 0.6 = 3.8V$$

$$i_1 = \frac{V_{D2} - V_i}{0.5} \Rightarrow i_1 = \frac{3.8 - 2}{0.5} = 3.6 \text{ mA} \neq 0$$

$$i_3 = \frac{10 - V_o}{0.5} \Rightarrow i_3 = \frac{10 - 4.4}{0.5} = 0.689 \text{ mA}$$


$$\text{At } V_o \text{ node, } i_3 + i_2 = i_1$$

$$i_2 = i_1 - i_3 = 3.6 - 0.689$$

$$\Rightarrow i_2 = 2.91 \text{ mA} \neq 0$$

∴ Assumption is correct.

(ii) Let $D1 = ON, M1 = OFF$

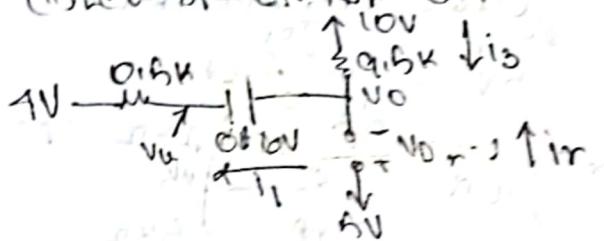

$$V_o = V_{D1} + 0.6 = 0.6 + 0.6 = 1.2V$$

$$V_{D1} = V_o - 0.6$$

$$\frac{V_o - 10}{0.5} + \frac{V_{D1} - 1.2}{0.5} = 0$$

$$\frac{10 - 1.2}{0.5} + \frac{V_{D1} - 0.6 - 1.2}{0.5} = 0$$

$$V_{D1} = 4.8V$$

$$V_{D1} = 4.8V - 0.6 = 4.2V$$


$$I_{D1} = \frac{4.2 - 1}{0.5} = 7.4 \text{ mA}$$

$$V_{D2} = 5 - 4.2 = 0.8V$$

The assumption is correct

Quiz - 01 (solution)

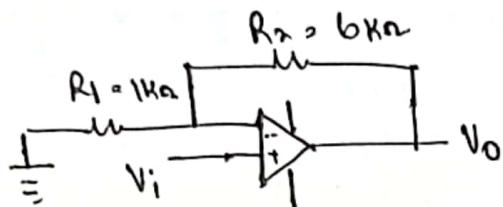(a) Non-inverting amplifier (π times amplification)



$$\text{We know, } V_0 = \left(1 + \frac{R_2}{R_1}\right) V_i$$

$$\text{Here, } 1 + \frac{R_2}{R_1} = \pi$$


$$\Rightarrow \frac{R_2}{R_1} = \pi$$

$$\text{if } R_1 = 1\text{k}\Omega, R_2 = 6\text{k}\Omega$$


$$(b) V_0 = \left(1 + \frac{R_2}{R_1}\right) V_i$$

$$\text{At } t = 1.5\text{ ms, } V_i = -1V$$

$$\therefore V_0 = \pi V_i \\ = -\pi V$$

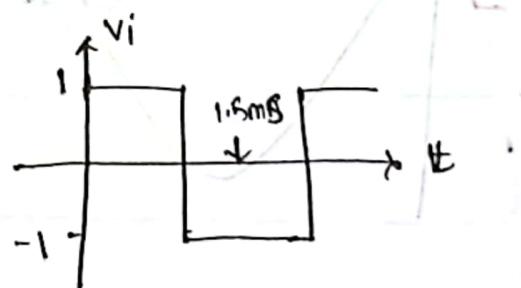
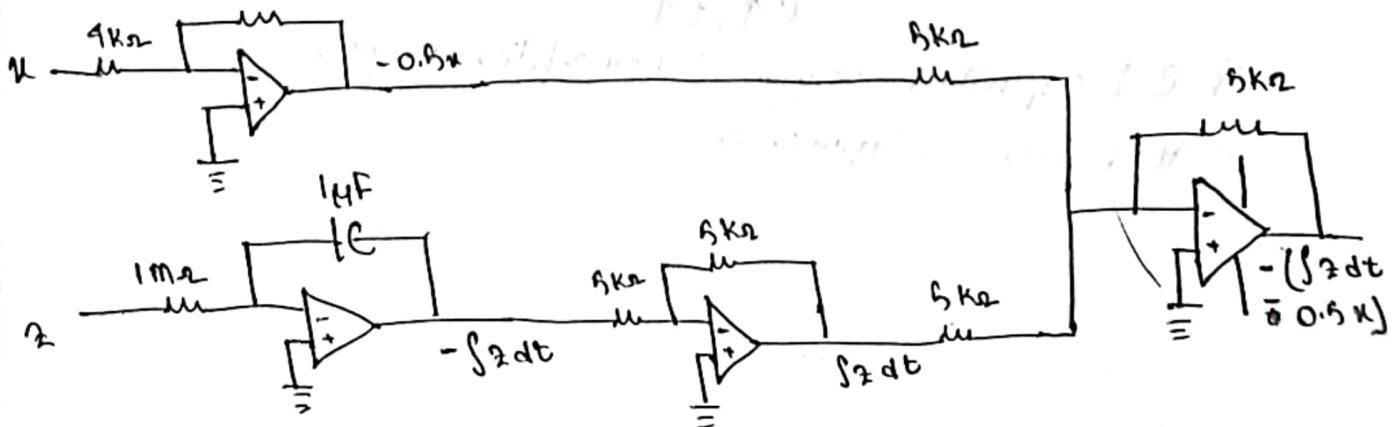
$$(c) f = 0.5\text{ K} - \frac{1}{2\pi R_2} = -\left(-0.5\text{ K} + \frac{1}{2\pi R_2}\right)$$




LECTURE

11

MONDAY

DATE: 27/02/23

filtering: Half-wave rectifier

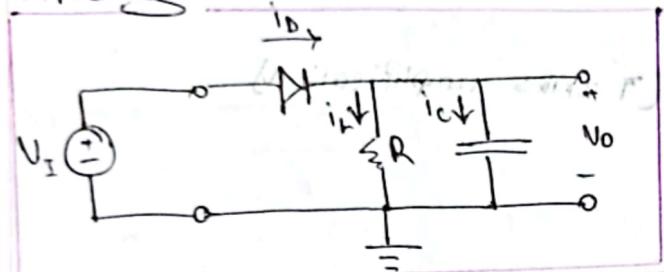

(initially) $V_O = 0V$

19.07.2022 2022-02-27 (0)

0.80 eV

0.41 eV


0.19 eV

0.07 eV

0.04 eV

0.01 eV

0.00 eV

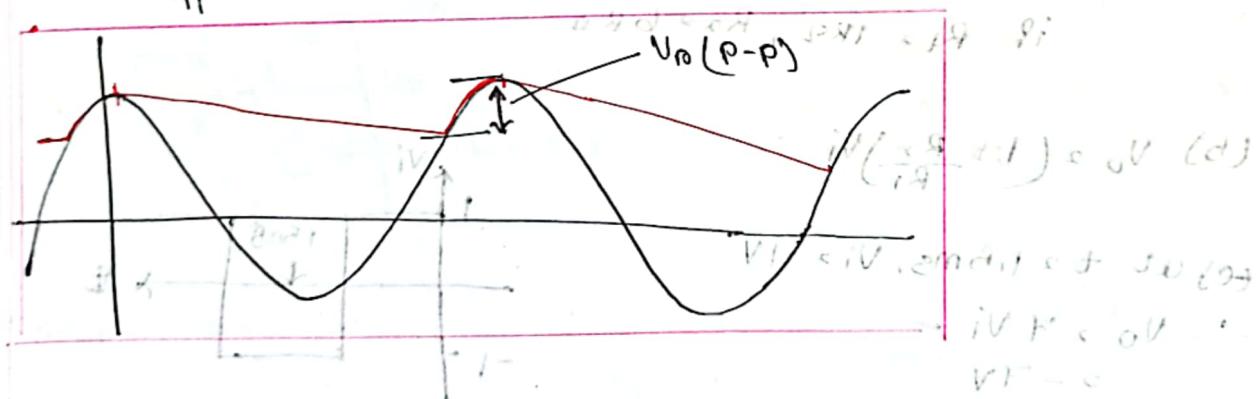


charging / discharging $t = 5T$

$$(i_b \cdot \delta) + 2h(RC) \rightarrow i_b \cdot \delta = 2h \cdot 0.8 \cdot 0.005 \cdot 0.001$$

$C \uparrow, t \uparrow$

if $C \uparrow$ capacitor slowly charges / discharges
Performance improves


$i_b \cdot \delta$

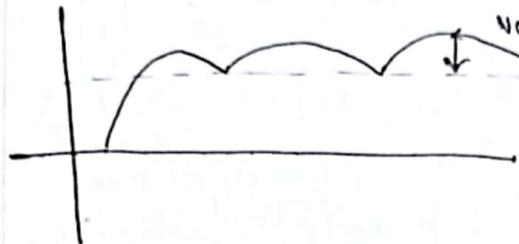

9.0.1.10.01
9.0.1.10.02

9.0.1.10.01
9.0.1.10.02

9.0.1.10.01
9.0.1.10.02

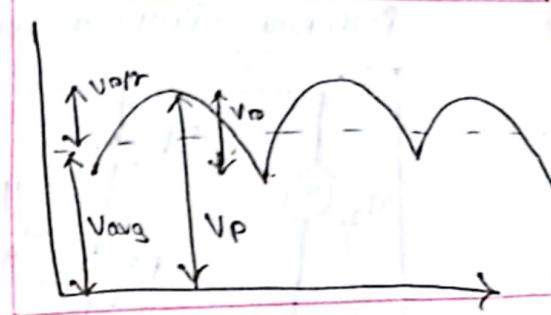

$$V_{avg} = V_{DC} = V_p - \frac{V_p(p-0)}{r}$$

$$V_o = V_{avg} \pm \frac{V_p}{r}$$

$$\textcircled{1} V_o = f \pm 0.7$$

$$\downarrow \quad \downarrow$$

$$V_{avg} \quad \frac{V_p}{r}$$

$$V_{avg} = 5 \text{ V}$$

$$V_p = \left(\frac{V_o}{r} \times 2 \right) = \left(\frac{0.7}{r} \times 2 \right) = 0.4 \text{ V}$$

$$V_{o,avg} = \frac{1}{T} \int_0^T V_o(t) dt$$

$$V_{o,avg} [\text{H/LW, W/LC capacitor}] = \frac{V_m}{\pi} - \frac{V_{o0}}{r}$$

(a) H/LW

(b) W/LC

(c) W/LW

(d) L/LC

(e) L/LW

(f) L/WC

(g) W/WC

(h) W/WL

(i) W/LC

(j) L/WL

(k) L/WC

(l) W/WL

(m) L/WL

(n) L/WC


(o) W/WL

(p) L/WL

(q) L/WC

(r) W/WL

filtering: full-wave rectifier

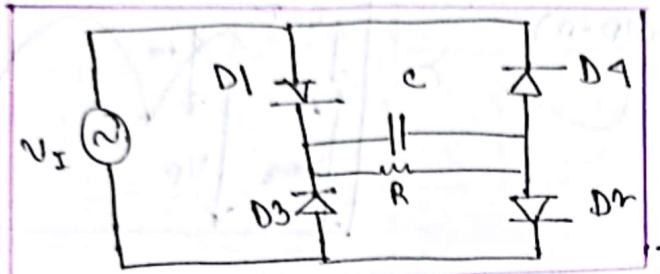


$$V_{o, \text{avg}} = \frac{1}{T} \int_0^T V_o(t) dt$$

$$V_{o, \text{avg}} [\text{F/}\omega, \omega/0 \text{ capacitor}] = \frac{2V_m}{\pi} = 2V_{D0}$$

$$V_{o, \text{avg}} [\text{with capacitor } H/\omega \text{ & } F/\omega] = V_p - \frac{V_p (P-P)}{2}$$

For half-wave rectifier

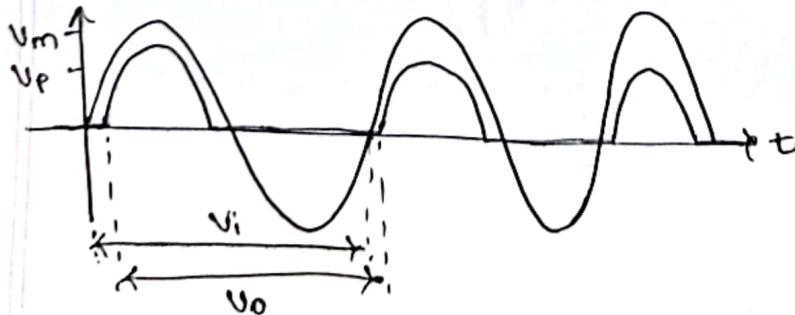


H/ω

$$T_0 = T_i$$

$$\Rightarrow \frac{1}{T_0} = \frac{1}{P_i}$$

$$\Rightarrow f_0 = f_i$$

For full-wave rectifier

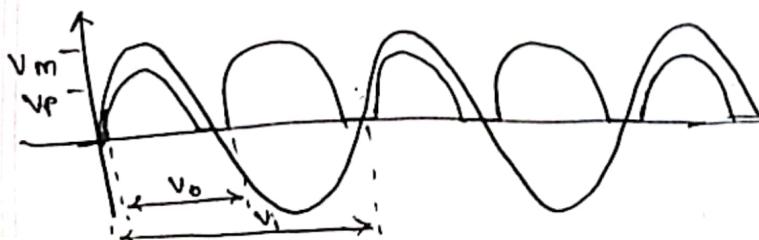

F/ω

$$T_0 = \frac{1}{2} T_i$$

$$\Rightarrow \frac{1}{T_0} = \frac{1}{2P_i}$$

$$\Rightarrow f_0 = 2f_i$$

* with/without capacitor, frequency relationship remains same.


$$* V_i = 10 \sin(2\pi f_i t)$$

$$V_i = V_m \sin(2\pi f_i t)$$

$$\therefore V_m = 10, V_i = 10 \sin(2\pi \cdot 120 t)$$

$$V_i = V_m \sin(2\pi f_i t) \quad \text{ideal formula}$$

↓
peak
voltage
of input

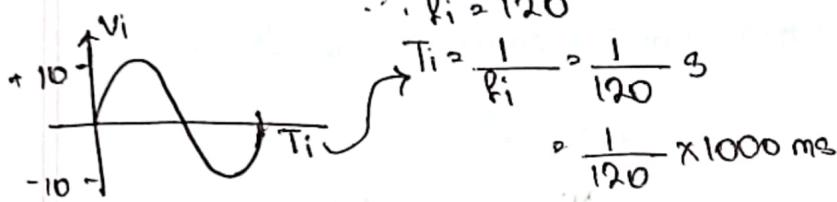

$$\therefore f_i = 120$$

$$T_i = \frac{1}{f_i} = \frac{1}{120} \text{ s}$$

$$= \frac{1}{120} \times 1000 \text{ ms}$$



$$(i) V_o = V_p \sin(240\pi t) \rightarrow \text{Half-wave rectified} [f_o = f_i \Rightarrow 120 = 120]$$

$$(ii) V_o = V_p \sin(480\pi t) \rightarrow \text{full-wave rectified} [f_o = 240, f_i = 120, f_o = 2f_i]$$

$$(iii) V_o = V_p \sin(40\pi t) \rightarrow \text{normal wave} [H(\omega), H(\omega) \text{ or } f(\omega)]$$


* To check whether a curve is half-wave rectified or full-wave rectified, we can check its f_o and f_i .

$$* I_{avg} = \frac{V_{oavg}}{R}$$

Example (from slide)

$$V_i = 8 \sin(2000\pi t)$$

(a)

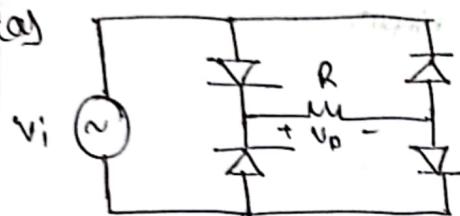

$$V_i = V_m \sin(2\pi f t)$$

$$\therefore V_m = 8 \text{ V}$$

$$V_p = V_m - 2V_{D0}$$

$$= 8 - 2(0.7)$$

$$= 6.6 \text{ V}$$

$$\text{Q3 } V_{o,\text{avg}} = \frac{2V_m}{\pi} - 2V_{D0}$$

$$= \frac{2(8)}{\pi} - 2(0.6)$$


≈

(38.57 V) in 800 x 10^-3

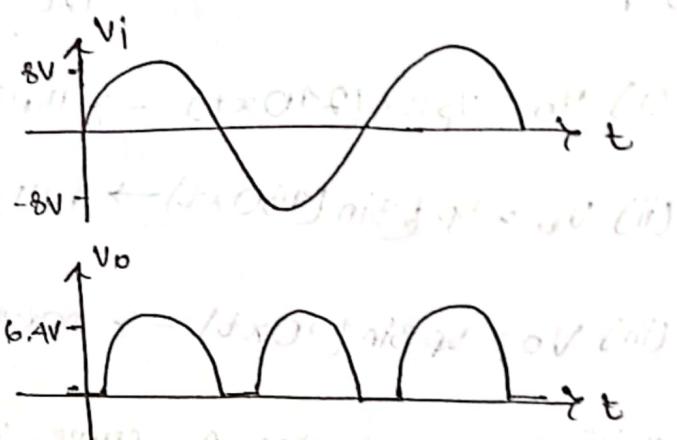(38.57 V) in 800 x 10^-3

∴ Output voltage is 6.6 V in a pulsating form.

∴ Output voltage is 6.6 V in a pulsating form.



∴ Output voltage is 6.6 V in a pulsating form.

$$V_i = 10 \sin(240\pi t) \rightarrow H/W \quad V_o = V_p \sin(240\pi t)$$

Since f_o and f_i are same, H/W is used.



$$(i) \text{ Peak output voltage} = V_p = V_m - V_{D0} = 10 - 0.7 = 9.3 \text{ V}$$

$$(ii) \text{ Peak diode current} = \text{Peak output current} = \frac{V_p}{R} = \frac{9.3}{10} = 0.93 \text{ mA}$$

$$(iii) \text{ Output frequency} = 120 \text{ Hz}$$

$$(iv) \text{ Average value of the output voltage} = \frac{V_m}{\pi} - \frac{1}{\pi} V_{D0}$$

(v) Sketch the Output and input voltage

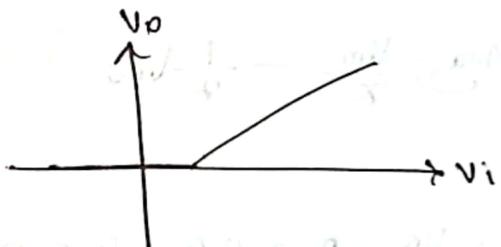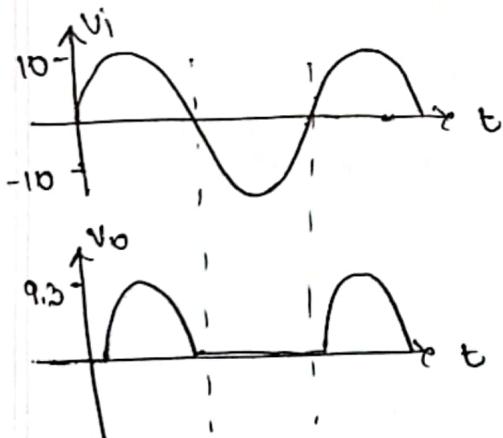



[For Transfer characteristics]

(dx 4.8) Neglect ω_0 with respect to ω (approximate)

Question 4

(a) First step of converting AC to DC.

Negative half cycle of input is removed.

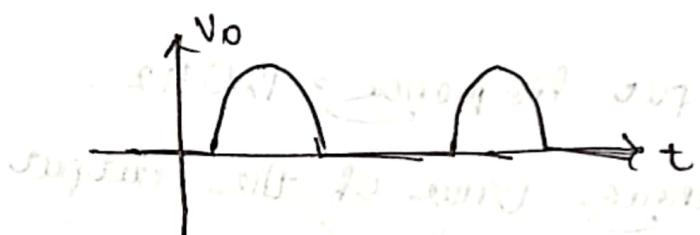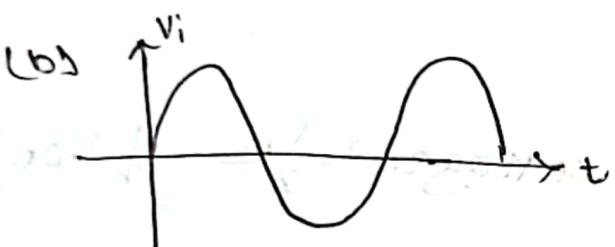

$$(c) V_{o, \text{avg}} = \frac{V_m}{\pi} - \frac{1}{2} V_{D0}$$

$$(d) V_D = \frac{V_D}{2} \times 2 = 0.2 \times 2 = 0.4$$

$$V_D = \frac{V_P}{R_C}$$


$$\Rightarrow C = \frac{V_P}{R_C R V_D}$$

$$= \frac{V_m - V_{D0}}{R_C R V_D}$$


Quiz 2 Solution:

$$(1) V_{DD} = 0.6 \text{ V}$$


$$R_D = 0.6 \text{ k}\Omega$$

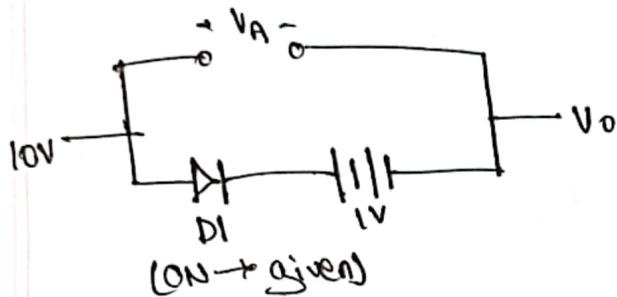

CVD:

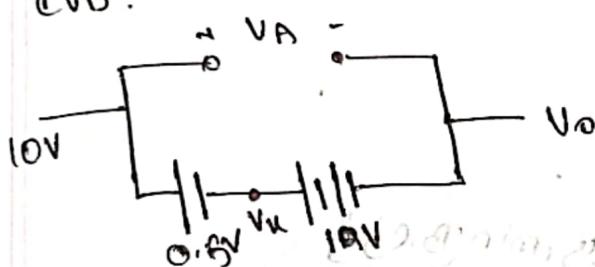

CVD + R:

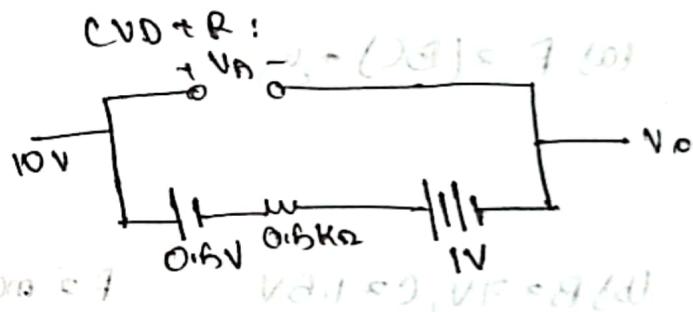


$$0.6 = 10 - V_{A1} \Rightarrow V_{A1} = 9.4 \text{ V}$$

$$1 = V_{A1} - V_O \Rightarrow V_O = 8.6 \text{ V}$$

$$\therefore V_A = 10 - V_O = 10 - 8.6 = 1.4 \text{ V}$$




(2)

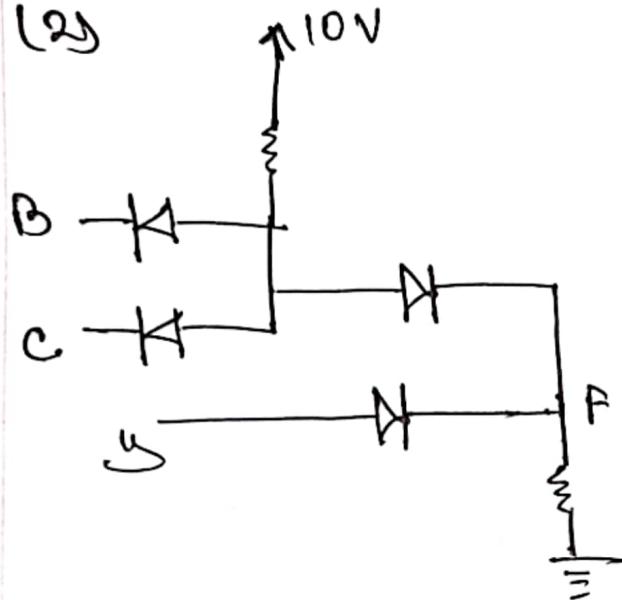


$$V_{AD} = 0.7V \text{ (I)}$$

$$0.8V < 0 < 0.9V$$

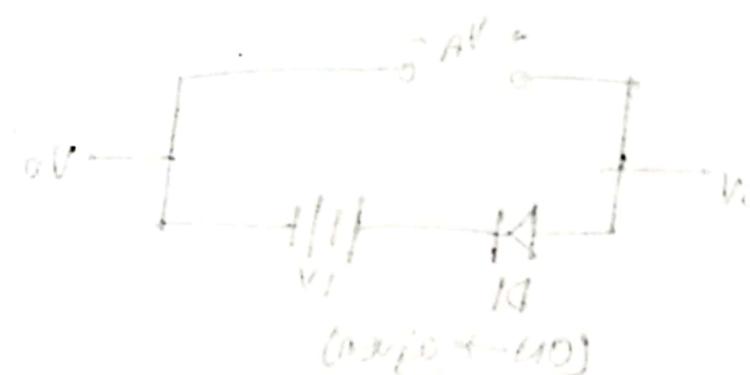

$$(a) F = (B, C) + g$$

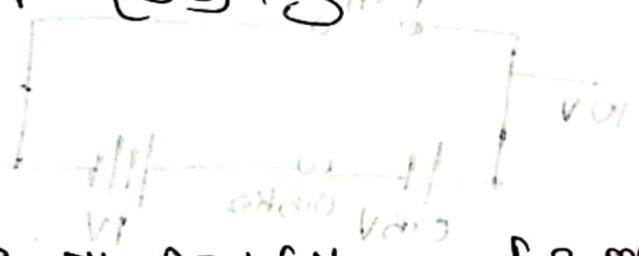


$$(b) B = 7V, C = 1.6V$$

$$F = \max(g, \min(B, C))$$


$$\text{Here, } \min(B, C) = 1.6V = 0.0$$

$$6.0 - 0.7 \text{ of } 6V = 5.3V = 1$$
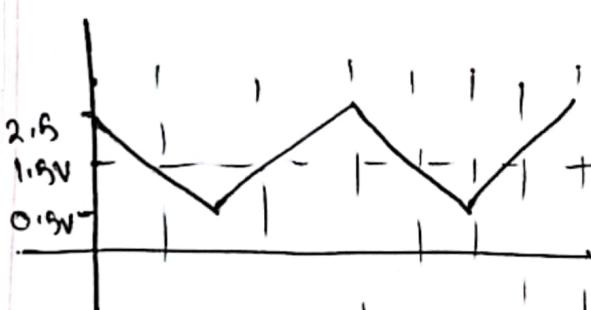
$$6.0 - 0.7 - 0.0 = 5.3 - 0.0 = 5.3V = 0.0$$





$$1.6V = \min(B, C)$$

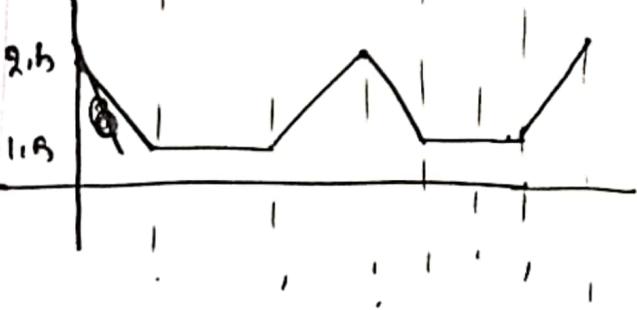


FINAL




ZENER DIODE

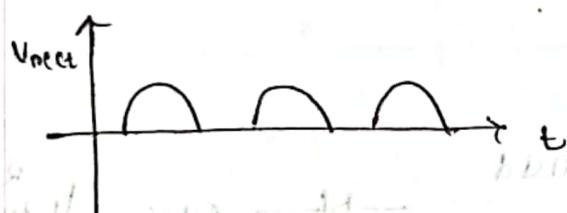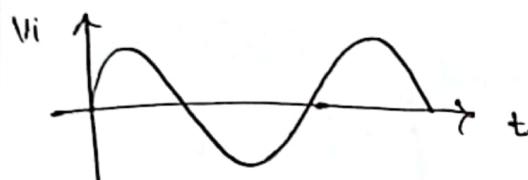


Invertor load & diff. output

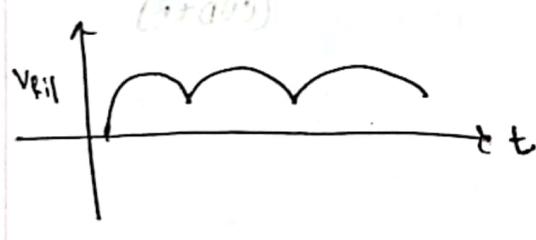




Invertor load & diff. output

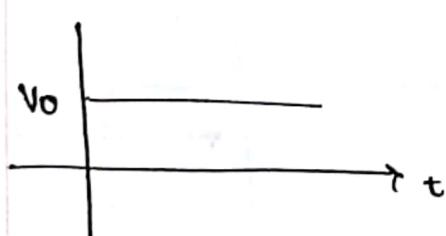


Invertor load & diff. output

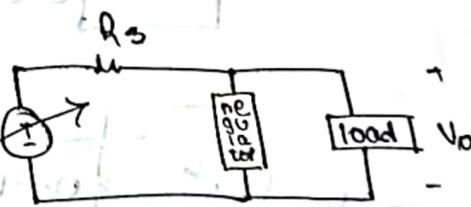




*Regulator

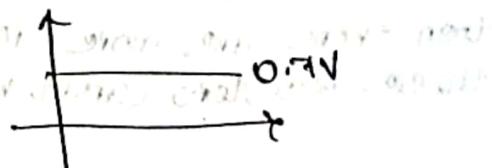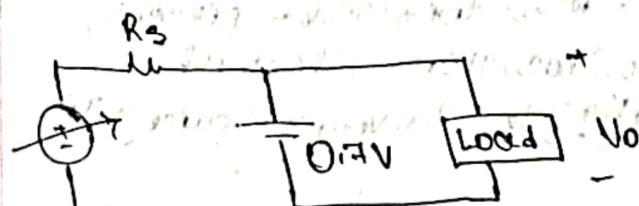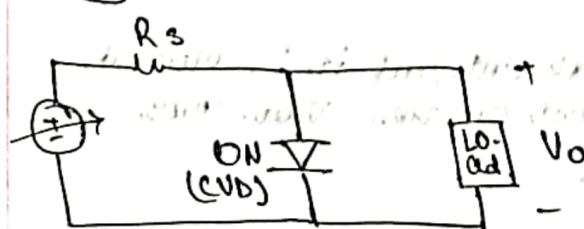

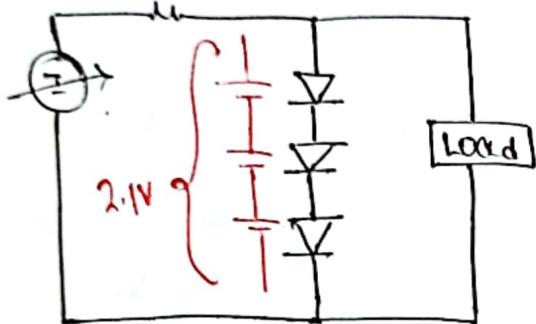

- ① Voltage values are limited
- ② R_2 can't be ignored if we add multiple diodes.


$$R_2 = 0.01 \text{ k}\Omega$$

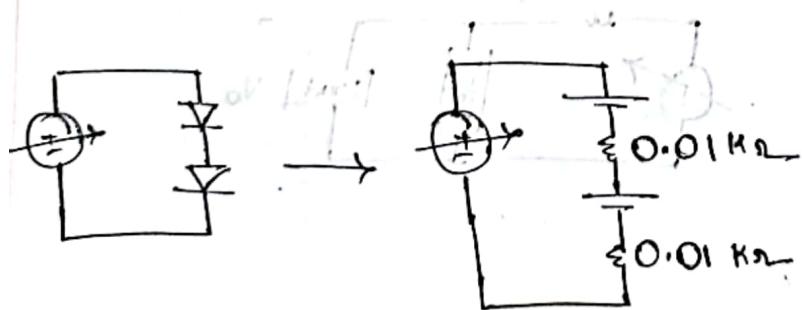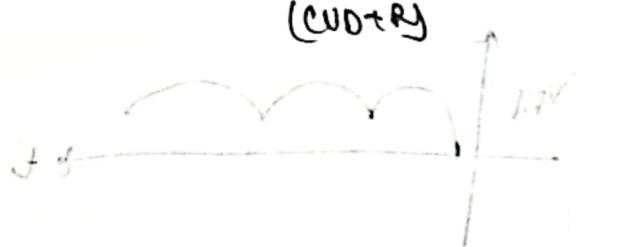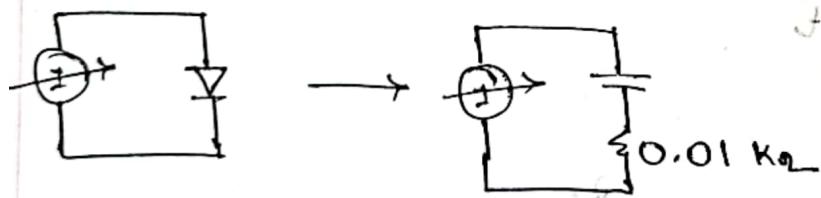

* If there is only one diode present, and it is closed, resistor does not have any effect on the V_{out} . Thus, $V_{out} = V_{source}$


* If there are more than one diodes present, then there are more resistors. Thus, the effect of these resistors cannot be negligible. So, $V_{out} = V_{source} + I_R$

* Zener Diode (Special type of diode)

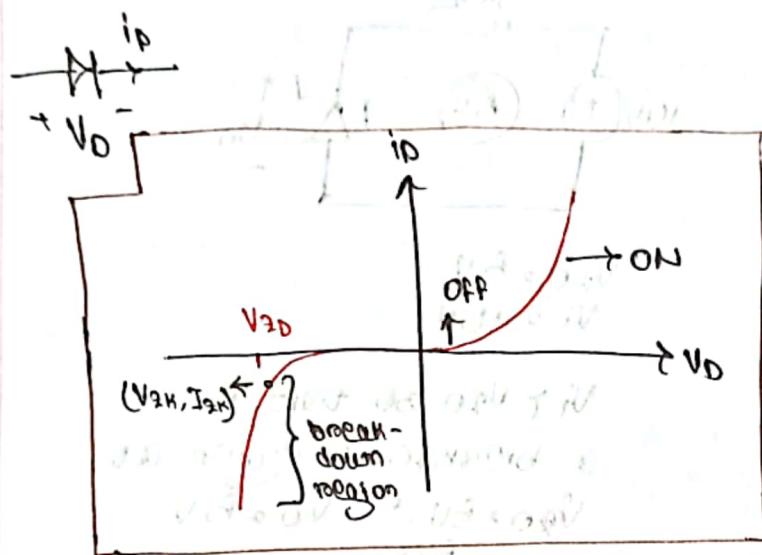

$V_{ZK} \rightarrow$ knee voltage

$i_{ZK} \rightarrow$ knee current

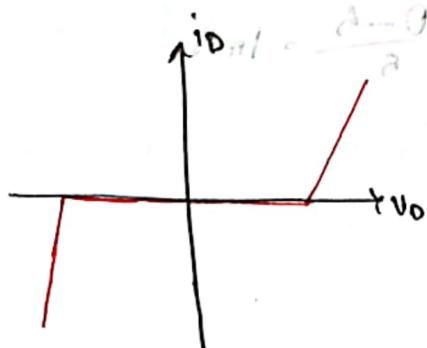

ON: $i_D \gg 0$

OFF: $V_{ZK} < V_D \leq V_{D0}$

BR: $i_D \approx -i_{ZK}$

for zener diode,


for normal diode,

piece-wise linear model,

and its two regions

• linear model of

$5k\Omega$

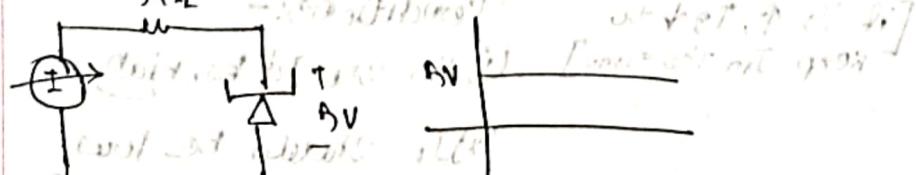

for Zener diode









$$\begin{aligned} V_Z &= V_{Z0} + i_D R \\ i_D &= i_{Z0} + i_D \end{aligned}$$

* breakdown region
 A_2 slope, $i_D = 0$
* zener diode is used
 for breakdown region.

* we use zener diode, if
 we need the breakdown
 region.


for normal diode,

$i_D = 0$

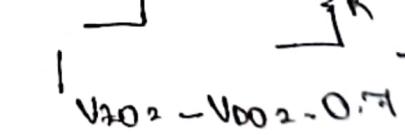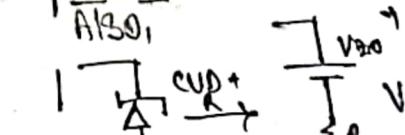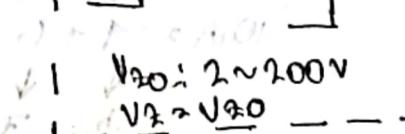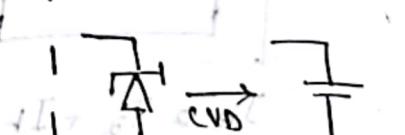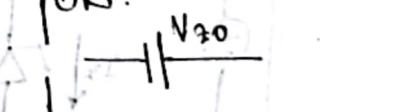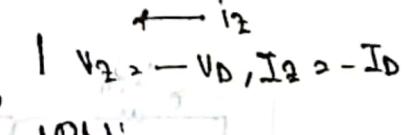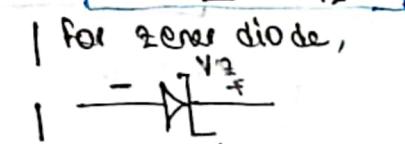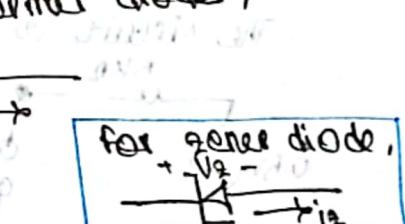

$$\begin{aligned} V_{Z0} &= V_{D0} = 0.7 \\ V_Z &= V_{Z0} + i_D V_R \\ V_Z &= V_{D0} + i_D V_R \end{aligned}$$

Ex 1:

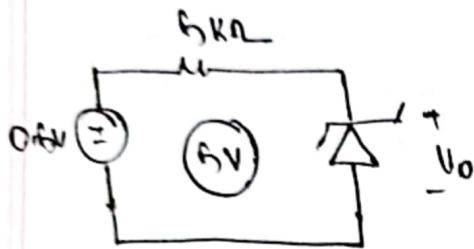


$$V_{20} = 5V$$

$$V_i = 0.5V$$

$V_i < V_{20}$, so it does not reach breakdown. The circuit is open.




Ex 2:

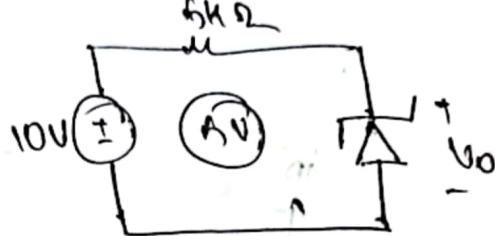


$$V_{20} = 5V, V_i = 10V$$

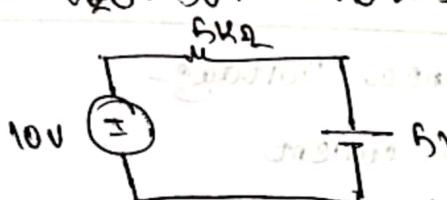$V_i > V_{20}$, so there is a breakdown region at $V_{20} = 5V$. $V_o = 5V$



$$I_2 = \frac{10 - 5}{5} = 1mA$$

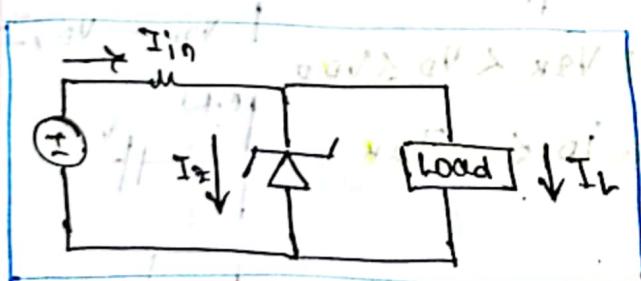

$$I_{in} = I_2 + I_L$$

$$10mA = 1 + 6$$

$$V_{20} = 5V \rightarrow I \downarrow \rightarrow I_L \downarrow \rightarrow I_2 \downarrow$$

[if $I_L \uparrow$, $I_2 \downarrow$ to keep I_{in} the same]

For regulator to work properly, Zener MUST be in breakdown region.

Conditions:-


(1) V_{in} should be high

(2) I_{in} should be low

(3) $I_2 \geq I_{in}$

$[V_{in} \uparrow \rightarrow I_2 \uparrow, I_L \uparrow \rightarrow I_2 \downarrow]$

Op-amp circuit analysis

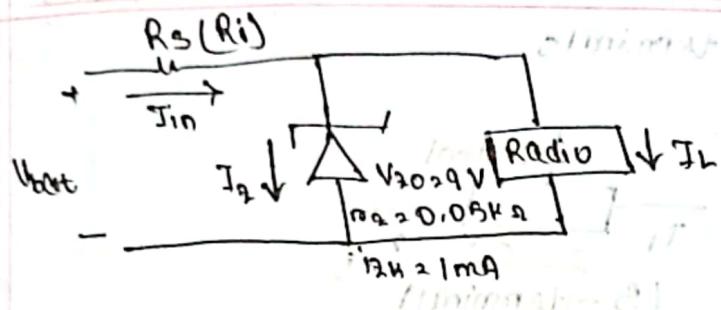

for worst case scenario,



- (1) $V_{in} = V_{in}(\text{MIN})$
- (2) $I_L = I_L(\text{MAX})$
- (3) $I_2 = I_2(\text{MIN}) = I_{2K}$

Radio requires $\approx 9V$

V_{out} : between 11 to 13.6 V

I_L : between 0 to 9 mA

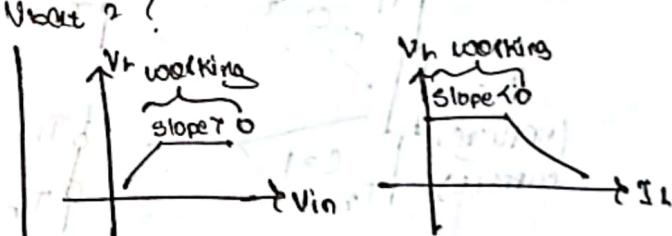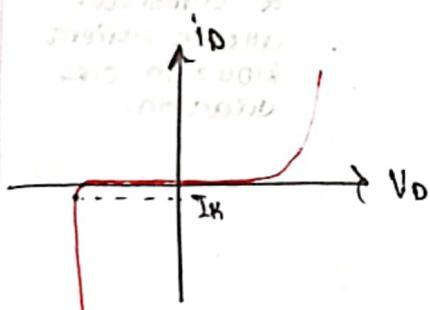At worst case, calculate $I_2, I_L, V_2, V_{out} = ?$



Soln: At worst case, $I_2 = I_{2,\text{min}}$

$$= I_{2K}$$

$$= 1 \text{ mA}$$

(from graph)

$$\text{line regulation} \quad \frac{\Delta V_L (\text{mV/V})}{\Delta V_{in} (\text{mV/V})}$$

$$\text{load regulation} \quad \frac{\Delta V_L (\text{mV/mA})}{\Delta I_L (\text{mV/mA})}$$

$$2. \quad \frac{R_2}{R_1 + R_2} \quad 2. \quad \frac{R_2 R_1}{R_1 + R_2}$$

$$V_{out} = 11V$$

$$\text{CVD: } \frac{V_2}{1}$$

$$\text{CVD} + R_1: \frac{V_2}{1 + \frac{R_2}{R_1}}$$

$$V_2 = V_{20} + I_2 R_2$$

$$V_2 = 9 + (1 \times 0.05)$$

$$V_2 = 9.05 \text{ V}$$

$$I_{in} = \frac{V_{out} - V_2}{R_1}$$

$$\begin{aligned} V_2 &= I_{in} \times R_1 \\ &= 10 \times 0.195 \\ &= 1.95 \text{ V} \end{aligned}$$

Op-amp characteristics: V-I



$$I_L = 9 \text{ mA}$$

$$I_{in} = I_2 + I_R$$

$$I_{in} = 10 \text{ mA}$$

$$I_{in} = \frac{V_{out} - V_2}{R_1} = 10 = \frac{11 - 9.05}{R_1}$$




LECTURE

19

MONDAY

DATE: 27/03/2023

* Transistor: circuit with 3 terminals

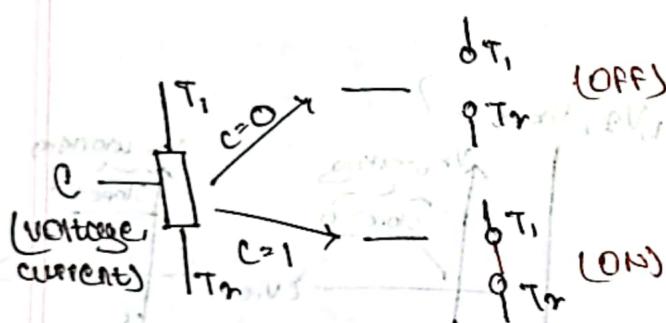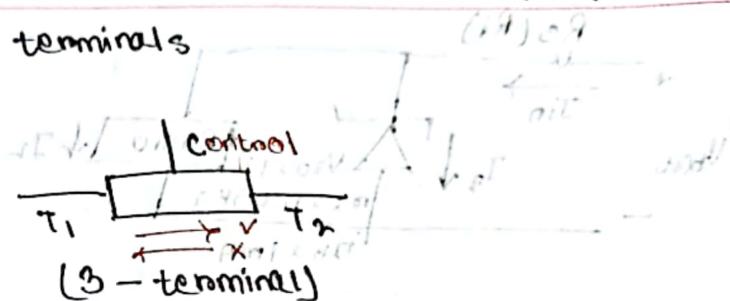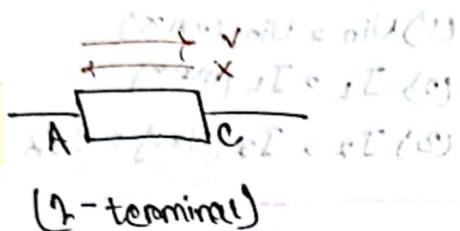

* Control terminal is used to control flow betw. T_1 & T_2 & T_3

* Both diode & transistor allows current flow in one direction.


Application

* As a switch

* As an amplifier $I_{O,V} \rightarrow I_{A,V}$

* As logic gates

I-V characteristics

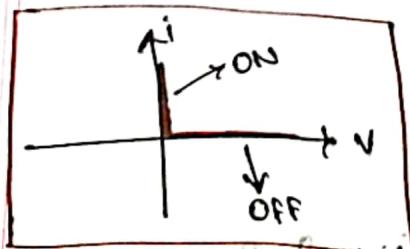

at $V=0$ $I=0$

at $V > 0$ $I \neq 0$

at $V < 0$ $I = 0$


at $V < 0$ $I \neq 0$

VII = work

OFF

ON


OFF

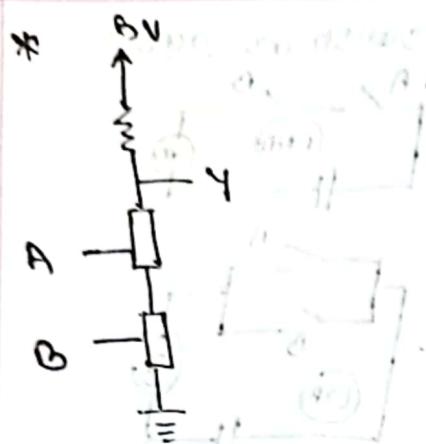

A	B	Y
0	0	5V \rightarrow 1
0	1	5V \rightarrow 1
1	0	5V \rightarrow 1
1	1	0V \rightarrow 0


NAND GATE

$$Y = \overline{A \cdot B}$$

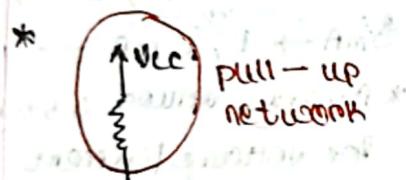


inverts the logic below

* AND [NAND + NOT]

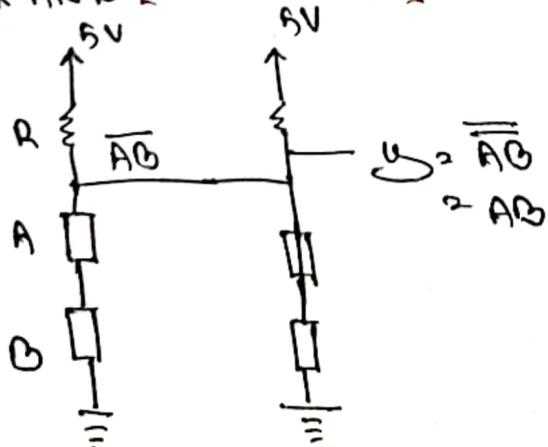

* NOR [NOR + NOT]

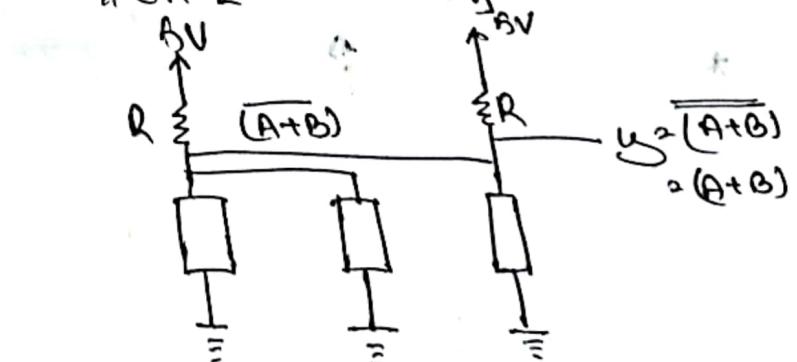


* Transistor

→ MOSFET (Control = V)


→ BJT (Control = I)

* MOSFET :




Symbol:

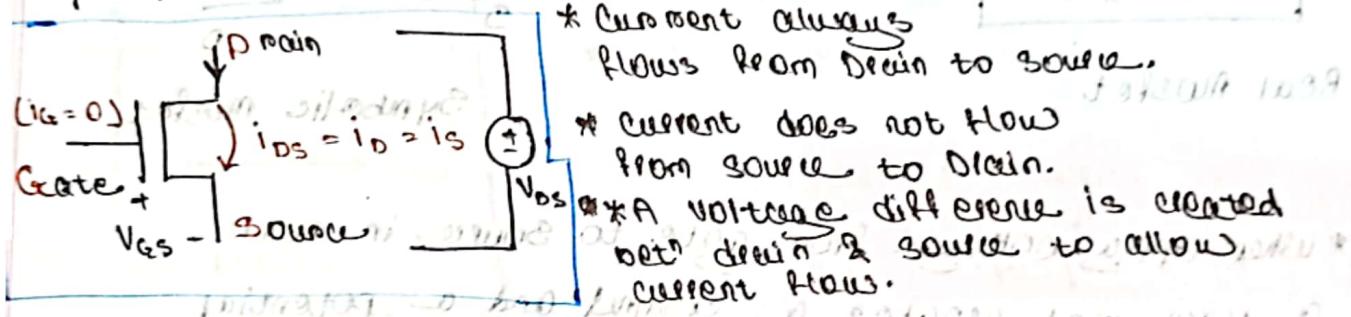


* NOT Gate

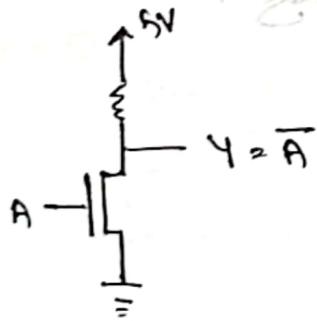

* i - V characteristics of mosfet

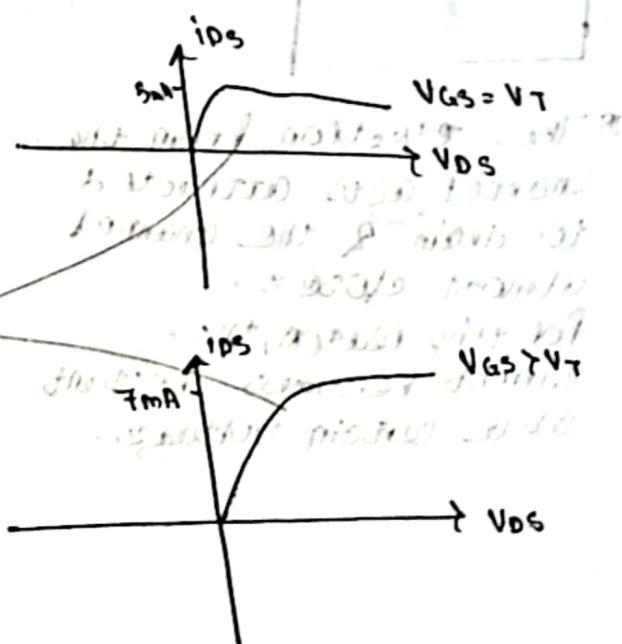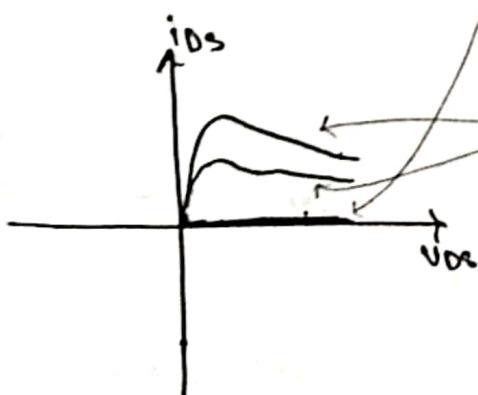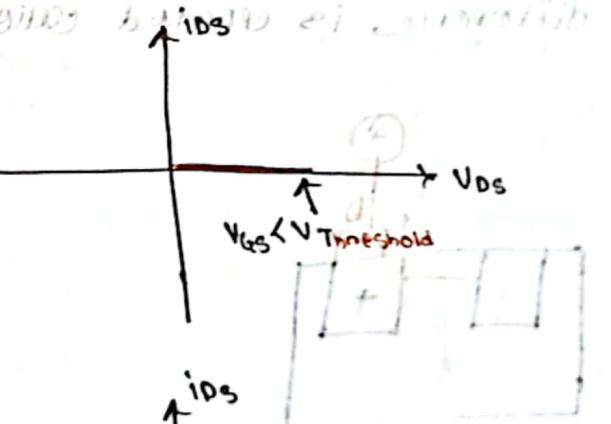

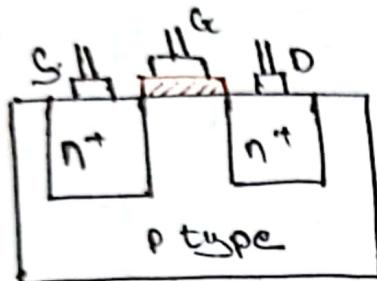
metal
 ↑ semi-conductor
MOSFET
 ↓ field ↓ transistor
 oxide effect



How does a mosfet works? } Function
 of Transistor }
 (1) \rightarrow (2) \rightarrow (3)

$n \rightarrow e^-$ electron
 $p \rightarrow e^-$ hole

currents increase

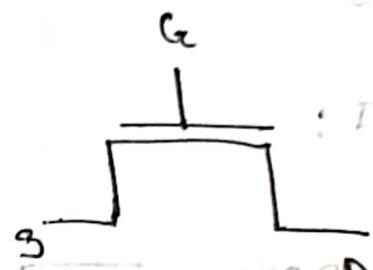

1. Field Effect

2. Back bias

3. Output

Symbolic mosfet


$V_{GS} = 0V$

Real mosfet

Earth the gate terminal to
anode of Zener diode

* When apply voltage from gate to source in such

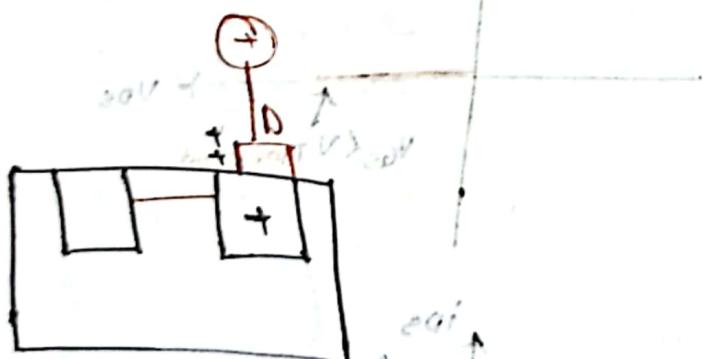a way that creates a channel and a potential
difference is created called "threshold voltage".



* The electron from the
 channel gets attracted
 to drain & the channel
 almost closes.
 For this reason, the
 current becomes constant
 at a certain voltage.



MONDAY

DATE: 03/04/23



VOLTAGE TRANSFER CHARACTERISTICS

$V_{GS} < V_T \rightarrow \text{OFF}$
(0)

$$V_O = V_{GS} - V_T \rightarrow 0$$

$V_{GS} \geq V_T \rightarrow \text{ON}$
(1)

$$V_O = V_{GS} = 0V \rightarrow 0$$

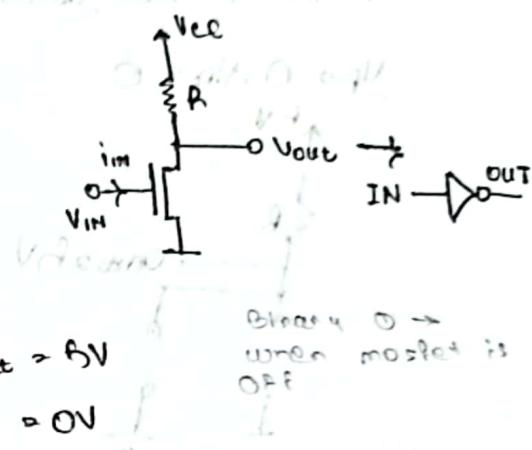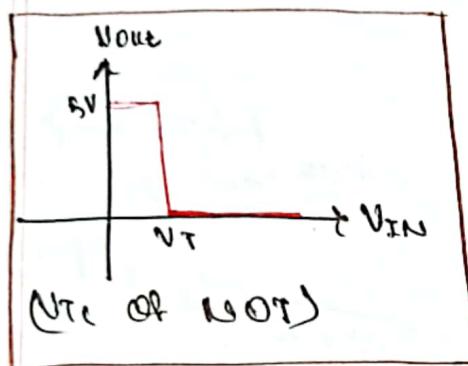


* $V_{GS} < V_T \rightarrow V_{out} = 5V$

* $V_{GS} \geq V_T \rightarrow V_{out} = 0V$


AND: $A \bar{B}$ | NAND: $\bar{A} \bar{B}$
OR: $A + B$ | NOR: $(A + B)$
XOR: $\bar{A}B + A\bar{B}$ | XNOR: $AB + \bar{A}\bar{B}$

* VTC of NAND:


$$V_A = 0$$

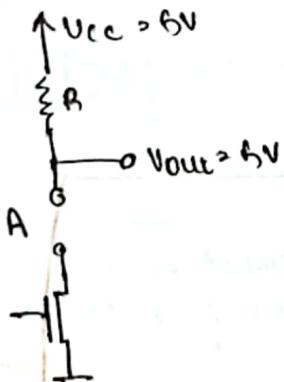


$$V_A = 0$$

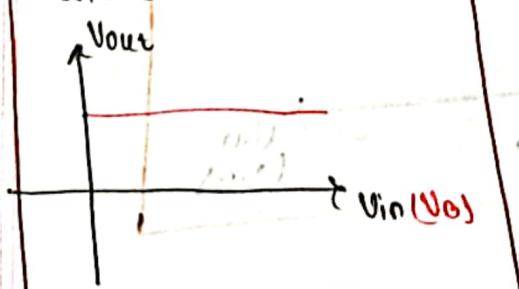


$$V_A = 1, V_B = 0$$

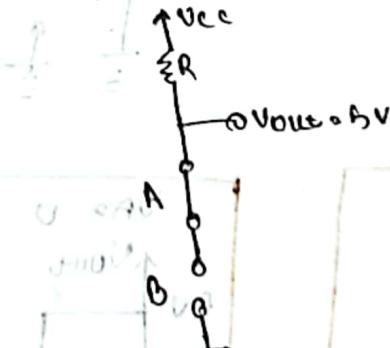

$$V_A = 1$$

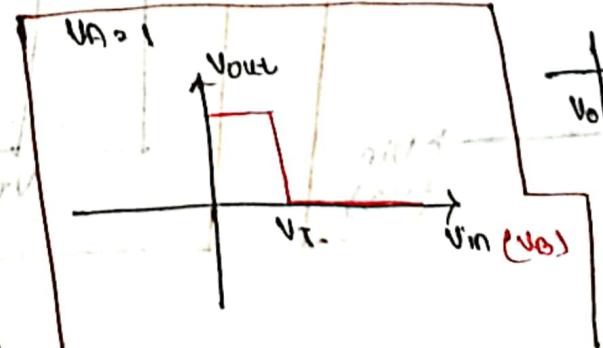

$$V_A = 1, V_B = 1$$

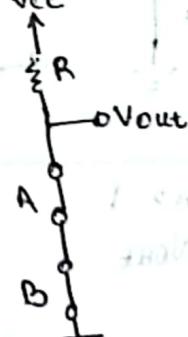

VA	VB	Vout
0	0	1
0	1	1
1	0	1
1	1	0


* When $V_A = 0$, no current flows through A & B

Op-amp circuit


Part 2

* VTC for NOR gate


VA_A = 0, VB = 0

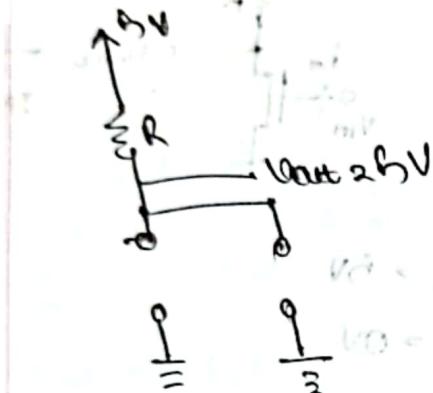


VA_A = 0, VB = 1

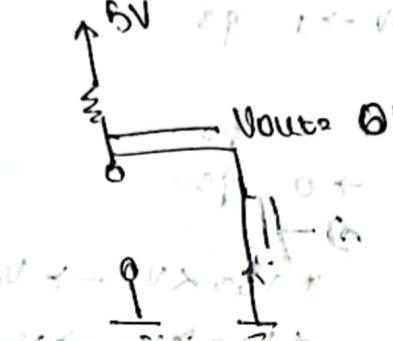


VA_A = 1, VB = 1

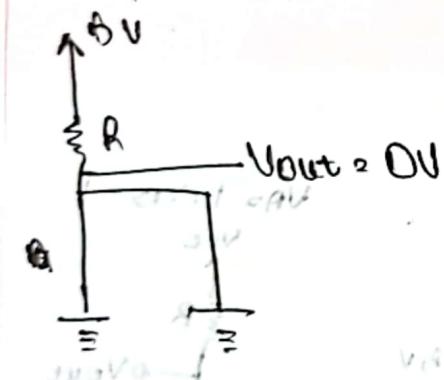


VA_A = 1, VB = 0

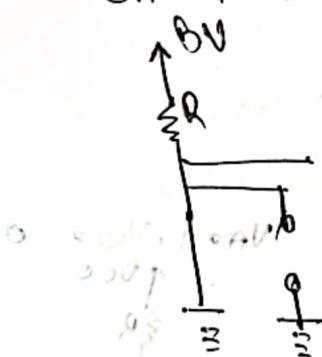


VA_A = 1

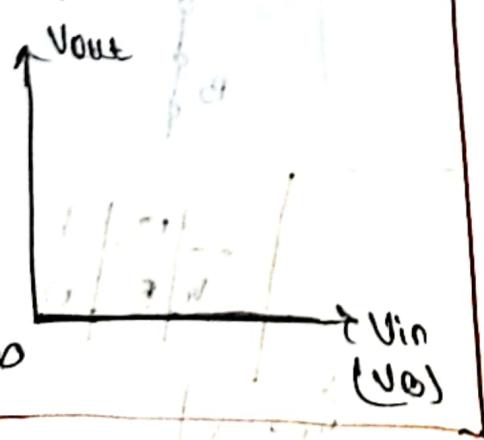


VA_A = 0

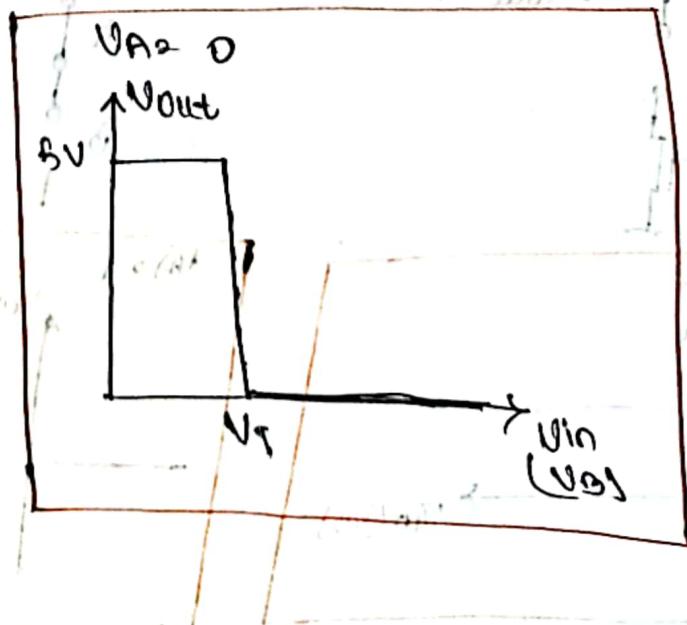


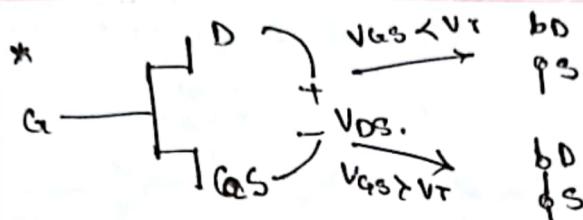
Part 2, Q3 part 2
Ground truth frame
at a a



[S-Model]

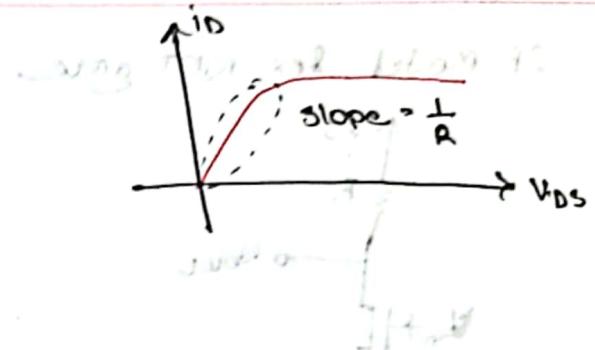

S-R model

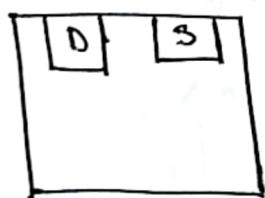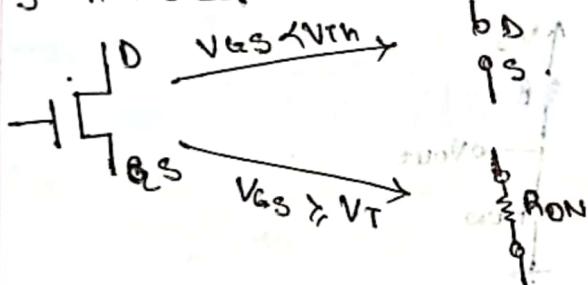

The distance between D & S in real mos fet is h and the width is W .

$$RON = \frac{1}{K'n \frac{W}{h} (VGS - VT)}$$

↑ process transconductance

$$RON = \frac{1}{K'NOV}$$



$$K = K' \frac{W}{L}$$

$$NOV = VGS - VT$$

(overdrive)


$VGS = \frac{VGS}{VDS}$ < VDS

SR model for NOT gate

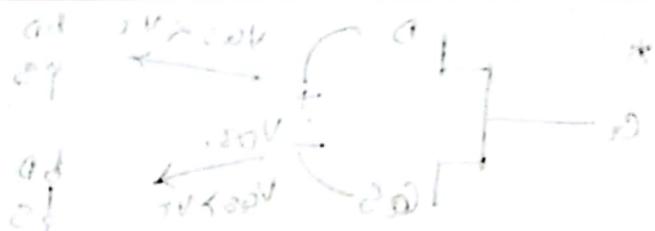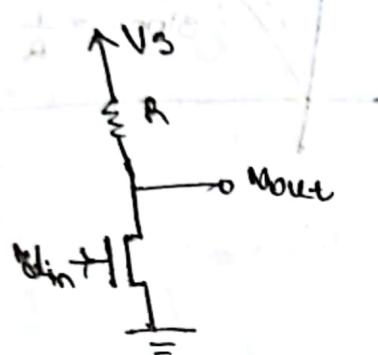


[Ind. 0.7 - 0.1]

$V_{GS} \approx V_T$

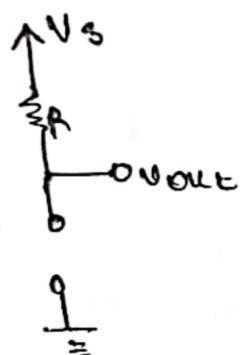


$V_{out, high} = 2.5V$

$NMOS \approx NMOS$

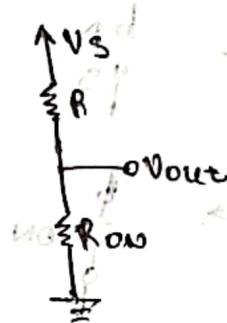

Ind. 0.7 - 0.1
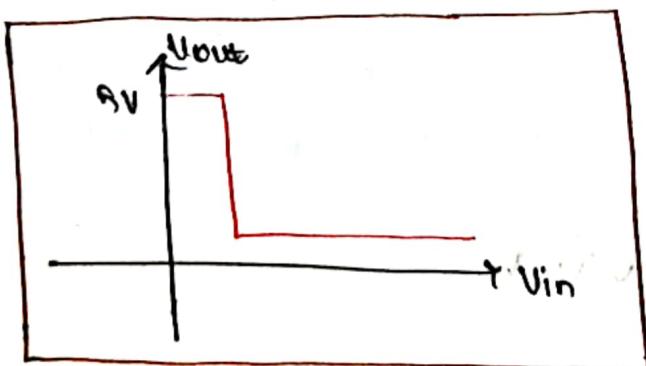
$$V_{out, high} = \frac{V_s R_{on}}{R_{on} + R_h} + 0$$



0.000192 - 0.000200 2.5
0.000192 - 0.000200 0.000200 0.000200
0.000192 - 0.000200 0.000200 0.000200

poly 800

1.2 analog


1.2 analog

0.000200

0.000200 0.000200

0.000200 0.000200

DESIGN OF LOGIC GATES

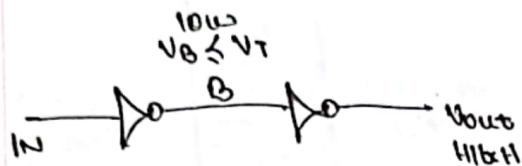

HIGH
 $[V_{IN}, V_T]$


Condition for designing logic gates:

$V_B = \frac{V_{DOL}}{R_{ON} + R_L}$ must be smaller than V_T

$$\text{than } V_T \quad \left[\frac{V_{DOL}}{R_{ON} + R_L} < V_T \right]$$

$$R_{ON} = \frac{1}{K' \frac{W}{L} (V_{DOL} - V_T)} = \frac{1}{K' \frac{W}{L} V_{DOL}}$$

QUESTION:

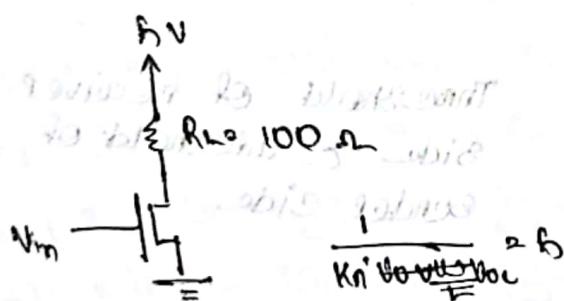

$$V_T = 1V$$


$$R_{ON} \leq 2.5$$

$$R_{ON} = \frac{1}{K' \frac{W}{L} (V_{DOL})} \leq 2.5$$

$$\Rightarrow \frac{W}{L} \leq 2.5$$

$$\Rightarrow \frac{W}{L} \geq \frac{5}{2.5} = 2$$

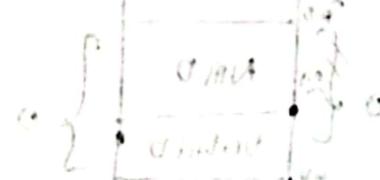
$$\therefore \frac{W}{L} \geq 2 \text{ nm} \rightarrow \text{let } L = 2 \text{ nm}, W = 8 \text{ nm}$$



DIGITAL REPRESENTATION


$$0 \rightarrow 2.5V \textcircled{0}$$

$$2.5 \rightarrow 5V \textcircled{1}$$

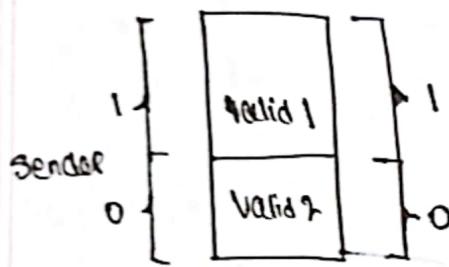


receiver

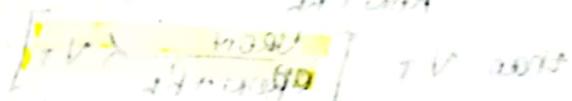single digital threshold not modified
volume and form must be good




Double threshold based system

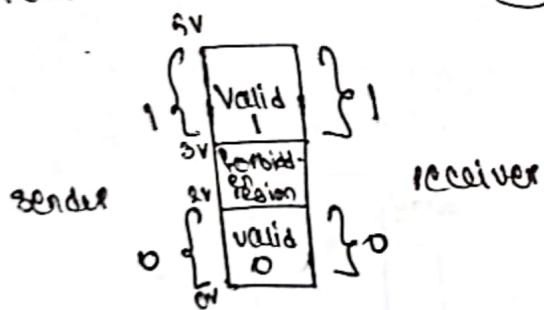

receiver

threshold of receiver
side & threshold of
sender side

Four threshold based system

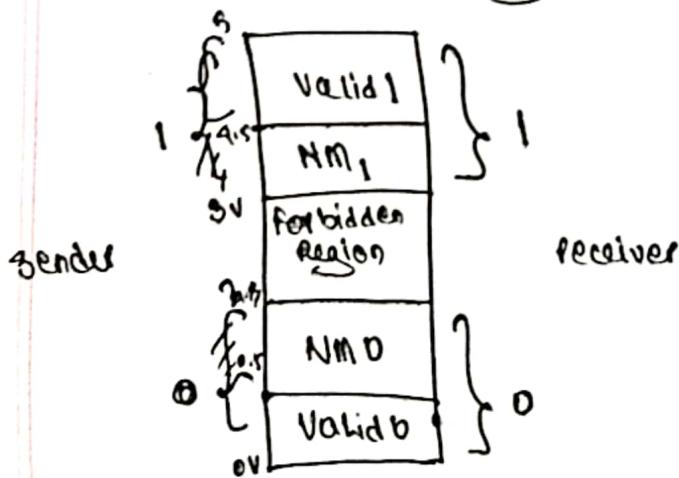

receiver

no threshold



$$V_{OH} = 0.5V$$

$$V_{OL} = 4.5V$$

- * The sender is taken as output and the receiver is taken as input.
- * The input receiver provides the input voltage.

STATIC DISCIPLINE

* V_{OH} & V_{OL} do not change with time, so it falls under static discipline.

V_{OH} = output high voltage threshold

V_{OL} = output low voltage threshold

V_{IH} = input high voltage threshold

V_{IL} = input low voltage threshold

Noise Margins



$$NM_1 = V_{OH} - V_{IH}$$

$$NM_0 = V_{IL} - V_{OL}$$

$$V_{OL} < V_{IL} < V_{IH} < V_{OH}$$





Mosfet

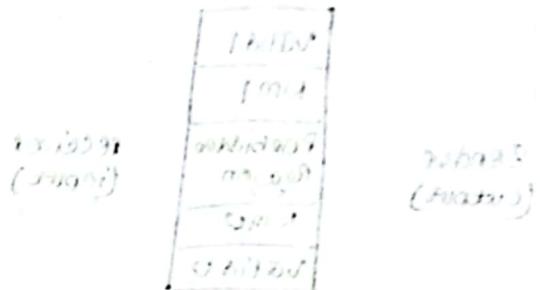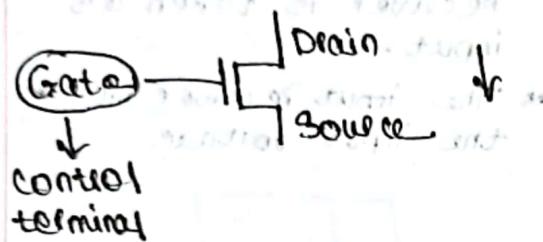


$V_{GS} < V_{th}$ \rightarrow b_0 (OFF)
 q_s

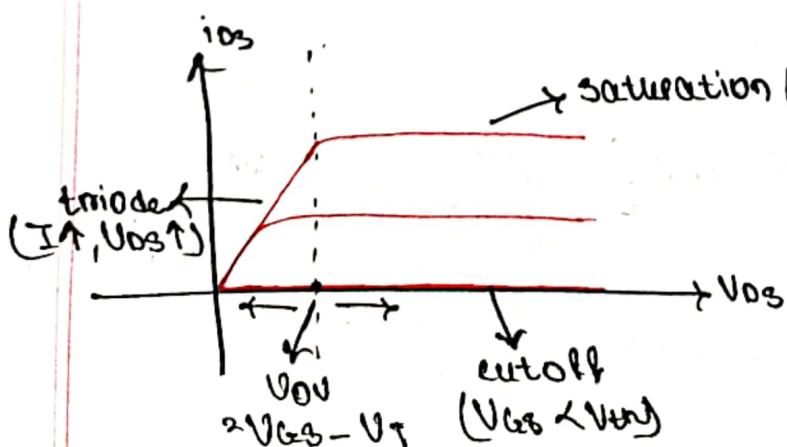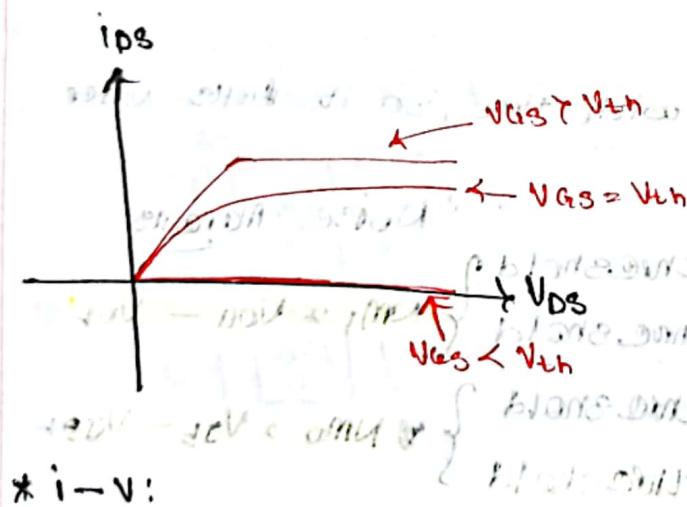$V_{GS} > V_{th}$ \rightarrow b_0 (ON)
 q_s




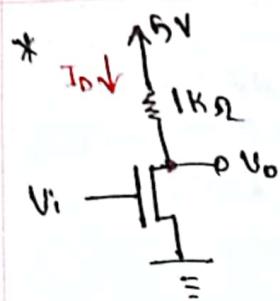\hookrightarrow At this point, RHS \rightarrow saturation
 " " LHS \rightarrow triode



$$I_D = ?$$

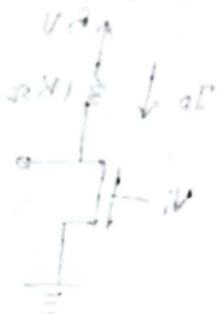Given: $V_D = 15V$, $R_D = 1k\Omega$, $V_g = 0V$, $V_T = 0V$



* Cutoff: $V_{GS} < V_{th}$, $I_D = 0$

Below threshold to cutoff

* triode: $I_D = K \left[V_{GS} V_{DS} - \frac{1}{2} V_{DS}^2 \right]$, $V_{GS} \geq V_T$, $V_{DS} \geq V_{OV}$

$$K = K_n \frac{W}{L} \quad \text{Unit: mA/V}^2$$

→ process trans-conductance

V_{OV} = overdrive voltage [drain at source

threshold voltage, $V_{DS} = V_{DSsat}$]

* $V_{th} = 1V$

$V_{GS} = 0.8V \rightarrow \text{OFF}$

$V_{GS} = 0.9V \rightarrow \text{OFF}$

$V_{GS} = 1V \rightarrow \text{ON}$

$V_{GS} = 1.8V \rightarrow \text{ON}$

$$V_{OV} = V_{GS} - V_{th} = 1.8 - 1 = 0.8V$$

* saturation: $V_{GS} \geq V_{th}$, $V_{DS} \geq V_{OV}$

$$I_{DS} = \frac{1}{2} K V_{GS}^2$$


for MOSFET, find assumption using saturation at first.

Assumption: $V_{DS} = V_{DSsat}$

$$V_D = V_{DS} + V_{DSsat} = V_{DS} + \frac{2V}{L} \cdot \frac{W}{L} \cdot V_{GS}^2$$

$$V_D = V_{DS} + 2V$$

$$V_{DS} = V_D - 2V$$

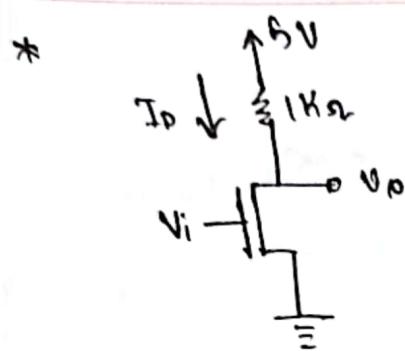

* $I_D = ?$

* $V_D = ?$

Given,

$$K = 0.1 \text{ mA/V}^2$$

$$V_{TH} = 1V$$

$$(i) V_i = 2V, (ii) V_i = 5V$$



Detail, Additional Data *

Method of assumed state:

Step 1: Assume ~~Vi = 2V~~, $V_{DSL} = 0V$ $\Rightarrow I_D = 0A$: Assume

Step 2: Solve

$$V_{DSL} = 0V \Rightarrow I_D = 0A$$

Step 3: Verify

$$(i) V_i = 2V$$

* Soln: Let the Mosfet is in saturation region $\Rightarrow V_D = 0V$

$$\therefore i_{DS} = \frac{1}{2} KV_{DS}^2$$

$$\begin{aligned} V_{DS} &= V_{DS} - V_{TH} = (V_G - V_i) - V_{TH} \\ &= (V_i - 0) - 1 = V_i - 1 \\ &= (2 - 0) - 1 = 1V \end{aligned}$$

$$V_{DS}^2 = 1 - V_D^2 \Rightarrow 1 - 0^2 = 1V^2$$

$$\therefore i_{DS} = \frac{1}{2} KV_{DS}^2$$

you recall, $V_D = 0V$ \Rightarrow ~~saturation region~~

$$= \frac{1}{2} (0.1) (1)^2$$

$$i_{DS} = 0.05 \text{ mA}$$

$$I_D = i_{DS} = 0.05 \text{ mA}$$

$$I_D = \frac{V - V_D}{1} \Rightarrow I_D = V - V_D$$

$$I_D = 5 - V_D$$

$$0.05 = 5 - V_D$$

$$V_D = 4.95V$$

$$\therefore V_D = V_D = 4.95V$$

Here,

$$V_{GS} = V_G - V_S$$

$$= 2 - 0$$

$$= 2 > V_{TH} \dots \dots V_{GS} > V_{TH} \checkmark$$

$$V_{DS} = V_D - V_S$$

$$= 4.75 - 0$$

$$= 4.75 > 1V \dots \dots V_{DS} > V_{DS} \checkmark$$

∴ The assumption is correct.

(ii) $V_i = 5V$

* Solⁿ: let the mosfet is in saturation region

$$i_{DS} = \frac{1}{2} k N V_{DS}^2$$

$$V_{DS} = V_{GS} - V_{TH}$$

$$= (V_G - V_S) - V_{TH}$$

$$= (5 - 0) - 1$$

$$V_{DS} = 4$$

$$\therefore i_{DS} = \frac{1}{2} k N V_{DS}^2$$

$$= \frac{1}{2} (0.15) (4)^2 \cdot 4mA$$

$$V_D = 5 - i_D = 5 - 4 = 1V > V_D$$

$$V_{DS} = V_D - V_S = 1 - 0 = 1V$$

Hence,

$$V_{GS} = V_G - V_S = 5V > V_{TH} \checkmark$$

$$V_{DS} = V_D - V_S = 1V < V_{DS} \checkmark$$

∴ The assumption is incorrect.

let the mosfet is in saturation region

$$i_D = K \left[(V_D - V_{DS}) - \frac{1}{2} V_D^2 \right]^n$$

$$V_{DS} = V_D - V_S$$

$$\Rightarrow V_D - 0 = V_D$$

$$i_D = 0.5 \left[4V_D - \frac{1}{2} V_D^2 \right]$$

$$i_D = \frac{6 - V_D}{1} \Rightarrow 6 - V_D = i_D$$

$$\therefore 6 - V_D = 0.5 \left[4V_D - \frac{1}{2} V_D^2 \right]$$

$$\Rightarrow 10 - V_D = 0.5 \left[8V_D - V_D^2 \right]$$

$$\Rightarrow 10 - V_D = 4V_D - \frac{1}{2} V_D^2$$

$$\Rightarrow \frac{1}{2} V_D^2 - 5V_D + 10 = 0$$

$$\therefore V_D = 2V, 10V$$

$$V_{DS} = V_D - V_S \xrightarrow{V_S = 0} 0$$


$$V_{DS} = V_D$$

$$V_{GS} = V_G - V_S$$

$$= 5 - 1 = 4V \neq V_{TH}$$

$$V_{DS} = 2V, V_{DS} = 1V$$


$$\therefore V_{DS} \neq V_{DS1}$$

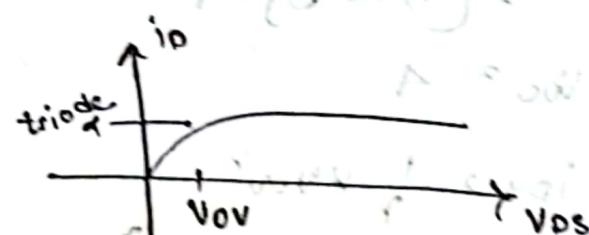

$$V_{GS} \approx V_{TH} \checkmark$$


$$V_{DS} < V_{DS1} \checkmark$$

Q2.7

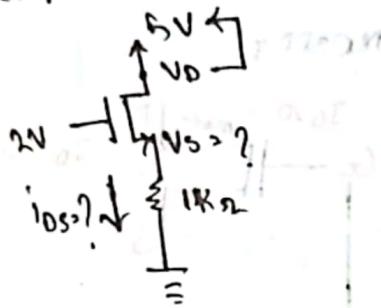

$$K = 4 \text{ mA/V}^m$$

$$V_{TH} = 1 \text{ V}$$

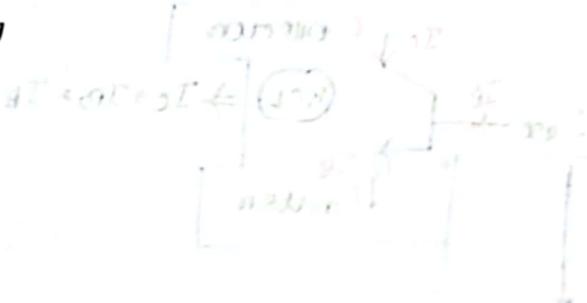

$$\text{Hence } V_D = 5 \text{ V}, V_G = 2 \text{ V}$$

let the NMOSFET is in the saturation region

$$i_D = \frac{1}{2} K V_{DS}^m$$

$$\text{Hence } V_{DS} = V_G - V_{TH} = (V_G - V_S) - V_{TH}$$

$$= 2(1 - V_S) - 1$$

$$= 1 - V_S$$

$$\text{Hence } i_D = \frac{1}{2} K V_{DS}^m$$

$$= \frac{1}{2} \times 4 \times (1 - V_S)^m$$

$$= 2(1 - V_S)^m$$

$$\text{Hence } i_D = \frac{V_S - 0}{1} = V_S$$

$$\therefore V_S = 1(1 - V_S)^m$$

$$\Rightarrow 2V_S^m - 2V_S + 1 = 0$$

$$\Rightarrow V_S = 0.6 \text{ V}, V_S = 2 \text{ V}$$

Hence,

$$\begin{aligned} V_{GS} &= V_G - V_S \\ &= 2 - 0.6 = 1 \text{ V} \\ &= 1.5 \text{ V} \end{aligned}$$

$$\begin{aligned} V_{DS} &= V_D - V_S \\ &= 5 - 0.6 = 4.4 \text{ V} \end{aligned}$$


$$V_{DS} = V_{GS} - V_{TH} = 1.5 - 1 = 0.5 \text{ V}$$

sat
 $\left\{ \begin{array}{l} V_{GS} \geq V_{TH} \\ V_{DS} \geq V_{DS} \end{array} \right.$


WEDNESDAY

DATE: 08/09/23

*Bipolar Junction Transistor (BJT):

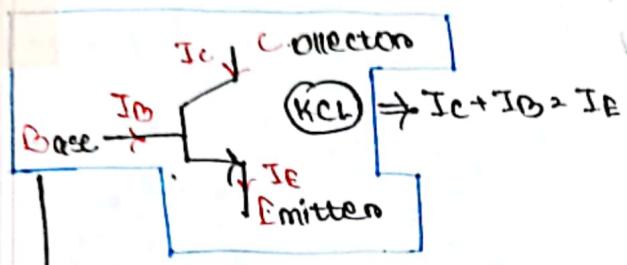


control terminal

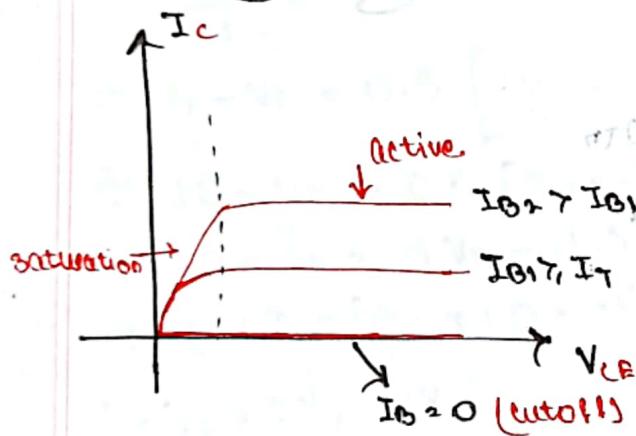control signal: I_B 


MOSFET & nmos

pMOS & PMOS

* MOSFET

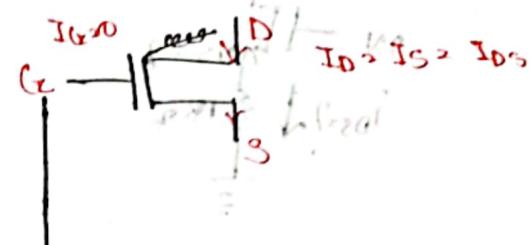

control terminal

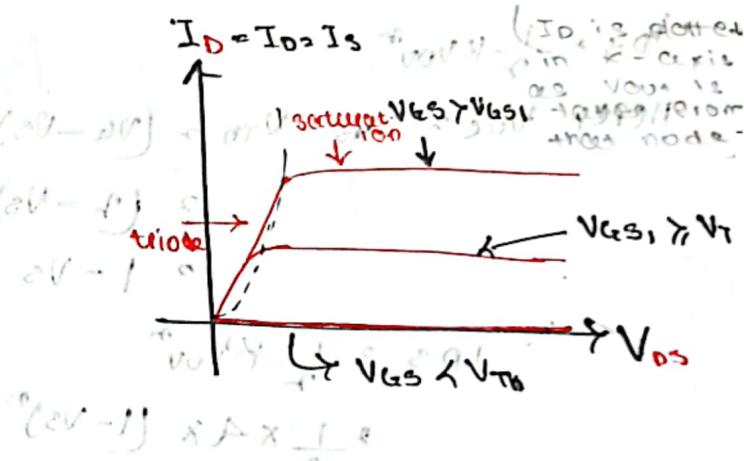control signal: V_{GS} 

$$I_D = \frac{1}{2} C_{DS} (V_{GS} - V_{DS})^2$$


$$V_{DS} = V_{DD} - I_D \cdot R_{DS}$$

$$V_{DS} = V_{DD} - \frac{1}{2} C_{DS} (V_{GS} - V_{DS})^2 \cdot R_{DS}$$

$$V_{DS} = V_{DD} - \frac{1}{2} C_{DS} (V_{GS} - V_{DS})^2 \cdot R_{DS}$$

$$V_{DS} = V_{DD} - \frac{1}{2} C_{DS} (V_{GS} - V_{DS})^2 \cdot R_{DS}$$

* Switch model:

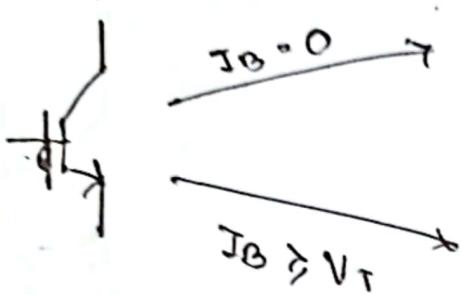

$I_B = 0$


$I_B > V_T$

(Logic 0)

(Logic 1)




* NOT gate:

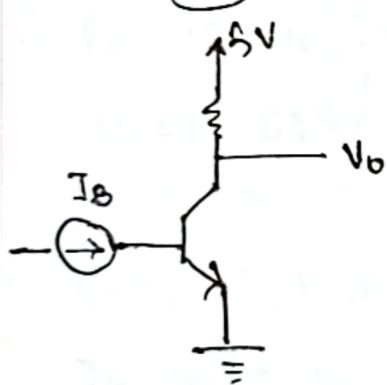

V_i

V_o

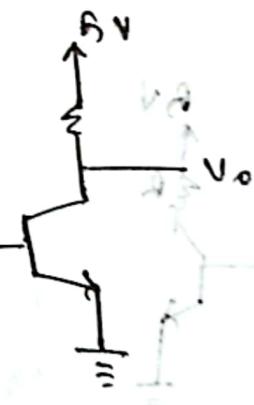


$I_B = 0 \rightarrow \text{OFF} \rightarrow V_o = 5V \text{ (1)}$

$I_B > V_T \rightarrow \text{ON} \rightarrow V_o = 0V \text{ (0)}$


* Problem

(1) input current, output voltage.



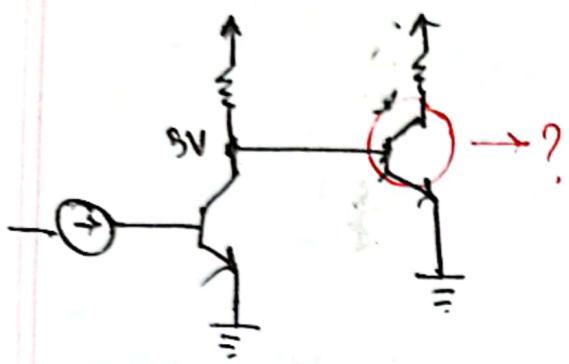


~~1 R~~

$$i = \frac{y}{R}$$

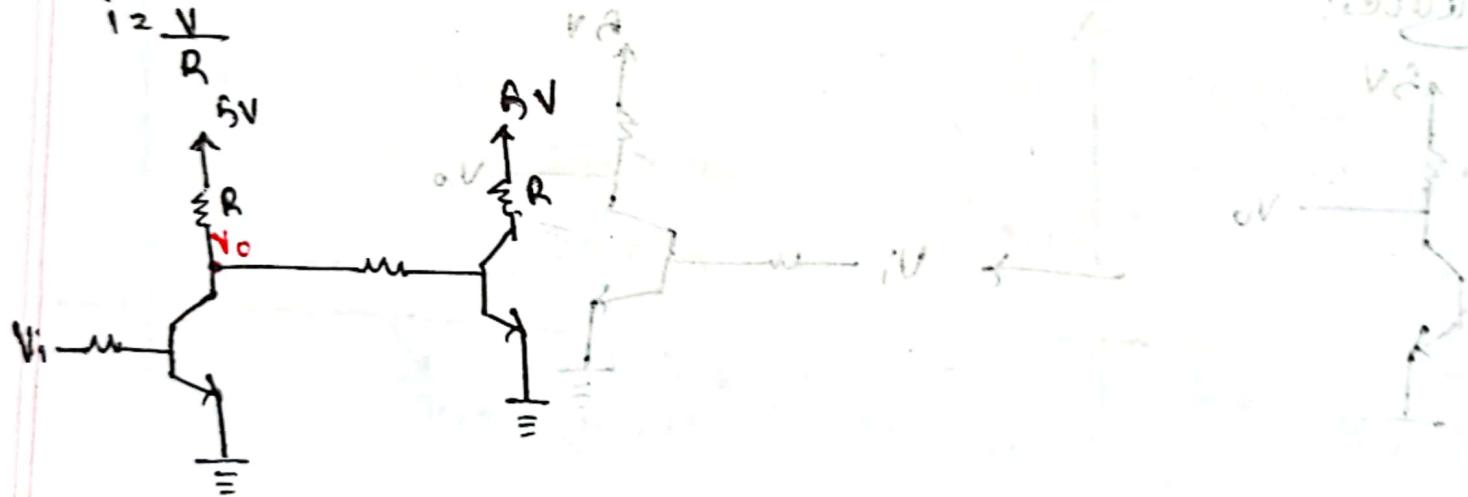

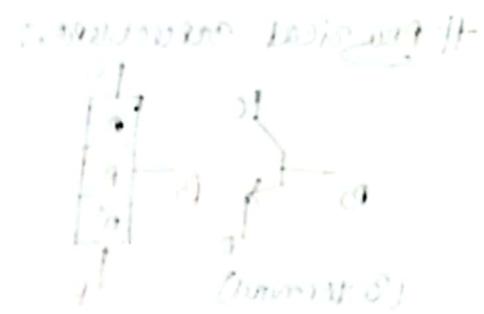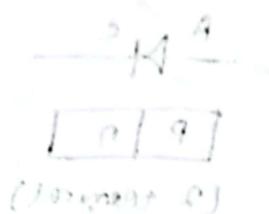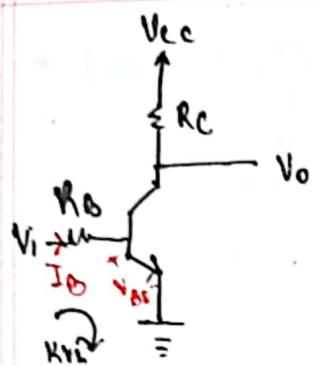(ii) difficult to build a good current source



$$V_i = I_B R_B + V_{BE}$$

$$\text{if } I_B = I_T, \text{ then}$$

$$\therefore V_i = V_{TRB} + V_{BE}$$

$$\text{if } R_B = 100\text{ k}\Omega, I_T = 0.022\text{ mA}, V_{BE} = 0.7\text{ V}$$

$$\therefore V_i = (0.022 \times 100) + 0.7 \\ \approx 3\text{ V}$$

[If $V_i \neq 3\text{ V}$, then BJT will not be ON]

$\therefore I_B$ must be at least I_T to turn the BJT on

$\therefore V_i$ must be at least $(I_{TRB} + V_{BE})$ for BJT on.

I_B \neq must at

$$V_{BE} + 0.7\text{ V}$$


$$0.7\text{ V} = 0.7\text{ V}$$

I_B \neq must at


$$[V_{BE}] + 0.7\text{ V}$$

$$[0.7\text{ V}] + 0.7\text{ V} = 1.4\text{ V}$$

Physical structure:

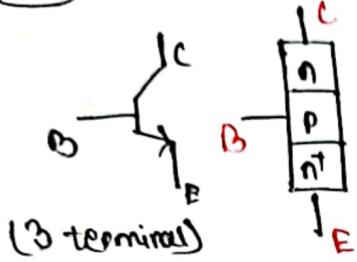

(2 terminal)

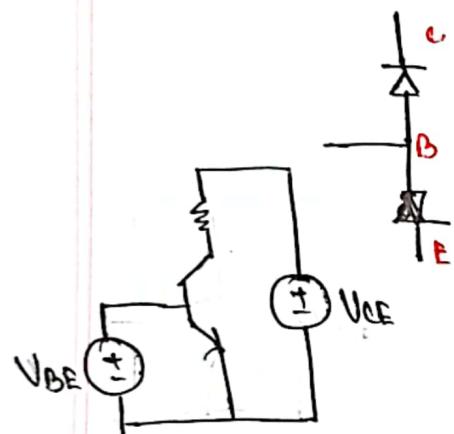


$$V_{BC} = V_B - V_C$$

$$= (V_B - V_E) - (V_E - V_C) = V_{BE} - V_{CE}$$

* Case 1: BC off, BE off [cutoff]


$$V_{BE} < 0.6V \quad V_{BE} < 0.7V$$

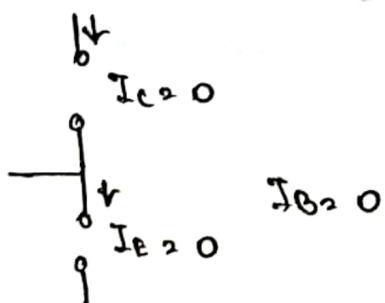

I_c and $I_e = 0$, so there is no route for I_B to flow.

$$\therefore I_B = 0$$

B_C	B_E	
OFF	OFF	cutoff
ON	ON	saturation
ON	OFF	Active
OFF	ON	reverse active

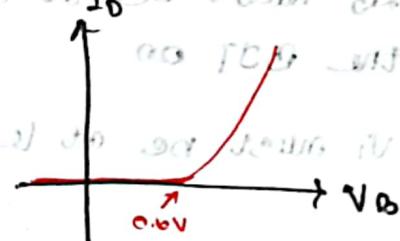

to turn BC off,

$$V_{BC} < 0.6V$$

$$\Rightarrow V_{BE} - V_{CE} < 0.6$$

to turn BE off,

$$V_{BE} < 0.7V \quad [\text{active}]$$

$$V_{BE} < 0.8V \quad [\text{saturation}]$$

* Case 2: BC ON, BE ON [saturation]


$$V_{BE} = V_{CE} \approx 0.6$$

$$V_{BE} I_B > 0$$


$$I_C > 0$$

$$V_{BE} = V_{CE} \approx V_{BE} - V_{BC} \\ \approx 0.8 - 0.6 \\ \approx 0.2 \text{ V}$$

* Case 3:

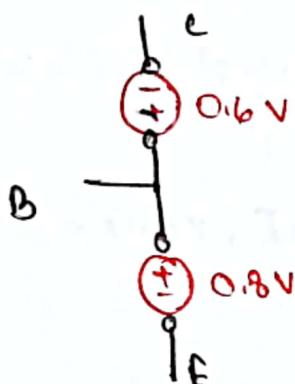

* Case 3: BC ON, BE OFF [active]

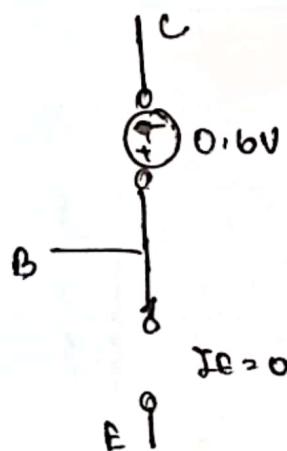

for this condition, if we use diode, I_B will be 0. But, here will be needing the value of I_B . So, BJT is used instead.

$$\sqrt{I_C = \beta I_B}$$


$$I_C \neq 0$$

$$= \beta I_B + I_C$$

Front page 40, 40 98; 8 3

$I_{DS} = K(V_{DS} - V_{DS(on)})^2$

at $V_{DS} = V_{DS(on)}$

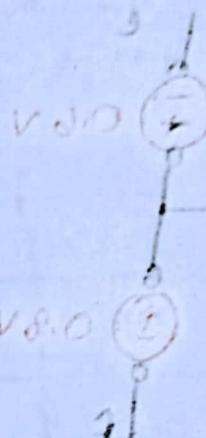

MOSFET

Region	Formula	Condition
saturation	$I_D = \frac{1}{2} K V_{GS}^2$	$V_{GS} > V_T$ $V_{DS} > V_{DS(on)}$
triode	$I_D = K(V_{GS}V_{DS} - \frac{1}{2}V_{DS}^2)$	$V_{GS} > V_T$ $V_{DS} < V_{DS(on)}$
cutoff	$I_D = 0$	$V_{GS} < V_T$

Front page 40, 40 98; 8 3

BJT

Region	Formula	Condition
active	$V_{BE} = 0.7V$ $I_C = \beta I_B$	$V_{CE} > 0.7$
saturation	$V_{BE} = 0.8V$ $V_{CE} = 0.2V$	$\frac{I_C}{I_B} < \beta$
cutoff	$I_B = I_C = I_E = 0$	$V_{BE} < 0.7$

MONDAY

DATE: 10/01/23

* Method of Assumed States

Step 1: Assume

→ cutoff $[I_B = I_C = I_E = 0]$ → active $[V_{BE} \geq 0.7V, I_C = \beta I_B]$ → saturation $[V_{BE} \geq 0.8V, I_C = 0.2V]$

Step 2: Solve

Step 3: Verify

→ cutoff $V_{BE} < 0.7V$ → active $V_{CE} > 0.2V$ → saturation $\frac{I_C}{I_B} > \beta$

For BJT, start assuming with active region.

Ex 1: $\beta = 100$
 $V_{i2} = 1V$

Ans: $V_{o2} = 9V$

Let, the BJT is in active region.

$$\therefore V_{BE} > 0.7V$$

$$V_B - V_E = 0.7$$

$$\downarrow$$

$$0$$

$$\Rightarrow V_B = 0.7V$$

$$\therefore I_B = \frac{V_i - V_B}{100} = \frac{1 - 0.7}{100} = 0.003 \text{ mA}$$

$$I_C = \beta I_B$$

$$= (100) (0.003)$$


$$= 0.3 \text{ mA}$$

Now, $I_C = \frac{10 - V_C}{3}$

$$\therefore V_C = 10 - 3 \times 0.3$$

$$= 9.1V$$
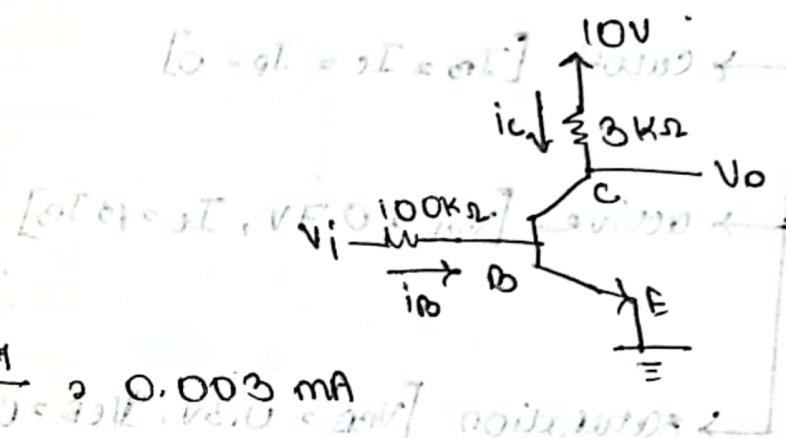
$$\therefore V_{CE} = 0, V_{CE} = V_C = 9.1V$$



Ans: $V_o = 9V$

Ans: $V_o = 9V$

$$Q2: B = 100 \\ V_B = 5V$$

Let the BJT is in active region

$$\therefore V_{BE} \approx 0.7V$$

$$V_B - V_E \approx 0.7V$$

$$V_B \approx 0.7V$$

$$\therefore I_B \approx \frac{V_B - V_E}{100} = \frac{5 - 0.7}{100} = 0.043mA$$

$$I_C \approx \beta I_B$$

$$\approx (100)(0.043)$$

$$\approx 4.3mA$$

Here, $I_C = \frac{10 - V_C}{3}$

$$V_C = 10 - (3 \times 4.3)$$

$$V_C = -2.9V$$

$$\therefore V_{CE} = -0.2V, V_{CE} = V_C = -2.9 \neq 0.2V$$

The assumption is incorrect for the active region.

*BJT in active mode acts like a current controlled current source & amplifier.

*MOSFET in saturation mode acts as a voltage controlled current source.

Let the BJT is in saturation region

$$V_{BE} = 0.8V$$

$$\Rightarrow V_B - V_E = 0.8$$

↓

0

$$\Rightarrow V_B = 0.8V$$

$$I_B = \frac{5 - V_B}{100}$$

$$= \frac{5 - 0.8}{100}$$

$$= 0.042 \text{ mA}$$

$$V_{EB} = 0.2V$$

$$\Rightarrow V_C - V_E = 0.2$$

$$\therefore V_C = 0.2V$$

$$I_C = \frac{10 - V_C}{5}$$

$$= \frac{10 - 0.2}{5}$$

$$I_C = 1.96 \text{ mA}$$

$$\frac{I_C}{I_B} = \frac{1.96}{0.042} = 46.67 < \beta \quad \checkmark$$

0.01 < α < 1
0.9 < β < 10

0.1 < α < 1
1 < β < 10

1 < α < 10
10 < β < 100

10 < α < 100
100 < β < 1000

0.5 < α < 1
1 < β < 10

1 < α < 10
10 < β < 100

1 < α < 10
10 < β < 100

1 < α < 10
10 < β < 100

1 < α < 10
10 < β < 100

1 < α < 10
10 < β < 100

1 < α < 10
10 < β < 100

1 < α < 10
10 < β < 100


1 < α < 10
10 < β < 100

1 < α < 10
10 < β < 100

WEDNESDAY

DATE: 12/09/23

* BJT amplifier (CE configuration):

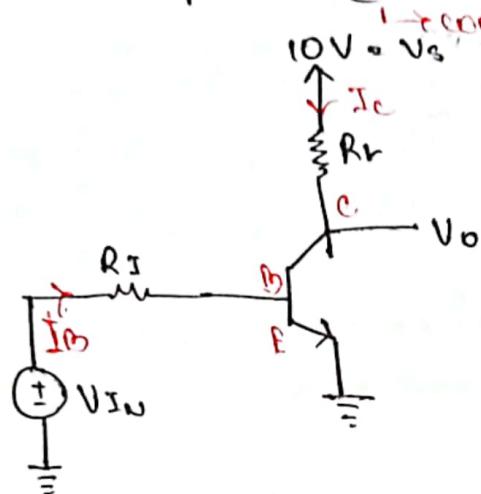

emitter is between V_I and V_o ,
so emitter is common node.

$R_S \rightarrow$ connected to V_{IN}
 $R_L \rightarrow$ connected to V_S

Types of amplifiers

- (1) Voltage amplifier ($IN = V_o / V_{IN}$, $Out = V_o$)
 - (2) Current amplifiers ($IN = I_o / I_{IN}$, $Out = I_o$)
 - (3) Transconductance amplifier ($IN = V_o / V_{IN}$, $Out = G$)
 - (4) Transresistance amplifier ($IN = I_o / V_{IN}$, $Out = V_o$)
- check, $\frac{V_o}{V_{IN}} = \frac{V_o}{\frac{V_S - V_{BE}}{R_R}} = \frac{V_o}{\frac{V_S}{R_R}} = \frac{V_o}{V_S} = G$ (conductance)

for amplification, we have to choose the active region.

Active

$I_C = \beta I_B$ [Increasing V_{IN} , increase I_B (which increases I_C)]

$$0.7 < V_{IN} < 0.7 + \frac{V_S - 0.7}{\beta R_R} R_I$$

* If $V_{IN} < 0.7$, BJT will be in cutoff region and no current flows.

* If $V_{IN} > 0.7 + \frac{V_S - 0.7}{\beta R_R} R_I$, BJT will be in saturation region.

$$V_{BE} = 0.7 + \frac{V_S - 0.7}{\beta R_R} R_I$$



$V_{BE} > V_{BE(on)}$
saturation region

Electronics


TRANSISTOR

	cutoff	active	saturation	when $V_B = 0.7V$ and $V_E = 0V$
V_O	$0.7 < V_{IN} < 0.7 + \frac{V_B - 0.7}{\beta R_L} R_I$	$V_O = V_B + \frac{V_B - 0.7}{R_I} R_L$	$V_O = V_B + \frac{V_B - 0.7}{R_I} R_L$	$V_O = 10V$

At cutoff, $V_O = 0V$

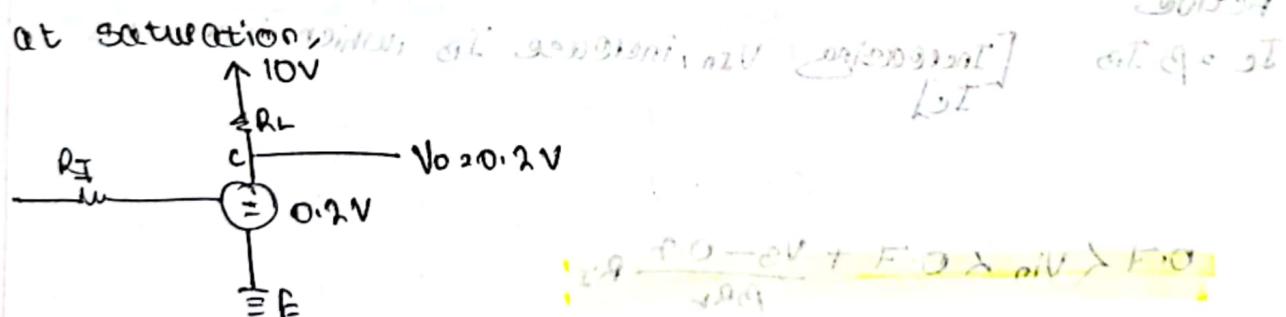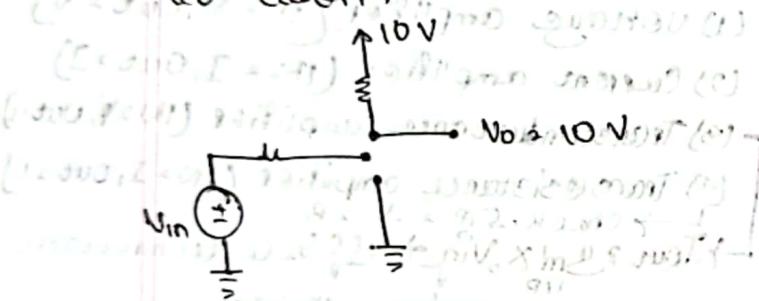

Transfer characteristics

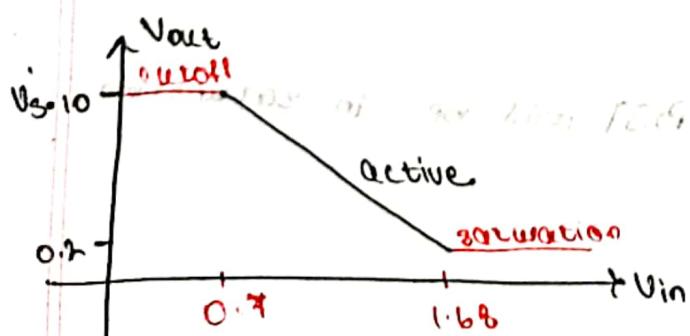

$$V_O = V_B + \frac{V_B - 0.7}{R_I} R_L = 10 + \frac{10 - 0.7}{10} \cdot 1 = 10.3V$$

constant \rightarrow amplifier factor $- 10 V_{IN}$

Given, $R_I = 100k\Omega$ and $\beta I = 100$

$$V_B = 10V$$

$$R_L = 10k\Omega$$


$$0.7 + \frac{V_B - 0.7}{\beta R_L} R_I = 1.68V$$

$$0.7 < V_{IN} < 1.68V$$

βI will be in active region in this range.

V_{IN}	V_O
0.6V	10V
0.8V	✓
1V	7V
1.2V	✓
1.4V	0.9V

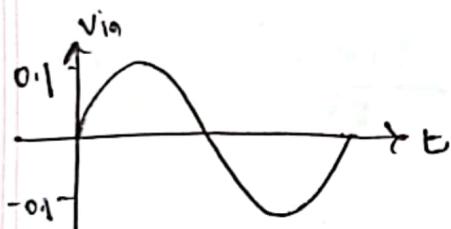
* This model is called "small signal approximation" as it only works for smaller input.




$$V_i = 0.1 \text{ Sin} \omega t$$

maximum = 1
minimum = -1


maximum = +0.1
minimum = -0.1

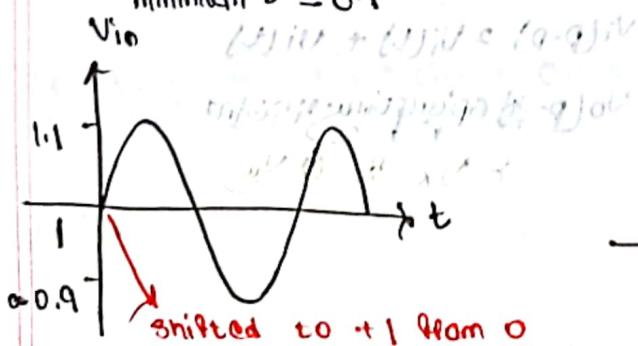

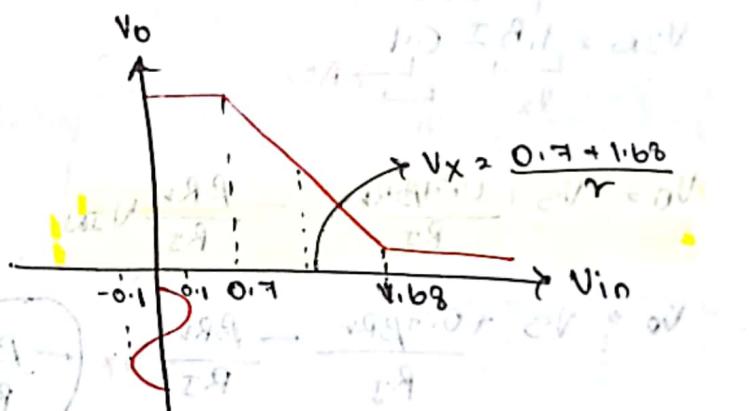* V_{LE} & V_{RE} are the operating points.



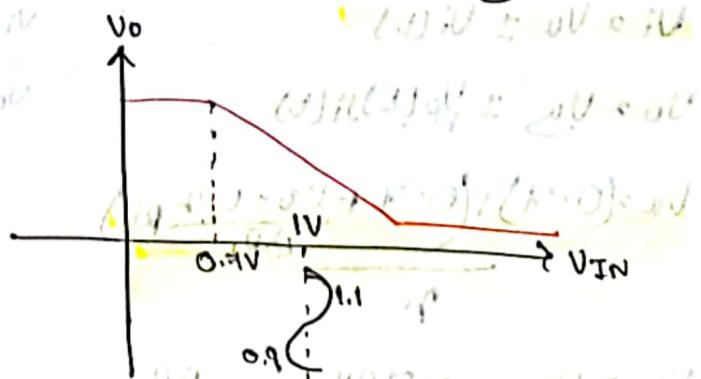* The V_{in} for is less than 0.7, so it lies in "cutoff". Thus, cannot be amplified using of BJT.




* A DC voltage is used to shift the cutoff region to the middle of active region.

- * A DC voltage offset voltage needs to be added.
- * The curve must lie completely within the active region.

- * Midpoint of active region needs to be find out to get the appropriate swing point.

begin assume no bias with $V_x = 0$

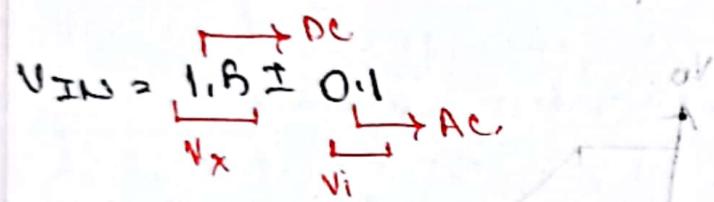

$$V_o = V_s + \frac{0.7 \beta R_L}{R_I} - \frac{\beta R_L}{R_I} V_{IN}$$

$$V_o = V_s + \frac{0.7 \beta R_L}{R_I} - \frac{\beta R_L}{R_I} V_x + \frac{\beta R_L}{R_I} V_i(t) + K V_i(t)$$

$$V_i = V_u \pm V_i(t)$$


$$V_o = V_u \pm K V_i(t)$$

$$V_u = (0.7) + (0.7 + \frac{V_s - 0.7}{\beta R_L}) R_I$$

$$V_u = V_s + \frac{0.7 \beta R_L}{R_I} - \frac{\beta R_L}{R_I} V_u$$

$$K = \frac{\beta R_L}{R_I}$$
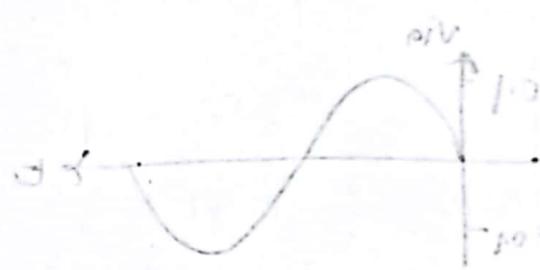
$$V_i(t) = V_u - 0.7 \quad \text{or} \quad V_i(t) = \frac{V_s - 0.7}{\beta R_L} R_I - V_u$$



$$\text{Scal. DC = } V_u$$

$$1 = 200 \text{ mV}$$


$$1 = 500 \text{ mV}$$

$$1 = 100 \text{ mV}$$

$$1 = 0 \text{ mV}$$


$$V_i(P-O) = V_i(t) + V_i(t)$$

$$V_o(P-O) = K V_i(t)$$

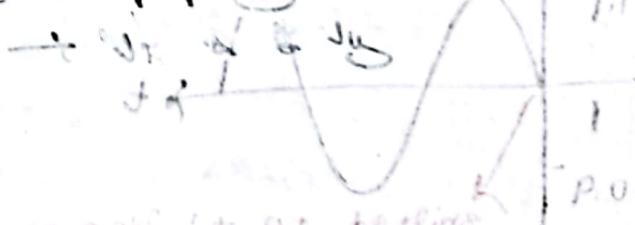

at 0.7V, 0.7V & 10V
at 0.7V, 0.7V & 10V

Example 1

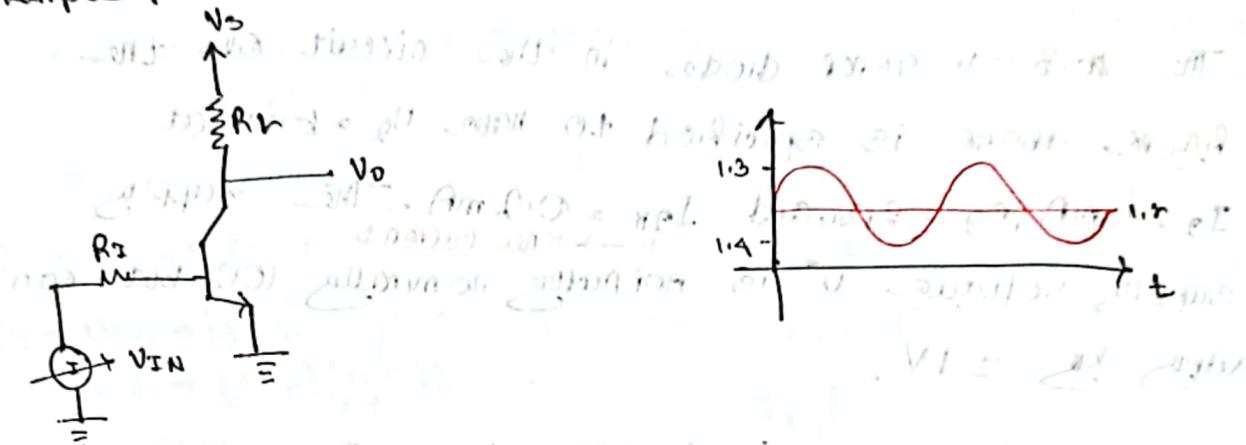

$$(a) V_{OJ} = V_s + \frac{0.1 \times \beta R_L}{R_J} - \frac{\beta R_L}{R_J} V_{XJ}$$

$$(b) K_2 = \frac{\beta R_L}{R_J}$$

$$(c) V_i (P-P) = 0.1 + 0.1 = 0.2V$$

$$(d) V_o (P-P) = |K_2| * V_i (P-P)$$




$$V_o (P-P) = 0.1 + 0.1 = 0.2V$$

PRACTICE PROBLEM

The 10.8-V zener diode in the circuit of the figure above is specified to have $V_Z = 6.8V$ at $I_Z = 5mA$, $R_2 = 20\Omega$, and $I_{ZK} = 0.2mA$. The supply voltage V^+ is normally 10V but can vary by $\pm 1V$.

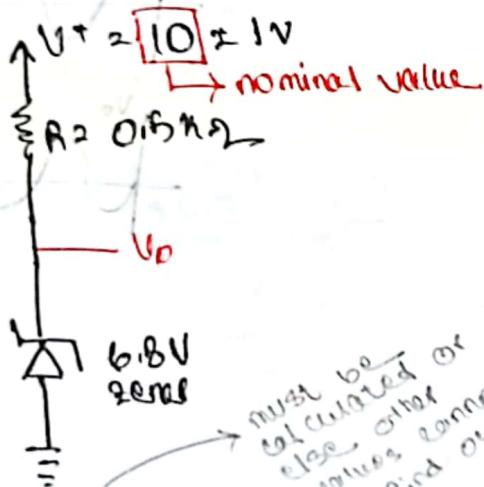(a) Find V_0 with no load and with V^+ at its nominal value.



$V^+ = 10 \pm 1V$ (nominal value)

$$V_0 = V^+ - I_Z R_2$$

$$I_Z = V_Z + I_Z R_2$$

$$0.8 = V_Z + (I_Z \times 0.02)$$

$$0.8 = 6.8 + (I_Z \times 0.02)$$

$$I_Z = 0.2mA$$


$$V_0 = 6.7V$$

$$I_T = 10$$

$$I_Z = 0.2mA$$

$$V_0 = 6.7V$$

$$I_Z = 0.02mA$$

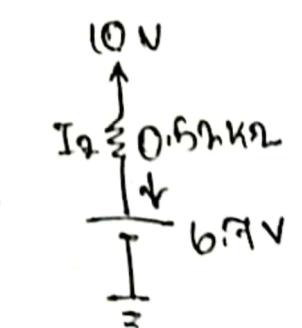


$$I_Z = \frac{10 - 6.7}{0.5k\Omega}$$

$$= 6.36mA$$

$$I_Z = \frac{10 - V_0}{0.5k\Omega}$$


$$V_0 = 10 - 0.5 \times I_Z \Rightarrow V_0 = 6.83V$$

REVIEW

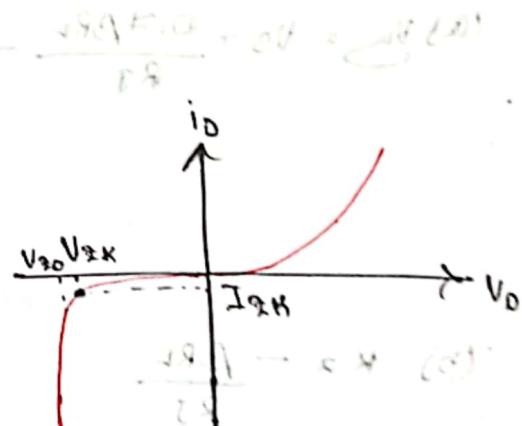

V_{ZK} (Knee voltage): The voltage at which current starts to drop.

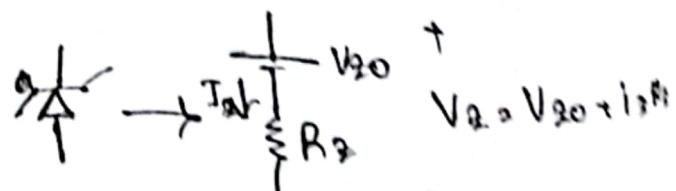I_{ZK} (Knee current): The current at V_{ZK} .



$$V_0 = 6.83V$$

(b) what is the minimum value of R_L for which the diode still operates as an amplifier? lowest value minimum value value 2A

$$V^+ = 9V$$

$$I_Q = I_{QH} = 0.2mA$$

$$V_Q = V_{D0} + i_Q R_Q$$

$$= 6.7 + (0.2)(0.02)$$

$$\approx 6.7V$$

$$I_{in} = \frac{9 - V_Q}{0.5}$$

$$= \frac{9 - 6.7}{0.5}$$

$$\approx 4.6mA$$


Applying KCL,

$$I_{in} = I_Q + I_R$$

$$4.6 = 0.2 + I_R$$

$$I_R = 4.4mA$$
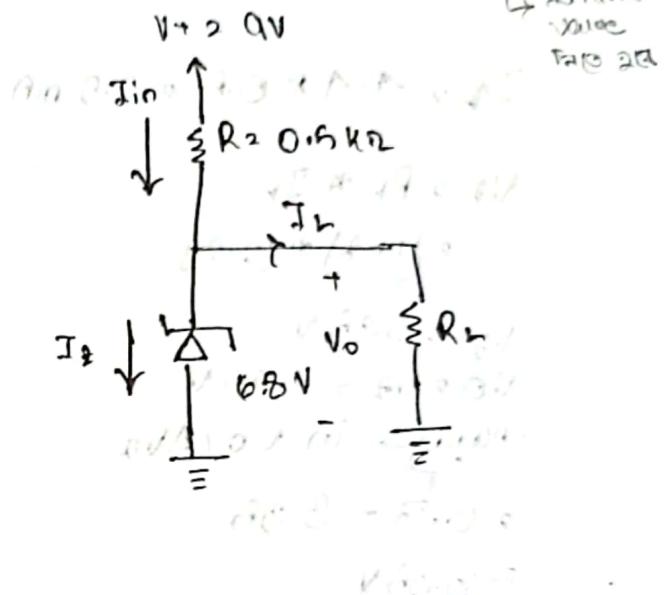
$$R_L = \frac{V_R}{I_R} = \frac{6.7}{4.4} = (1.52)k\Omega$$



(c) Explain the change in output voltage with the load current is reduced by 50%.

$$I_R = 4.4 \times 0.5 = 2.2 \text{ mA}$$

$$V_R = R_L \times I_R$$

$$= (1.62) \times (2.2)$$


$$V_R = 3.56 \text{ V}$$

$$V_D = V_R = 3.56 \text{ V}$$

change in V_D / V_R

$$= 6.7 - 3.56$$

$$= 3.36 \text{ V}$$

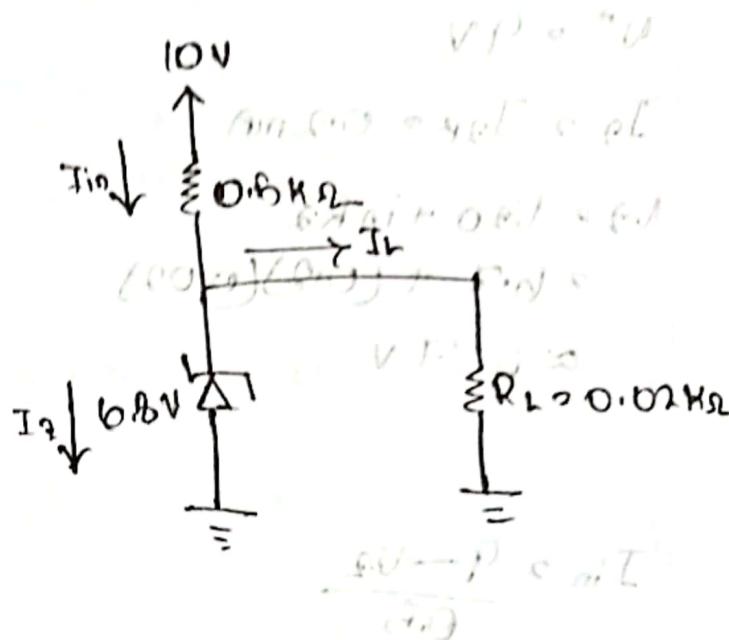

Ans 3.36

Ans 3.36

$\frac{10}{6.7} = 1.4999$

$1.4999 \times 6.7 = 10.16$

$10.16 - 10 = 0.16$


$0.16 \times 6.7 = 1.072$

$$-0.8 \times (0.16) = \frac{6.7}{6.7 + 0.8} \times 10 - 10.16$$

≈ 1.072

In this circuit above, the MOSFETs have the following parameters, $k'n = 2 \text{ mA/V}^2$, $\frac{W}{L} = 2.5$, $V_T = 0.5 \text{ V}$

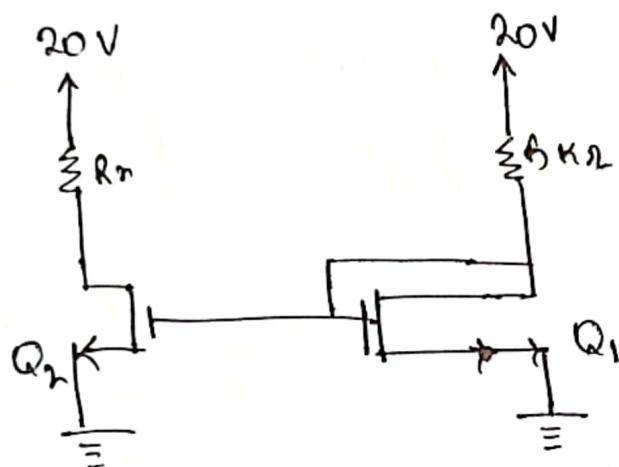Let's find out the operating mode of Q_1 [Hint: for Triode mode $V_{DS} < V_{OV}$ and for saturation $V_{DS} \geq V_{OV}$]



$$V_S = 0 \text{ V}$$

$$V_{GS} = V_G - V_S = V_G$$

$$V_{DS} = V_D - V_S = V_D$$

$$V_{OV} = V_{GS} - V_T$$

$$\text{Here, } V_D = V_G$$

$$V_{DS} = V_{GS}$$


$$\therefore V_{DS} < V_{OV}$$

$$\therefore \text{saturation}$$

$$\begin{aligned} i_D &= \frac{1}{2} k'n V_{OV}^2 = \frac{1}{2} \left(k'n \frac{W}{L} \right) * V_{OV}^2 \\ &\geq \frac{1}{2} \times 2 \times 2.5 \left(V_{GS} - V_T \right)^2 \\ &= 2.5 \left(V_D - 0.5 \right)^2 \\ \therefore i_D &= \frac{20 - V_D}{R_m} = 2.5 \left(V_D - \frac{1}{2} \right)^2 \end{aligned}$$

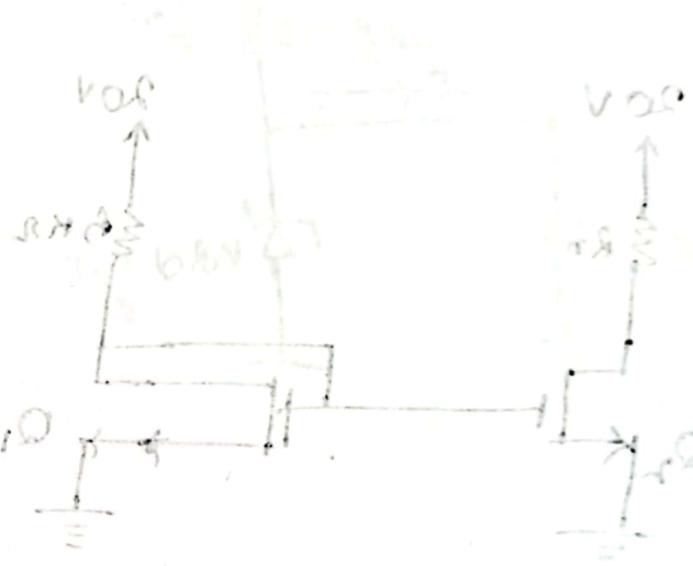(b) find the value of R_B that results in Q_2 in the operating at the edge of saturation, point.

when $V_{BE} = 0.7$ volt $V_{CE} = 12$ volt $I_C = 10$ mA
[not on the minimum not the maximum value]



$$V_B = 2V$$

$$\Delta V = 2V - 0.7V = 1.3V$$

$$\Delta V = 1.3V - 0.7V = 0.6V$$

$$1.3V - 0.7V = 0.6V$$


$$\Delta V = 0.6V - 0.3V$$

$$0.3V = 0.3V$$

$$V_{BE} = 0.3V$$

$$0.3V = 0.3V$$
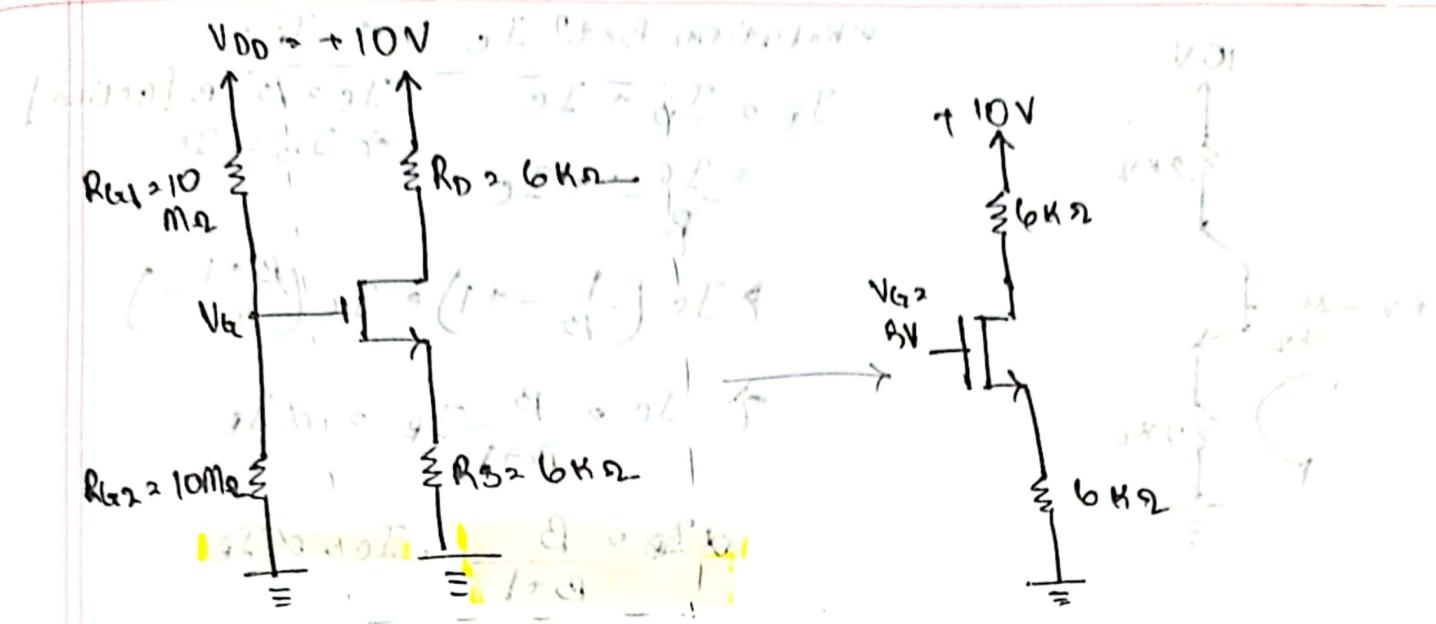
$$\frac{V_{BE} = 0.3V}{(12 - 0.3) \times 10 \times 10^{-3}} = \frac{0.3V}{11.7 \times 10^{-3}}$$



$$\frac{V_G - R_{G2}}{R_{G2} + R_{G1}} * V_{DD}$$

$$\frac{10}{10+10} * 10$$

$$V_1^2 \approx V$$

201 c 8

001 53

11-001

$$\frac{1057500}{500} = \frac{9}{5}$$


1918

Let the diode be in saturation region

$$2 \frac{\sqrt{3-0}}{6} \xrightarrow{\text{value need to find}} 2 \text{ is}$$

on P.O.O. vs. 27

622

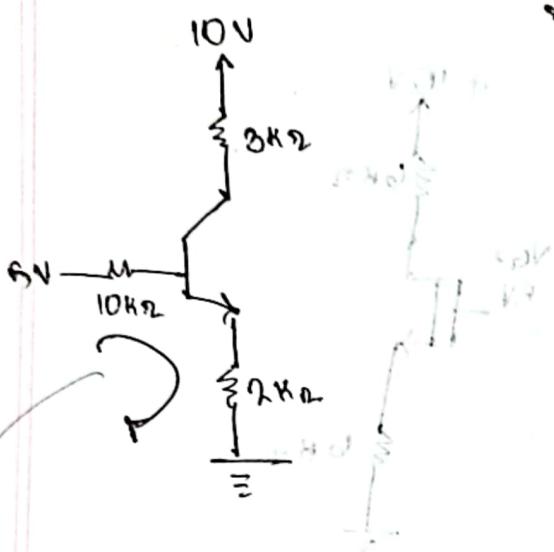

* Relation Betwⁿ I_C and I_E

$$\begin{aligned}
 I_F &= I_B + I_C & I_C &= \beta I_B \text{ [active]} \\
 \Rightarrow \frac{I_E}{\beta} &= I_C & \Rightarrow I_B &= \frac{I_C}{\beta} \\
 \Rightarrow I_C \left(\frac{1}{\beta} + 1 \right) &= I_C \left(\frac{\beta + 1}{\beta} \right) \\
 \Rightarrow I_C &= \frac{\beta}{\beta + 1} I_E = \alpha I_E \\
 \alpha I_E &= \frac{\beta}{\beta + 1} \quad I_C = \alpha I_E
 \end{aligned}$$

Here,

$$V_{BE} = 0.7 \text{ V} \text{ [active]}$$

$$\beta = 100$$

$$\text{applying KCL, } \beta = 10I_B + V_{BE} + 2I_F$$

$$\beta = 10I_B + V_{BE} + 2 \cdot \frac{\beta}{\alpha} I_B$$

$$\beta = 10I_B + 0.7 + 2 \cdot 10 \cdot \frac{1}{100} I_B$$

$$I_B = 0.02 \text{ mA}$$

$$I_C =$$

$$I_E =$$

$$\begin{aligned}
 I_C &= \alpha I_E \\
 \beta I_B &= \alpha I_E \\
 I_E &= \frac{\beta}{\alpha} I_B
 \end{aligned}$$

Here,

$$\beta = 100$$

$$\alpha = \frac{100}{100 + 1}$$

$$\begin{aligned}
 \frac{\beta}{\alpha} &= 100 \times \frac{100}{100 + 1} \\
 &= 100
 \end{aligned}$$

$$I_C = \frac{10 - V_C}{3} \neq 10 - 3I_C$$

Assignment 2 (AP1)

$$(1) V_2 = V_{20} + I_2 R_2$$

$$\Rightarrow 5.15 = V_{20} + (5 \times 0.05)$$

$$\Rightarrow V_{20} = 5.05 \text{ V}$$

$$(2) V_{in} = V_{in(\text{min})} = 10 - 0.1 = 9.9 \text{ V}$$

$$I_2 = I_{2K} = 0.3 \text{ mA}$$

$$V_2 = V_{20} + I_2 R_2$$

$$= 5.15 + (0.3 \times 0.05)$$

$$V_2 = 5.15 \text{ V}$$

$$(3) I_L = \frac{V_2 - V_{20}}{R_L}$$

$$= \frac{5.15 - 5.05}{10}$$

$$I_L = 0.05 \text{ mA}$$


$$I_3 = I_2 + I_L$$

$$I_3 = 0.3 + 0.05 \Rightarrow I_3 = 0.35 \text{ mA}$$

$$(4) I_3 = \frac{V_{in} - V_2}{R_3}$$

$$0.35 = \frac{9.9 - 5.15}{R_3}$$

$$R_3 = 4.10 \text{ k}\Omega$$

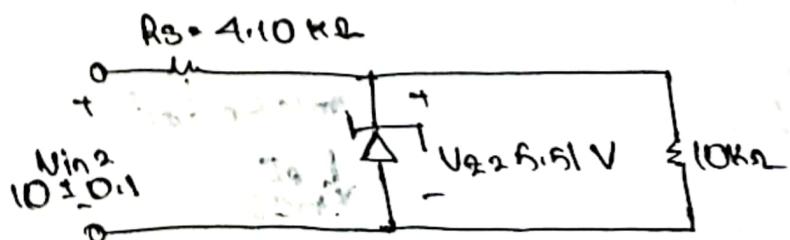

$$(b) (a) I_2 = I_{2K} + 0.75 \text{ mA}$$

$$V_2 = V_{20} + I_2 R_2$$

$$V_2 = 11 - 0.75 \times 0.5$$

$$V_2 = 11 \text{ V}$$

$$V_2 = I_2 R_2$$

$$4 = I_2 (1)$$

$$I_2 = 4 \text{ mA}$$

$$I_3 = I_2 + I_R \Rightarrow I_3 = 0.75 + 1$$

$$\Rightarrow I_3 = 1.75 \text{ mA}$$

$$0.05I^2 + 0.5V = 0.5I^2$$

$$(0.05 \times 0.75)^2 + 0.5 \times 11 = 0.5 \times 0.75^2$$

$$V_{20} = 11 \text{ V}$$

$$V_{D.P.} = 11 - 0.75 \times 0.5 \text{ (using milli)}$$

$$10.625 = 11 - 0.375 \text{ (in mA)}$$

$$0.375 + 0.5 \times 0.75 = 0.5$$

$$(0.05 \times 0.75)^2 + 0.5 \times 0.75 = 0.5$$

$$(b) I_3 = \frac{V_{D.P.} - V_2}{R_3}$$

$$1.75 = \frac{V_{D.P.} - 4}{0.1}$$

$$V_{D.P.} = 4.175 \text{ V}$$

$$\frac{0.5 - 0.375}{0.05} = 2.5$$


$$\frac{1.75}{0.1} = 17.5$$

(c) $V_{D.P.} \uparrow, I_3 \uparrow, I_2 \uparrow, I_2 \uparrow, I_R \uparrow, I_2 \uparrow$ for regulation.

$\therefore V_{D.P.} \uparrow$ does not affect regulation.

$$0.05(0.75)^2 + 0.5 \times 11 = 10.625 + 0.375 = 11 \text{ V}$$

Supply voltage

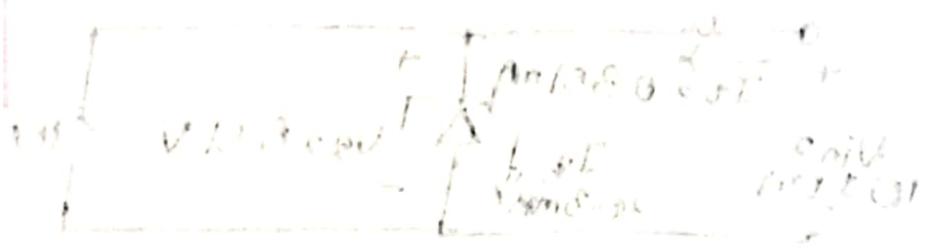


$$\frac{0.5 - 0.375}{0.05} = 2.5$$

$$\frac{1.75 - 0.375}{0.05} = 27.5$$

$$(a) \text{ Let } f = \bar{A}B + \bar{A}\bar{B}$$

$$(f = \bar{A}B + \bar{A}\bar{B})$$


(b)

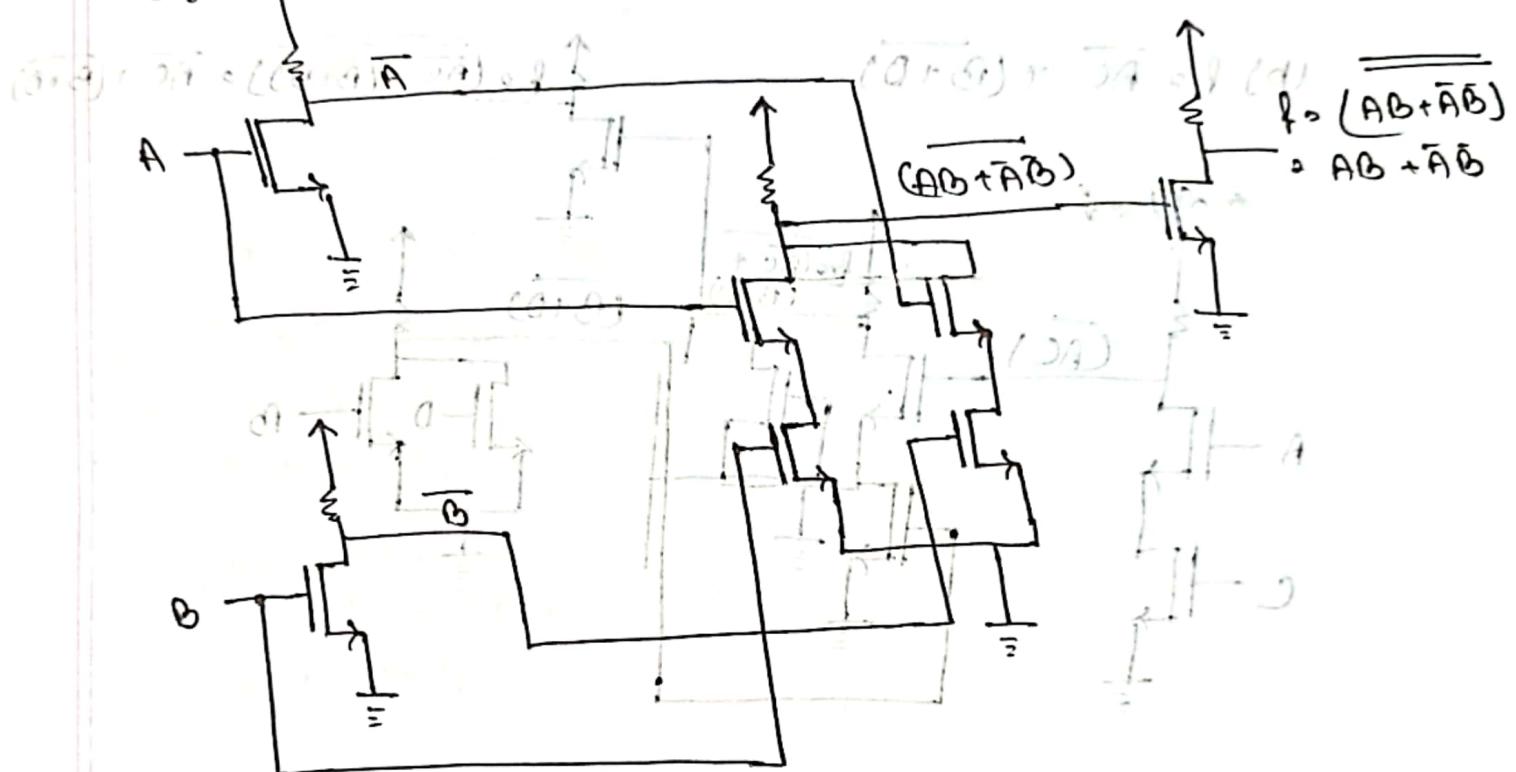

$$(2) \text{ f} = \overline{D} \overline{A} \overline{B} + C$$

For OR of all 0
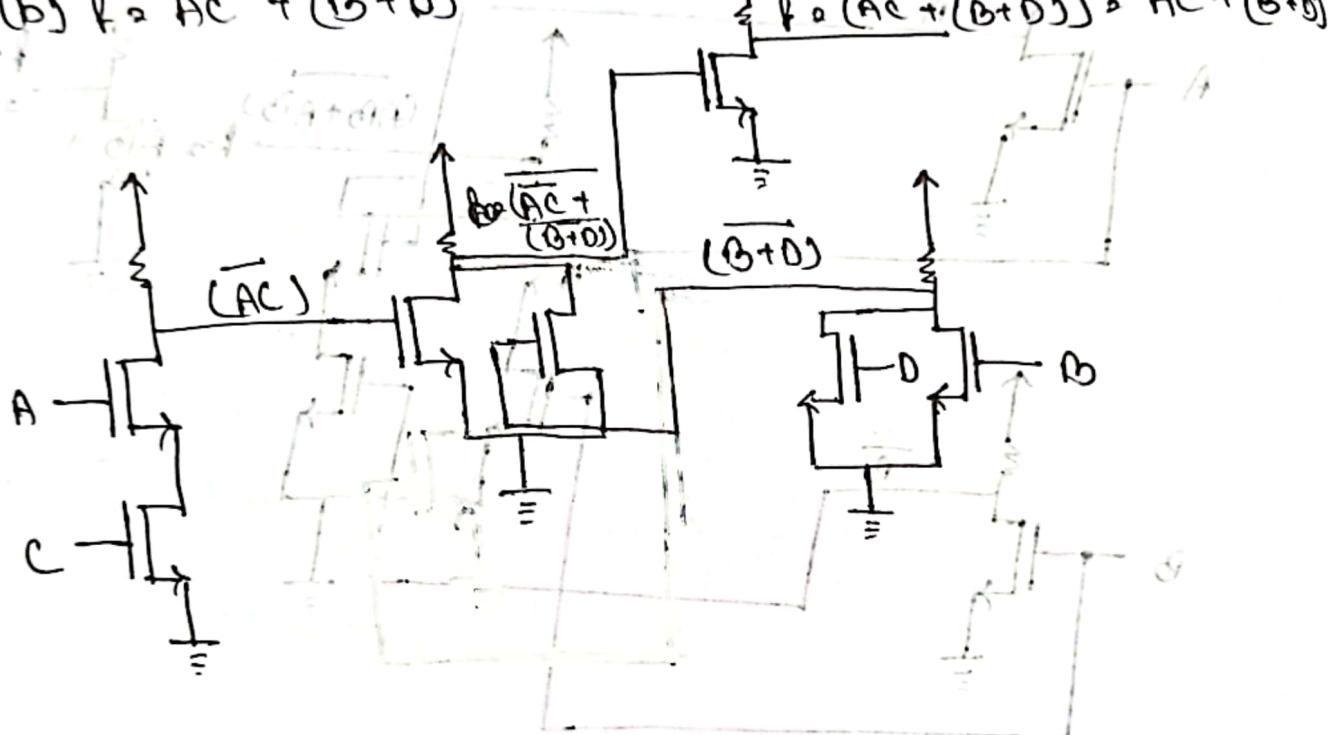
$$(b) f = \overline{AC} + (\overline{B} + \overline{D})$$



$$(b) (a) I_2 = I_{2K} (\text{min}) = 1 \text{ mA}$$

$$V_2 = V_{20} + I_2 R_2$$

$$= 9 + (1 \times 0.05)$$

$$V_2 = 9.05 \text{ V}$$

$$V_{in} = N V_{in} (\text{min}) = 11 \text{ V}$$

$$I_2 = I_2 (\text{max}) = 9 \text{ mA}$$

$$(b) I_3 = I_L + I_2$$

$$= 9 + 1$$

$$I_3 = 10 \text{ mA}$$

$$V_3 = V_{in} - V_2$$

$$V_3 = 11 - 9.05$$



$$V_3 = 1.95 \text{ V}$$

$$(c) V_3 = I_3 R_3$$

$$1.95 = 10 R_3$$

$$R_3 = 0.195 \text{ k}\Omega$$
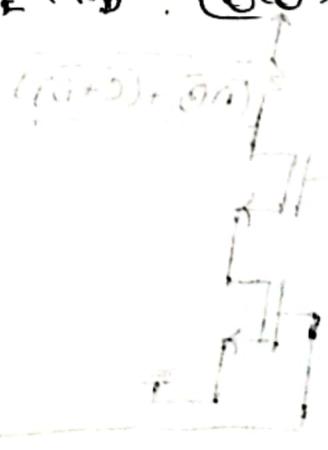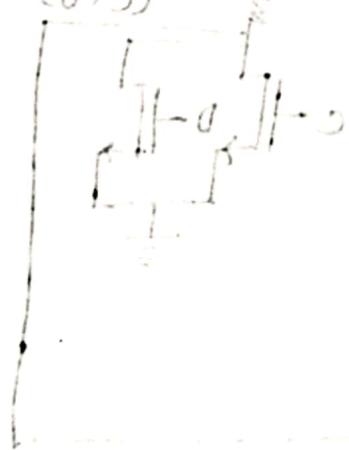
$$(d) \text{line regulation} = \frac{R_2}{R_2 + R_3} \times \frac{0.05 \text{ V}}{(0.05 + 0.195) \times 10} = 204.08 \%$$



(7) CKt-1:

$$f = \overline{(A+B)}C$$

out of this net is $\overline{C} \oplus D$

or $\overline{C} \oplus D \oplus 0 = \overline{C}$

$(C \oplus D) + \overline{D} =$

$C \oplus D \oplus 0 = C$

CKt-2

$$f = \overline{A} \overline{(B+C)}D$$

out of this net is $\overline{A} \oplus D$


$A \oplus D \oplus (C \oplus D) = \overline{A} \oplus D$

$\overline{A} \oplus D \oplus C \oplus D =$

$\overline{A} + D =$

$A \oplus D = \overline{A} \oplus D$

(7) (i) $Y = AB + C$

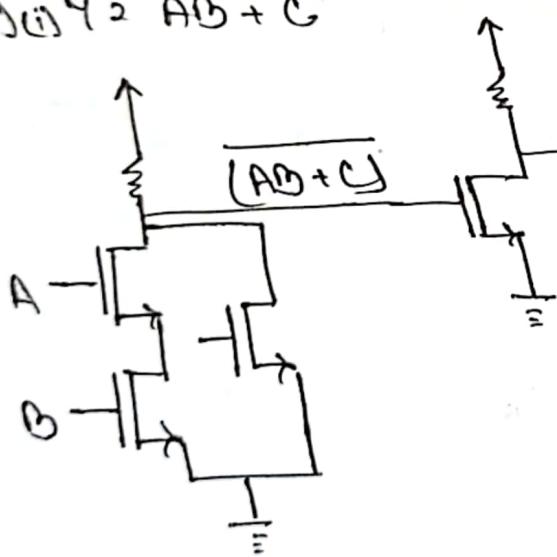

$$\overline{(AB+C)} = \overline{AB} + \overline{C} = \overline{A} \oplus \overline{B} + \overline{C} = A \oplus B \oplus C$$

$\overline{A} \oplus \overline{B} = AB$

$\overline{A} \oplus B = \overline{AB}$


$\overline{B} \oplus C = \overline{BC}$

$\overline{A} \oplus \overline{B} \oplus C = \overline{AB} + C$

$\overline{AB} + C = AB + C$


$\overline{AB} + C = AB + C$

$\overline{AB} + C = AB + C$

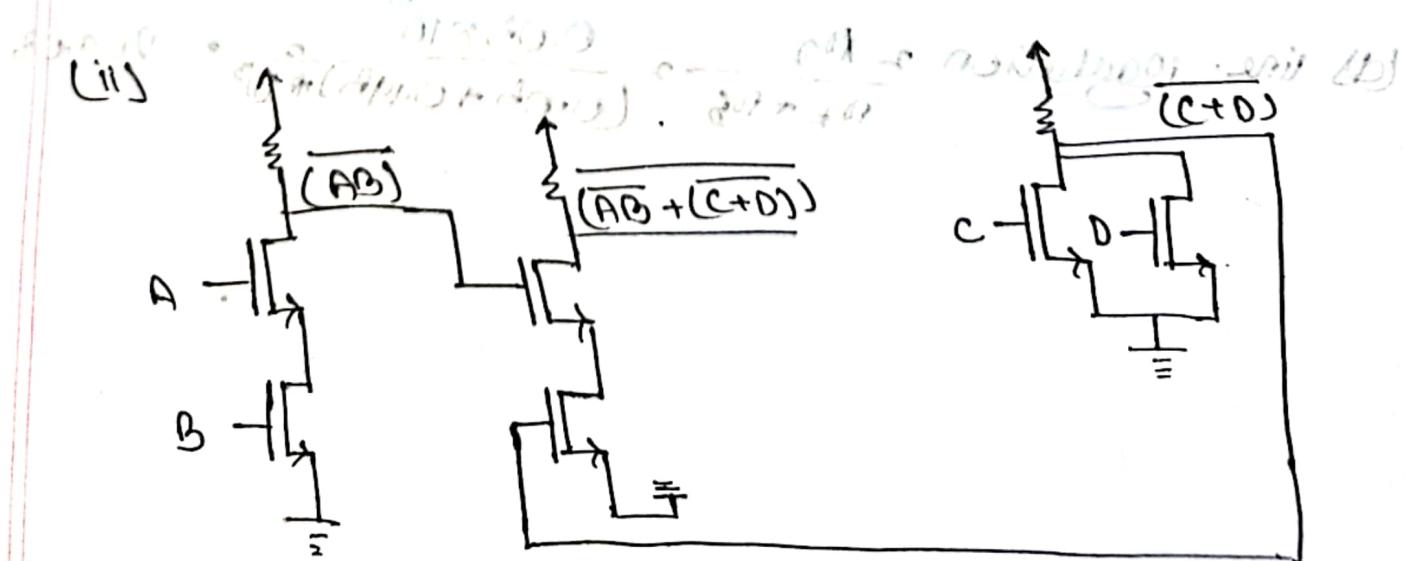

Assignment 3 (AF1)

(1) (a)

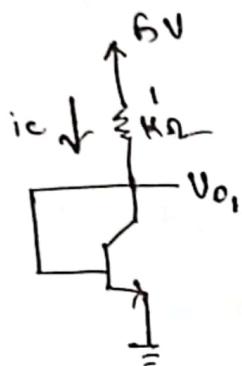

Let BJT be in active state.

$$V_B - V_E = 0.7V$$

$$V_B - 0 = 0.7V$$

$$V_B = 0.7V$$

$$V_{BE} = 0.7V$$


$$V_{CE} = V_C - V_B$$

$$= 0.7V - 0.2V = 0.5V < 0.7V$$

∴ Assumption is correct.

$$V_{O1} = V_C = 0.7V$$
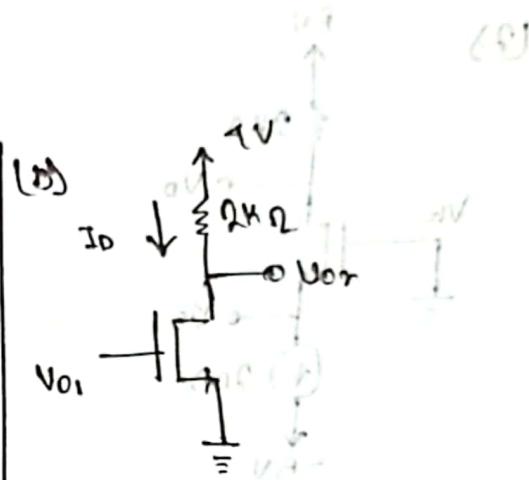
$$i_C = \frac{V_B - 0.7}{1} \Rightarrow i_C = 4.3mA$$



$$V_{O2} = 0.7V$$

Let mosfet be in saturation region

$$i_D = \frac{1}{r} K (V_{GS} - V_T)^2$$

$$= \frac{1}{r} (0.7 - 0.2 - 0.7)^2$$

$$i_D = 0.6mA$$

$$V_{GS} = 0.7 - 0.2 = 0.5V$$

$$i_D = \frac{1 - V_{GS}}{r}$$

$$0.6 = \frac{1 - V_{GS}}{r} \Rightarrow V_{GS} = 0.4V$$

$$V_{GS} = 0.7 - 0.2 = 0.5V$$

∴ Assumption is correct.

$$i_D = 0.6mA$$


$$V_{DS} = V_D = 0.7V$$

$$= 1.7V - 0.7V = 1V$$

$$= 1.7V - 1V = 0.7V$$

$$= 1.7V - 0.7V = 1V$$

(2)

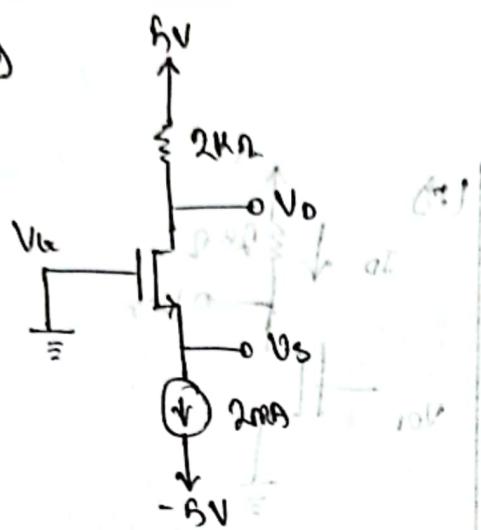

(17) & 30 marks



Circuit

(a) $V_{DS} = 0V, I_{DS} = 2mA$

(b) $I_{DS} = \frac{5 - V_D}{2k\Omega} \cdot 2mA$

$V_{DS} = 5 - \frac{5 - V_D}{2k\Omega} \cdot 2mA$

$V_D = 1V$ for Q_1 & Q_2

(c) Let the mosfet be in saturation region

$$I_{DS} = \frac{1}{2} k (V_{DS} - V_{th})^2$$

$$2k\Omega \cdot \frac{1}{2} k (V_{DS} - V_{th})^2$$

$$1 = (-V_{DS} - 1)^2$$

$$V_{DS} = 2V_3 + 1 = 1$$

$$V_3 (V_3 + 2) = 0 \text{ and } 3 = 0$$

$$V_3 = 0V, V_3 = -2V$$

$$V_{DS} = 0 - 0 \neq 1 \times$$

$$V_{DS} = 0 - (-2) \neq 1 \times$$



$$V_{DS} = 1 - (-2) = 3 \neq 1 \times$$

∴ Assumption is correct

$$V_3 = -2V$$

$$V_{DS} = 2V_3 + 1 = 1$$

$$V_{DS} = 2(-2) + 1 = 1$$

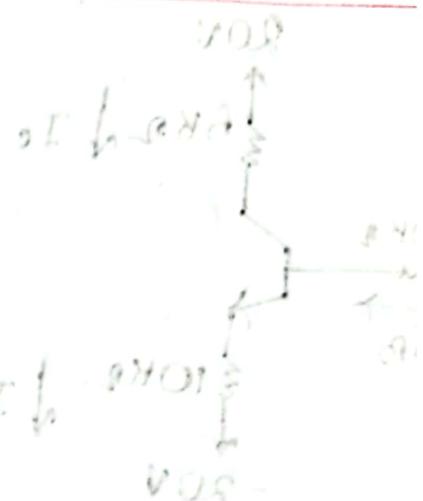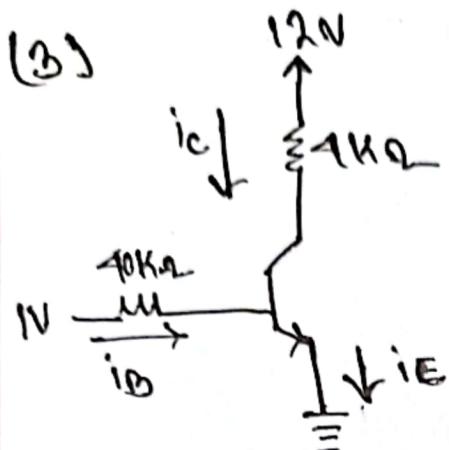

Let BJT be in active state

$$VBE = 0.7$$

$$V_B - V_E = 0.7 \Rightarrow V_B = 0.20.7$$

$$V_B = 0.14V$$

$$i_B = \frac{1 - 0.7}{40} \Rightarrow i_B = 0.025 \text{ mA}$$

$$i_C = \beta i_B = 100 \times 0.025 \text{ mA} = 0.75 \text{ mA}$$


$$i_C = \frac{12 - V_C}{1k} \Rightarrow 0.75 = \frac{12 - V_C}{1k} \Rightarrow V_C = 9V$$

$$V_{CE} = V_C - V_E = 9 - 0.29 = 8.71V$$

∴ Assumption is correct

$$\text{Hence } i_C = 0.75 \text{ mA}$$

$$V_{CE} = 9V$$

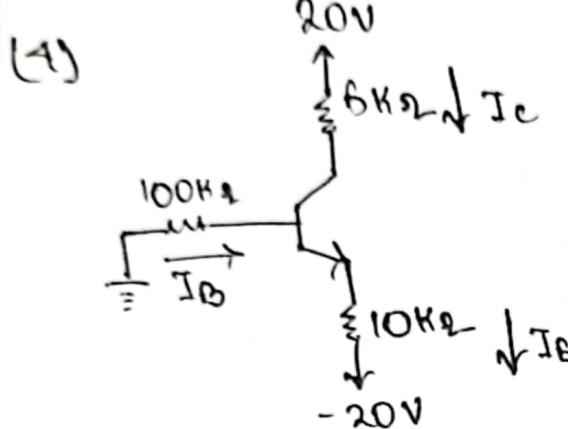

Let BJT be in active state

$$V_{BE} = 0.7 \text{ V}$$

$$I_B = \frac{0 - V_B}{100} \Rightarrow V_B = -100I_B \quad (1)$$

$$I_C = \frac{20 - V_C}{5} \Rightarrow V_C = 20 - 5I_C$$

$$I_E = \frac{V_E + 20}{10} \Rightarrow V_E = 10I_E - 20$$

$$I_B + I_C = I_E \quad [I_C = \beta I_B = 100I_B]$$

$$I_E = I_B + 100I_B$$

$$\Rightarrow I_E = 101I_B$$

$$I_E = \frac{101V_B}{100}$$

$$V_E = 10 \left(\frac{-101V_B}{100} \right) - 20$$

$$V_E = -\frac{101}{10} V_B - 20$$

$$V_{BE} = V_B - V_E$$

$$0.7 = V_B - \left[-\frac{101}{10} V_B - 20 \right]$$

$$V_B = -1.74 \text{ V}$$



$$V_E = \frac{-101(-1.74) - 20}{10} = 0.6$$

$$V_E = 2.13 \text{ V}$$

$$I_C = \beta I_B$$

$$\frac{20 - V_C}{5} = 100 \left[0 - \frac{(-1.74)}{100} \right]$$

$$V_C = 11.3 \text{ V}$$

$$V_{CE} = V_C - V_E = 11.3 - (-2.13)$$

$$V_{CE} = 13.43 > 0.2 \text{ V}$$


∴ Assumption is correct.

$$I_B = \frac{0 - (-1.74)}{100} \Rightarrow I_B = 0.0174 \text{ mA}$$

$$I_C = 100(0.0174) \Rightarrow I_C = 1.74 \text{ mA}$$

$$I_E = 0.0174 + 1.74$$

$$I_E = 1.76 \text{ mA}$$

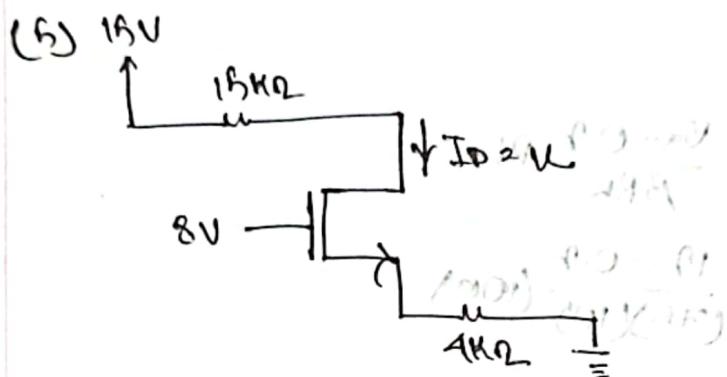

1821 - 1 - 22 1821

PLATE AND THE 50

Let $MOST$ be in saturation region

$$I_D = \frac{1}{2} K (V_{GS} - V_T)^n$$

$$I_D = \frac{1}{2} (q) (8 - 4n - 1)^n \quad \text{VPF-17} \quad \text{Ansatz, } \quad I_D = \frac{VS - 0}{1} \Rightarrow VS = 4 \cdot 10^6$$

$$u = 2 (7 - 4N)^r$$

$$12 = 2 \left[49 - 16bN + 16N^2 \right] \quad \frac{12}{2} = \frac{96 - 32bN + 32N^2}{2} \quad \frac{48 - 16bN + 16N^2}{2} = 0 \quad 16N^2 - 16bN + 48 = 0$$

$$16\Omega^m - 113\Omega^L + 98.2 \Omega^R$$

$$I_2 = 6.08 \text{ mA}, I_3 = 1.01 \text{ mA}$$

$$V_{\text{deg}} = 8 - 4n$$

$$V_{EG} = 8 - 4(6.05) = -16.2 \text{ V}$$

$$N_{\text{FeS}_2} = 4(1.01) = 3.96 \text{ V.T.P.}$$

وَهُوَ مُؤْمِنٌ بِاللَّهِ وَالنَّبِيِّ وَالْمُؤْمِنُونَ

$$2[15-6(1.01)] \rightarrow 4(1.01)$$

U_{DS} = 5.91 V, 2.96 A V_{DS} = 5.0 V, I_D = 2.96 A

∴ Assumption is correct

1. Assumption is ~~as~~ ^{that} ID = 1.01 mA

$$V_{DS} = 6.91V$$

Assignment 1 (AF1)

$$(1) (0.7 \times V_{in}) + 0.7 + \frac{V_{in} - 0.7}{R_L} R_L = 12$$

$$\Rightarrow 0.7 \times V_{in} + 0.7 + \frac{12 - 0.7}{(76)(10)} (100) = 12$$

$$\Rightarrow 0.7 \times V_{in} + 2.27 = 12$$

$$(2) K_2 = \frac{R_L}{R_i} = \frac{(76)(10)}{100} = 7.6$$

$$(3) V_{in} = \frac{0.7 + 2.27}{7} \Rightarrow V_{in} = 1.49V$$

$$V_{in} = V_{in} + \frac{0.7 R_L}{R_i} = \frac{R_L}{R_i} V_{in}$$

$$= 12 + \frac{0.7 (76)(100)}{10} = \frac{(76)(100)}{10} (1.49)$$

$$V_{in} = -580.6V$$

$$(4) V_{out} = (2.27 - 1.49) = 0.78V$$

$$V_{in} = 12 + \frac{0.7 (76)(100)}{10} - \frac{(76)(100)}{10} (0.78)$$

$$V_{in} = -48V$$

$$(2) \text{ by } V_R = 0.7 + 0.7 + \frac{V_B - 0.7}{R_L}$$

$$2 \cdot 0.7 + 0.7 + \frac{20 - 0.7}{(60)(2)} = 10$$

$$V_R = 1.525 \text{ V}$$

$$V_{O2} = V_B + \frac{0.7 R_L}{R_i} = \frac{R_L}{R_i} V_R$$

$$20 + \frac{0.7(60)(2)}{10} = \frac{(60)(2)}{10} (1.525)$$

$$V_{O2} = 10.1 \text{ V}$$

$$(ii) K_2 = \frac{-R_L}{R_i} = -\frac{(60)(2)}{10} = -12$$

Assignment 1 (F3H)

$$(1) I_2 = I_{2H} = 1.6 \text{ mA}$$

$$V_2 = V_{ZD} + I_2 R_2$$
$$= 4.5 + (1.6)(6)$$

$$V_2 = 12 \text{ V}$$

$$I_T = \frac{V_2}{R_L} \Rightarrow I_T = \frac{12}{4} = 3 \text{ mA}$$

$$I_i = I_2 + I_T = 1.6 + 3 = 4.6 \text{ mA}$$

$$V_{i2} = I_i R_i$$
$$= (4.6)(300)$$

$$\boxed{V_i = 1380 \text{ V}}$$

$$V_{i0} = 1380 \text{ V}$$

$$(2) V_{in} = V_{in}(\text{min}) = 15 - (15.04 - 10.4) = 13.5 \text{ V}$$

$$I_2 = I_{2H} = 2 \text{ mA}$$

$$V_2 = V_{ZD} + I_2 R_2$$

$$= 4.5 + (2)(\frac{10}{1000})$$

$$V_2 = 4.502 \text{ V}$$

$$I_i = \frac{V_i}{R_i} = \frac{13.5}{250} = 0.054 \text{ mA}$$

$$I_L = I_i - I_2$$

$$= 0.054 - 0.002$$

$$I_L = 0.052 \text{ mA}$$

$$R_L = \frac{V_2}{I_L} \Rightarrow R_L = \frac{4.502}{0.052} \Rightarrow R_L = 86.6 \text{ k}\Omega$$
$$R_L = 86.6 \text{ k}\Omega$$

(b) $I_{20}, I_{2R} = 1.6 \text{ mA}$


$$V_{20} = V_{20} + I_{2R}r_2 \\ = 4 + (1.6 \times \frac{100}{1000})$$

$$V_{20} = 4.6 \text{ V}$$

$$V_L = V_2 - 0 \\ N_L = 4.6 \text{ V}$$

$$(4) F = \overline{(AB + C)} D$$

$$(5) F = \overline{AB} + C$$

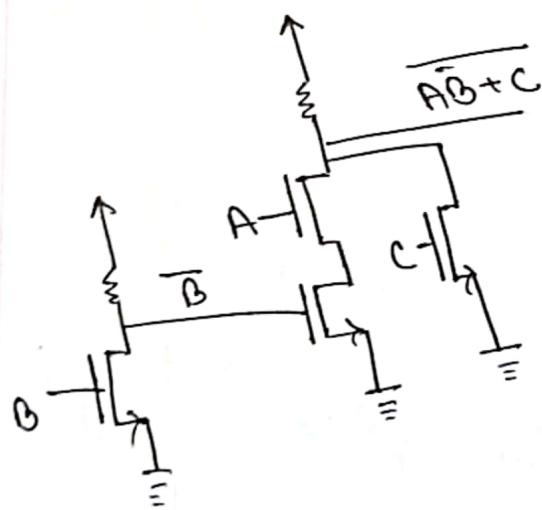


(6)




(6)

NOR Gate

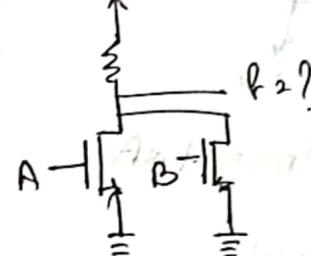

$A = 1, B = 0$	$B = 1, A = 0$	$A = 1, B = 1$
V_{cc}	V_{cc}	V_{cc}
$f_2 = 0$	$f_2 = 0$	$f_2 = 0$
$f_1 = 1$	$f_1 = 1$	$f_1 = 1$


A	B	V_{out}
0	0	1
0	1	0
1	0	0
1	1	0

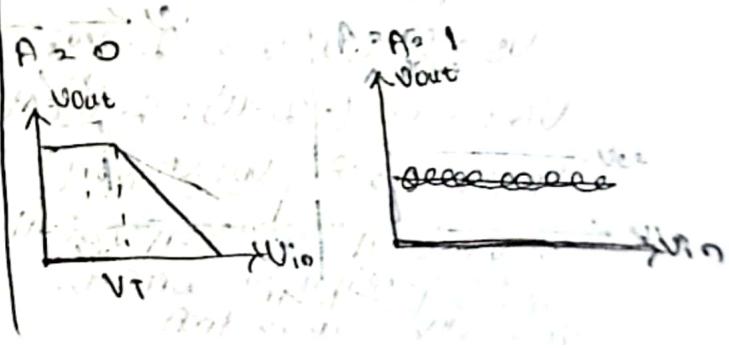

Assignment 6 (F3H)

Ansatz 2023

(a)

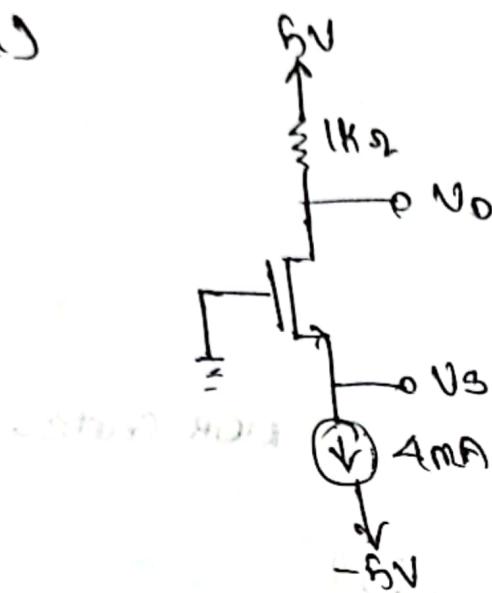

(a) $V_G = 0V, I_{D3} = 4mA$

(b) $I_{D3} = \frac{b - V_D}{1}$

$$\geq 4 \geq \frac{5 - V_D}{1} \geq V_D = 1V$$

(c) Let mosfet be in saturation region

$$I_{D3} = \frac{1}{2} k (V_G - V_S - V_T)^n$$

$$4 = \frac{1}{2} (4)(0 - V_S - 1)^n$$

$$2 = (-V_S - 1)^n$$

$$V_S + 2V_S - 1 = 0$$

$$V_S = 2.41V, V_S = -2.41V$$

$$V_{DS} = 0 - (-2.41) = 2.41V$$

$$V_{DS} = 2.41 - 1 = 1.41V$$

$$V_{DS} = 1 - (-2.41) = 3.41V > 1.41V$$

Assumption is correct.

$$V_{DS} = 2.41V \quad I_{D3} = 1mA$$

$$(2) \frac{V_{G2}}{R_{on}} < V_T$$

$$\frac{R_{on}}{R_{on} + R_L} < V_T$$

$$(b) \frac{R_{on}}{R_{on} + R_L} < 0.9$$

$$\Rightarrow 0.9 R_{on} < 0.9 R_{on} + R_L$$


$$\Rightarrow R_{on} < 0.882$$

$$R_{on} > \frac{1}{K_1 V_{on} \left(\frac{V_0}{L} \right)}$$

$$0.882 > \frac{0.25}{\frac{V_0}{L}}$$

$$\frac{V_0}{L} > 0.25$$

$$V_0 > 0.25 L$$

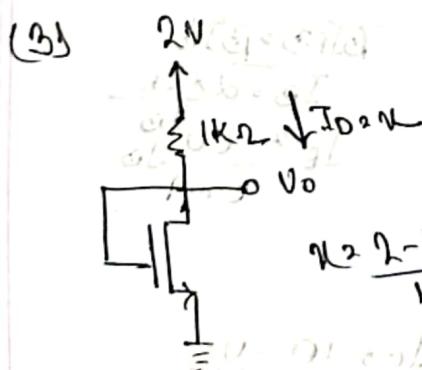

$$K_2 \frac{V_{G2} - V_T}{1} \Rightarrow V_{D2} = K_2 R_L$$

$$V_{G2} = V_{D2} + V_T$$

$V_{G2} = V_{D2} + V_T$
Let the mostet be in saturation region

$$I_{D2} = \frac{1}{2} K_2 (V_{G2} - V_T)^n$$

$$I_{D2} = \frac{1}{2} K_2 (V_{G2} - V_T)^n$$

$$I_{D2} = 2 (V_{G2} - V_T)^n$$

$$K_2 = R_L (3.03 - 3.66 + 0.75) \text{ mA}$$

$$R_L = 8.2 \text{ k}\Omega + 6.48 \text{ k}\Omega = 14.68 \text{ k}\Omega$$

$$K_2 = 3.03 \text{ mA}, n = 1.07 \text{ mA}$$

$$V_{G2} = (2 - 1.07) = 0.93 > 0.7 \text{ V}$$


$$V_{D2} = (2 - 1.07) = 0.93 > 0.73 \text{ V}$$

∴ Assumption is correct.

$$V_o = V_{D2} = 0.93 \text{ V}$$

$$I_{D2} = K_2 = 1.07 \text{ mA}$$

(a)

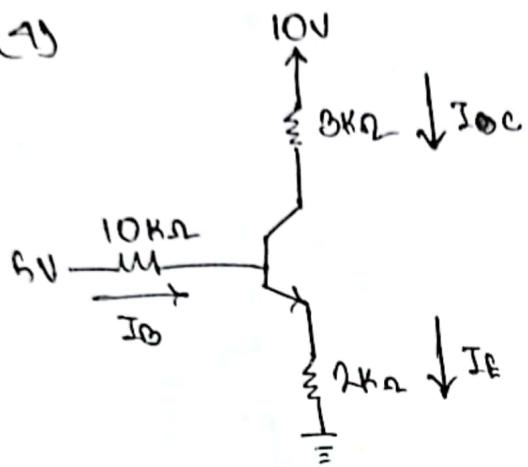

Let BJT be in active state

$$V_{BE} = 0.7V, I_C = \beta I_B = 100 I_B$$

$$5 + 10I_B + V_{BE} + 2I_E + 0 = 0$$

$$5 + 10 \left(\frac{0.99 I_E}{100} \right) + 0.7 + 2I_E = 0$$

$$I_E = -2.72 \text{ mA}$$

$$I_C = (0.99)(-2.72) = -2.69 \text{ mA}$$

$$I_B + I_C = I_E$$

$$I_B = (-2.72) - (-2.69)$$

$$I_B = -0.03 \text{ mA}$$

$$V_{CE} = V_C - V_E$$

$$= 18.07 - (-5.44)$$

$$= 23.51 \text{ V} \approx 0.2 \text{ V}$$

Given $V_C = 18V$, $V_E = 5V$
 $\beta = 100$, $V_{BE} = 0.7V$, $I_B = -0.03 \text{ mA}$
 $I_C = -2.69 \text{ mA}$, $I_E = -2.72 \text{ mA}$
 $V_{CE} = 23.51 \text{ V}$

$V_{CE} = 23.51 \text{ V}$

$\approx 23.5 \text{ V}$

$I_C = 2.69 \text{ mA}$

$\approx 2.7 \text{ mA}$

$I_B + I_C + I_E = 0$

$I_B + 2.69 + 2.72 = 0$

$I_B = -5.41 \text{ mA}$

$\approx -5.4 \text{ mA}$

$$\alpha = \frac{\beta}{1+\beta} = \frac{100}{1+100} = 0.99$$

$$I_C = \beta I_B$$

$$I_C = \alpha I_E$$

$$\beta I_B = \alpha I_E$$

$$I_B = \frac{\alpha I_E}{\beta}$$

$$I_B = \frac{0.99 \times 2.72}{100} = -0.0272 \text{ mA}$$

$$I_C = \frac{10 - V_E}{3} = \frac{10 - 5}{3} = 1.67 \text{ mA}$$

$$I_C = 1.67 \text{ mA}$$


$$V_{CE} = 10 - 3(1.67) = 18.01 \text{ V}$$

$$I_E = \frac{V_E - 0}{R_E} = \frac{5 - 0}{2} = 2.5 \text{ mA}$$

$$V_E = 5 - (-2.72)$$

$$V_E = 5 + 2.72 = 7.72 \text{ V}$$

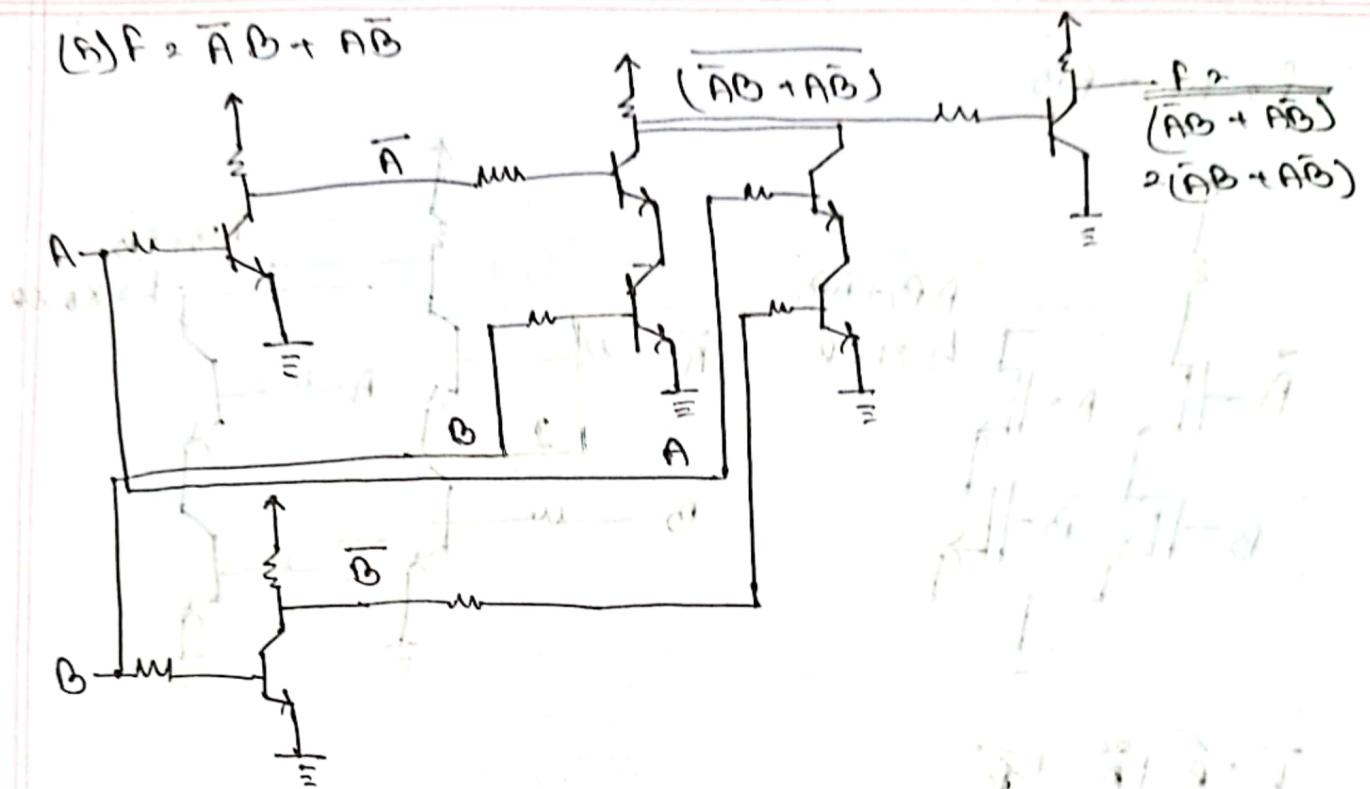
$$(g) f = \overline{A}B + A\overline{B}$$



$$(6) f \propto \overline{(AB + C + D)}$$

1	0	1
1	0	1
0	1	1
1	0	1


$$f = \bar{A}B + A\bar{B}$$

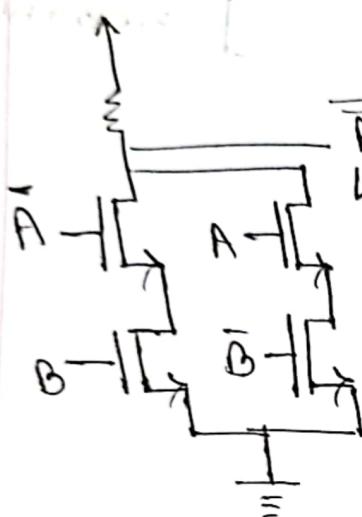

$$\bar{A}B + A\bar{B}$$

→ XNOR
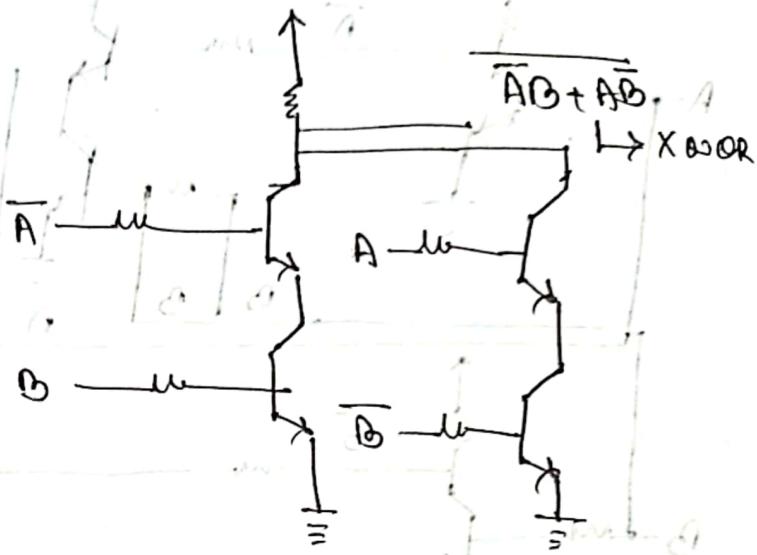
$$\bar{A}B + A\bar{B} = \bar{A}\bar{B} + A\bar{B}$$



A	B	\bar{A}	\bar{B}
0	0	1	1
0	1	1	0
1	0	0	1
1	1	0	0



A	B	vout
0	0	1
0	1	0
1	0	1
1	1	0



NAND

A=1

A=0

BJT

active: $V_{BE} \approx 0.7V$

$$I_C = \beta I_B \quad \alpha = \beta \theta \quad \frac{I_C}{I_B} = \alpha B$$

$$I_C = \alpha I_B$$

saturation: $V_{BE} \approx 0.8V$

$$V_{CE} \approx 0.2V$$

$$\frac{I_C}{I_B} \approx AB$$

cutoff: $I_C = I_B = I_E = 0mA$

$$V_{BE} \approx 0.7V$$

MOSFET

saturation: $V_{DS} \leq VT \approx VT$


$$V_{DS} \approx V_{DS} \quad I_D = \frac{1}{2} K V_{DS}^2$$

triode: $V_{DS} \approx VT$, $V_{DS} \approx V_{DS}$

$$I_D = K (V_{DS} - \frac{1}{2} V_{DS}^2)$$



cutoff: $I_D \approx 0mA$, $V_{DS} \approx VT$

LAB

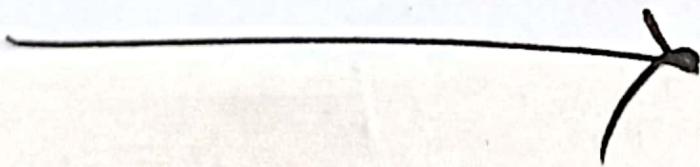


TUESDAY

DATE: 31/01/23

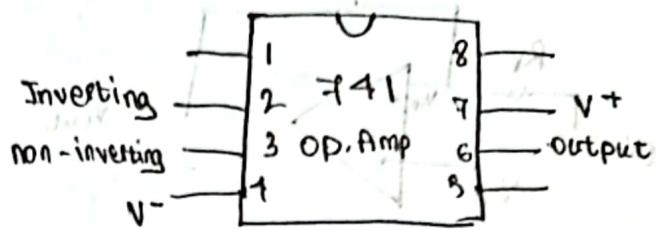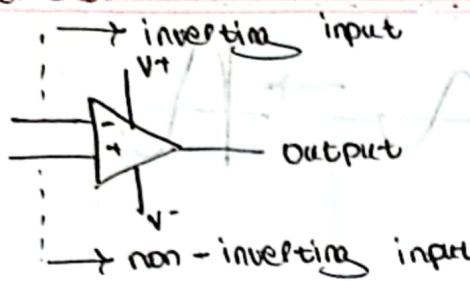

comparator


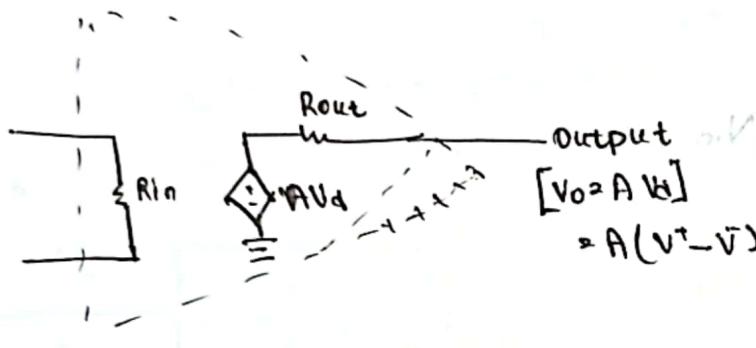


for ideal op. amp



$$R_{in} \rightarrow \infty$$

$$R_{out} \rightarrow 0$$

$$A \rightarrow \infty$$

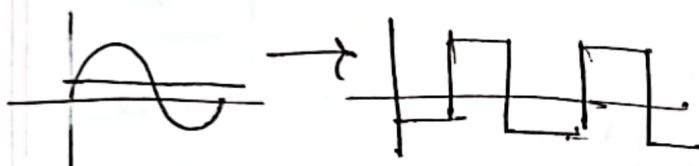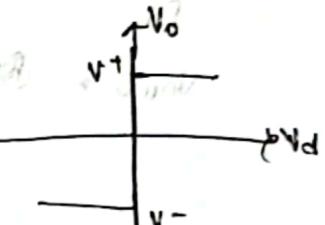

I/P $\xrightarrow{\text{Op}}$ feedback

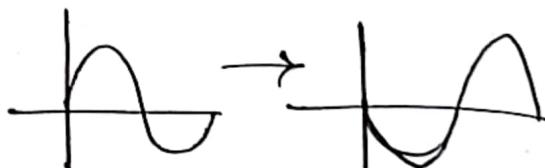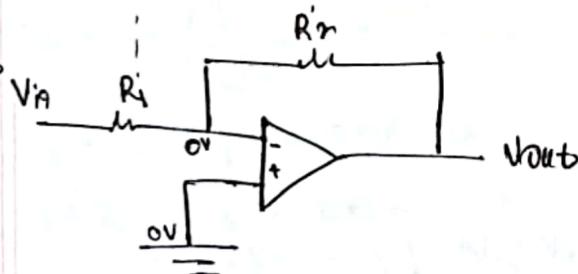

$$\frac{V_{in} - 0}{R_1} = \frac{0 - V_{out}}{R_2}$$



$\rightarrow R_2 \rightarrow$ phase shift

$$V_{out} = \left(\frac{-R_2}{R_1} \right) V_{in}$$

amplification

$\xrightarrow{\quad} \xrightarrow{\quad} \xrightarrow{\quad} \xrightarrow{\quad} \xrightarrow{\quad} \xrightarrow{\quad} \xrightarrow{\quad} \xrightarrow{\quad}$

Non-inverting
amplifiers

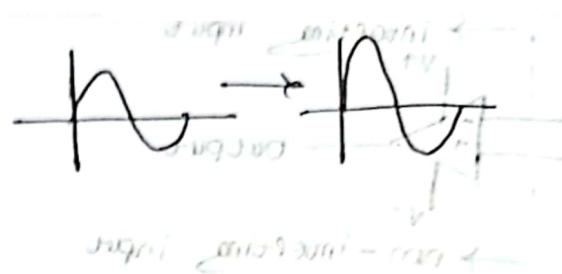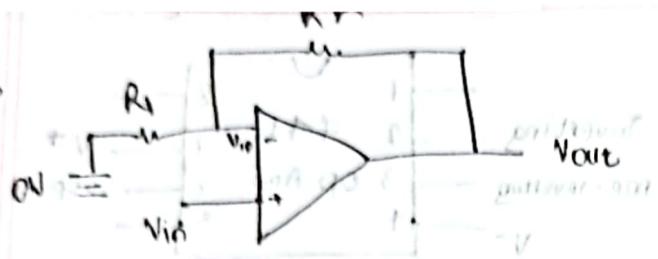

$$0 - \frac{V_{in}}{R_1} \rightarrow \frac{V_{in} - V_{out}}{R_2} = 0$$

$$V_{out} = \frac{R_2}{R_1} \left(1 + \frac{R_2}{R_1} \right) \times V_{in}$$

always +ve



$$200V = 0 \Rightarrow 0 = 0V$$


$$200V = 0 \Rightarrow 0 = 0V$$

$$0V \left(\frac{R_2}{R_1} \right) = 200V$$

canceling



Decision Block

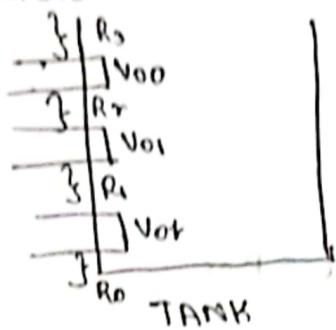

water level

18V $[5, 5, 5] \rightarrow R_0$

11V $[1, 8, 5] \rightarrow R_1$

7V $[1, 1, 5] \rightarrow R_2$

3V $[1, 1, 1] \rightarrow R_3$


Signal indicates of UCL
Wind $\Rightarrow (V_{01} + V_{02} + V_{03}) \frac{1}{n}$

to keep the output in range
Vout $\propto \frac{1}{n}$

Vout \propto depth of water

when probe in water | when probe out of water

V0 = 18V

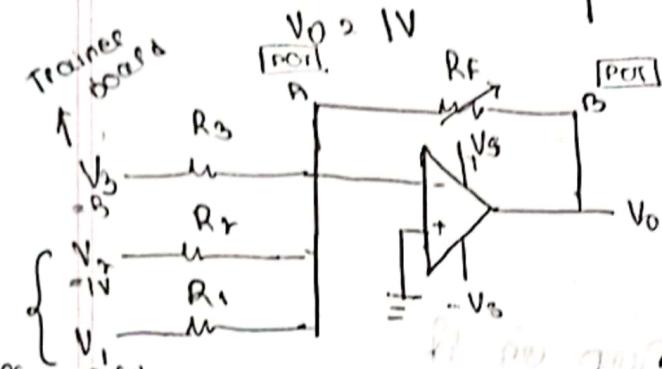

MUST SHORT GROUND OF TRAINED BOARD AND POWER SUPPLY

$$V_0 = + \frac{R_f}{R_3} V_3, V_{00} = \frac{R_f}{R_2} V_2, V_{01} = \frac{R_f}{R_1} V_1$$

$$V_0 = - \left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right)$$



$$R_f = 100k \text{ or } 50k, 25k \text{ etc.}$$

$$R_1 = R_2 = R_3 = 100k$$


$$V_0 = -(V_1 + V_2 + V_3) + -(V_1 + V_2 + V_3) \times 0.5 = -(V_1 + V_2 + V_3) \times 0.25$$

to make the Rf smaller


Potentiometer

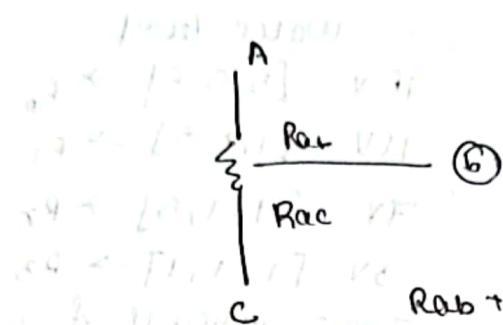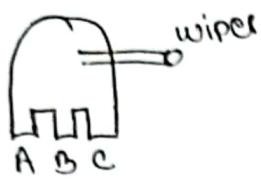

$$R_{ab} + R_{bc} = R_{ac}$$

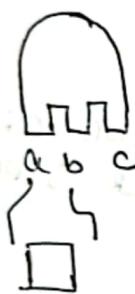


Decision Block

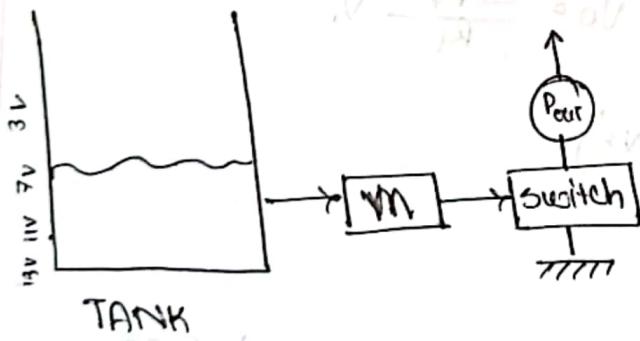

level of water
V1

W1, L2 → Out of tank off

2 V_{IN}

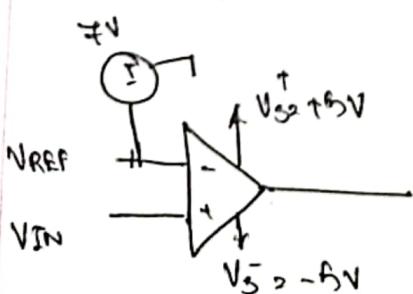

$$V^+ \gamma \gamma \Rightarrow V_o = V_s^+ \\ V^+ \wedge V^- \Rightarrow V_o = V_s^+ - V_s^-$$

Pump on if


V_{IN} > V_{REF} \Rightarrow Pump on
AV



Pump off if

V_{IN} < V_{REF} \Rightarrow Pump off
-AV







Output level (AV), voltage, 2V, pump off, 2V

Schmitt Trigger

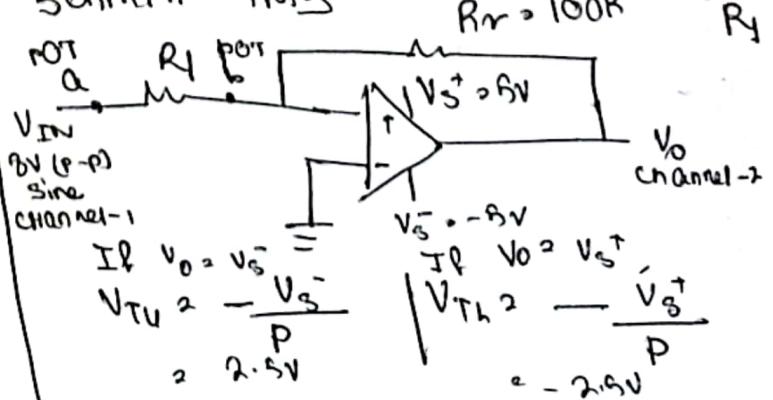


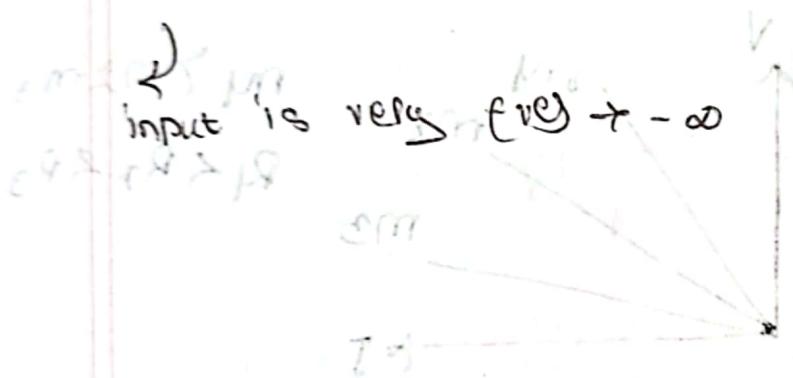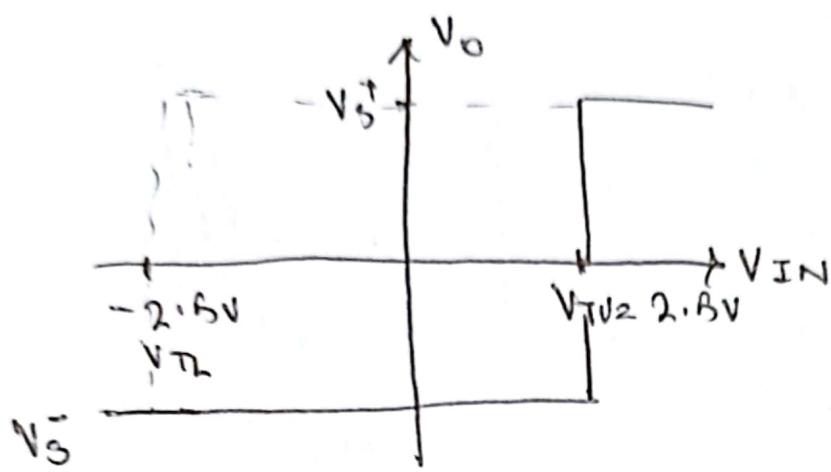


I-V characteristics

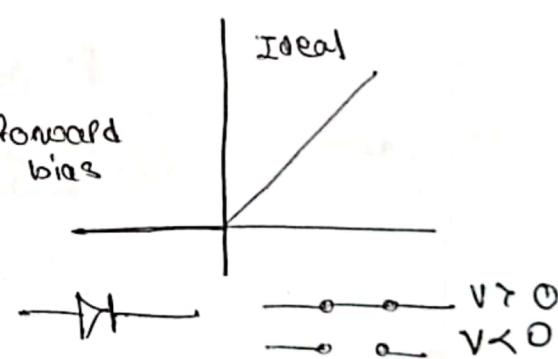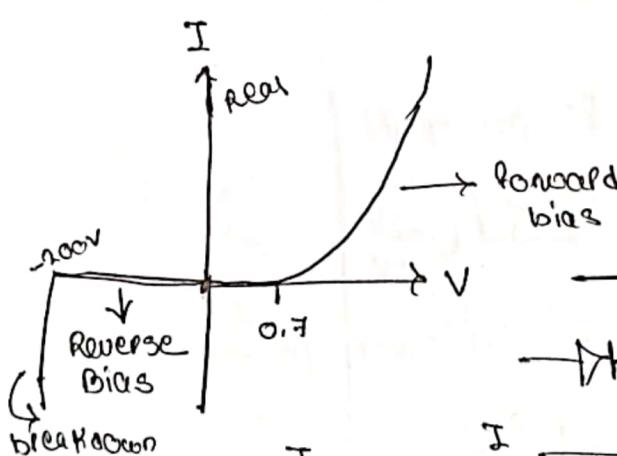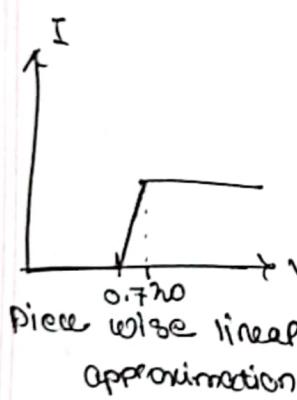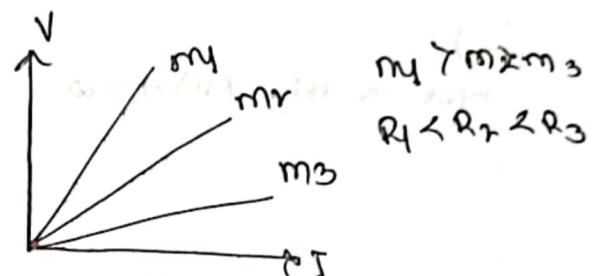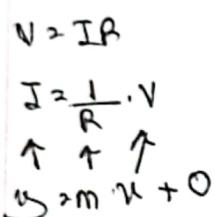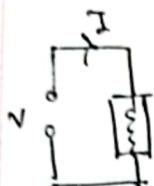

Diode

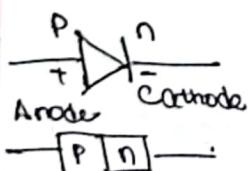

P-n junction diode

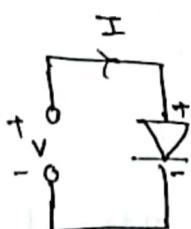

A diagram of a cylindrical capacitor. It has two leads extending from the top and bottom. The top lead is labeled with a '+' sign and the bottom lead is labeled with a '-' sign, indicating the polarity of the capacitor.

$$I_d = I_s \left\{ e^{\frac{\sqrt{D}}{nV_T}} - 1 \right\}$$

* Depletion
layer : barrier
b/w P & n

↓ depletion when V_{BE} is from
reverse saturation current target: n moves to the
thermally free space in P_e
applied voltage barrier is erected.
intrinsic factor \downarrow voltage

$$V = IR$$

$$I = \frac{V}{R} \rightarrow \text{volt}$$

$$I = \text{mA}$$

$$\frac{V}{10^3} = \frac{10^{-3}}{10^3} \rightarrow \frac{1}{10^3} = 10^{-3}$$

$$10^{-3} = 10^{-3}$$

Efficiency

$$I_d = I_s \left\{ \exp \left(\frac{V_d}{nV_T} \right)^2 - 1 \right\}$$

For Zener Diode

$$I_d = I_s \exp \left(\frac{V_d}{nV_T} \right)$$

$$\frac{1}{nV_T} = \alpha$$


$$I_d = I_s \exp(\alpha V_d)$$

$$I_{d1} = I_s \exp(\alpha V_{d1}) \rightarrow \textcircled{1}$$

$$I_{d2} = I_s \exp(\alpha V_{d2}) \rightarrow \textcircled{2}$$


$$\frac{\textcircled{1}}{\textcircled{2}} \Rightarrow \frac{I_{d1}}{I_{d2}} = \exp \alpha (V_{d1} - V_{d2})$$
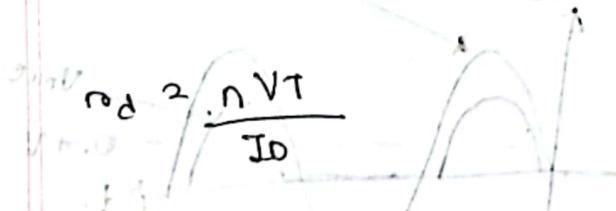
$$\alpha = \ln \left(\frac{I_{d1}}{I_{d2}} \right) \frac{1}{V_{d1} - V_{d2}}$$





\rightarrow Zener diode \rightarrow operate at breakdown

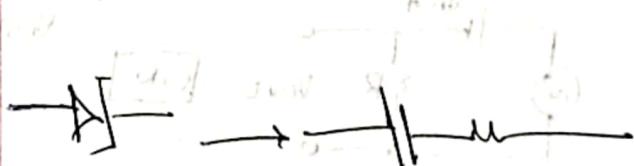$nV_T \rightarrow$ does not go beyond V_Z



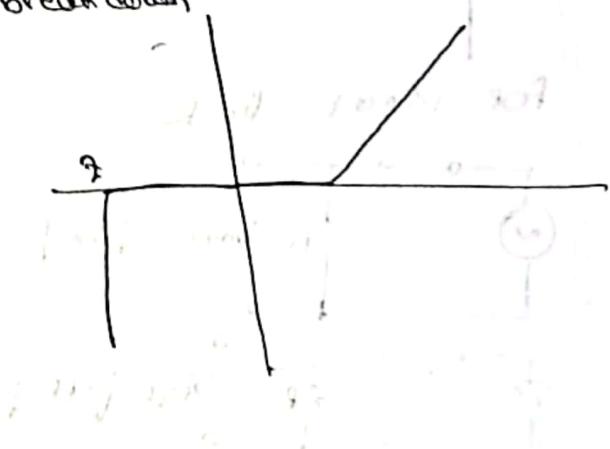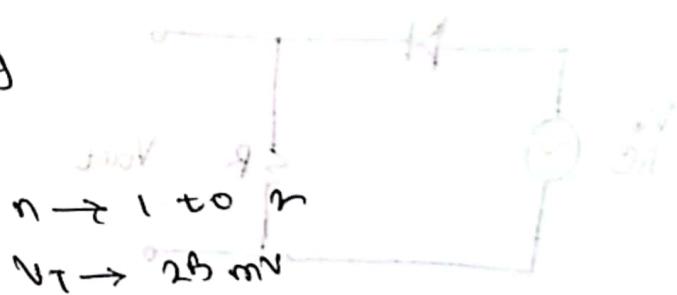\rightarrow Zener diode current \rightarrow I_L



LAB
4

TUESDAY

$$90\text{ V} \\ 220 \text{ V AC} \\ 50 \text{ Hz}$$

AC


DATE: 28/02/23

Half wave and full wave rectifier ($\frac{1}{2}V_{AC}$) graph & bkt



AC \rightarrow DC





220 V AC
50 Hz

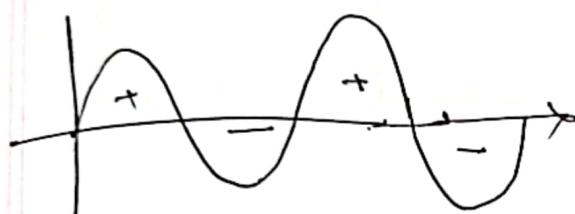

Half-wave rectifier:-

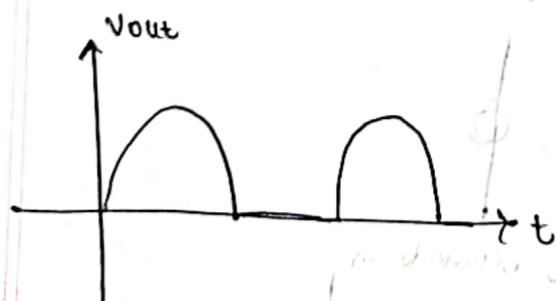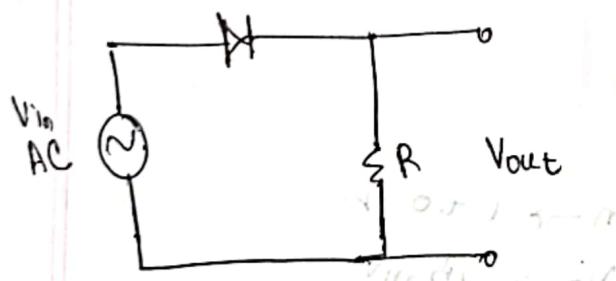


For ideal diode

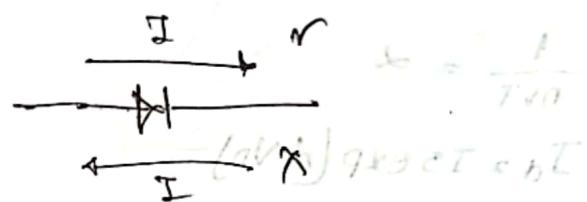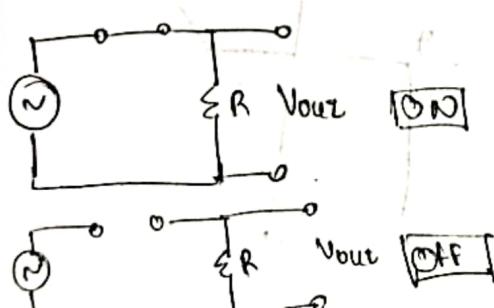


① \rightarrow 60 V DC graph = bkt

② \rightarrow 60 V DC graph = bkt
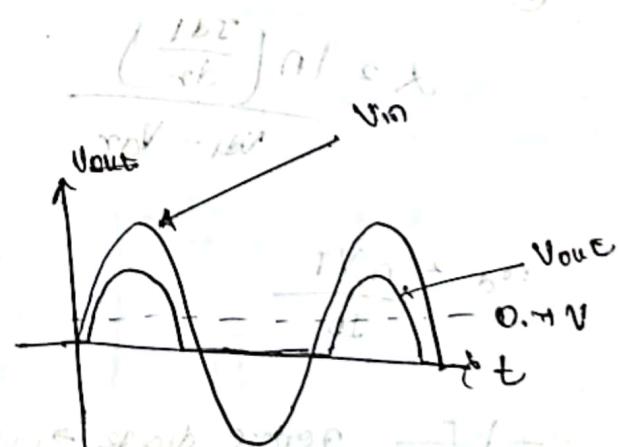
$$(60V - 1.6V) \text{ graph} = \frac{10V}{50\text{Hz}} = \text{bkt}$$



for real diode

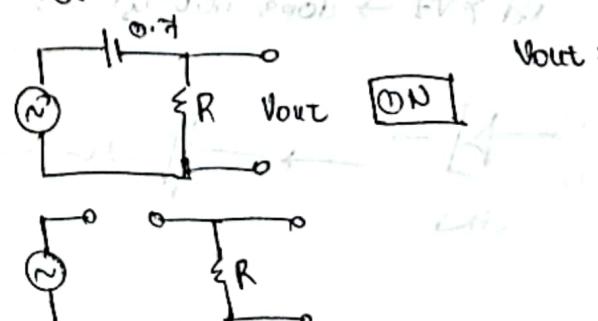


$$0.7V \text{ drop} = BV$$

$$V_{out} = V_{in} - 0.7V$$

ac/dec: 1111

$$V_{out, np} = V_m - 0.7V$$

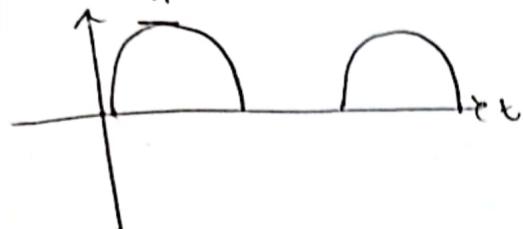

$$No \ 2 \ V_{DC} + V_{AC}$$

$$V_{DC} = \frac{V_m}{\pi} = \frac{V_{BO}}{\pi}$$

$$V_{AC} = V_{rms}$$


Position scale of Vin & Vout

should be 2V.

* Scale ch1 = scale ch2 = 2V

* Bias ch1 = Bias ch2 = 0V

with capacitor

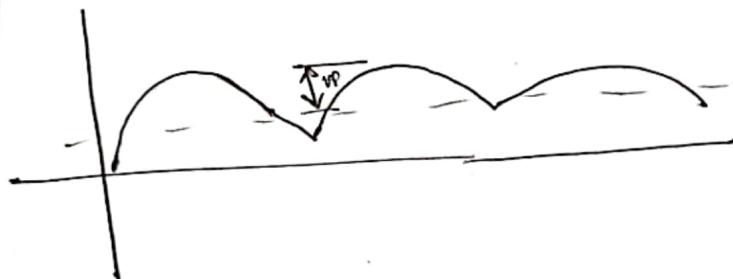

$$\frac{V_p}{V_F} = \frac{V_p}{V_{DC}}$$

$$n = \frac{V_{rms}}{V_{avg}} \quad [Ripple Factor]$$

$$n = \frac{V_{AC}}{V_{DC}}$$